

# Design of Digital Circuits

## Lecture 7: Sequential Logic Design

Prof. Onur Mutlu

ETH Zurich

Spring 2018

15 March 2018

# Readings

---

- Please study Slides 102-120 from Lecture 6 on your own
- This week
  - Sequential Logic
    - P&P Chapter 3.4 until end + H&H Chapter 3 in full
  - Hardware Description Languages and Verilog
    - H&H Chapter 4 in full
  - Timing and Verification
    - H&H Chapters 2.9 and 3.5 + Chapter 5
- Next week
  - Von Neumann Model, LC3, and MIPS
    - P&P Chapter 4-5 + H&H Chapter 6
  - Digital Building Blocks
    - H&H Chapter 5

# What We Will Learn Today

---


- Circuits that can store information
  - R-S Latch
  - Gated D Latch
  - D Flip-Flop
  - Register
- Finite State Machines (FSM)
  - Moore Machine
  - Mealy Machine
- Verilog implementations of sequential circuits

# Circuits that Can Store Information
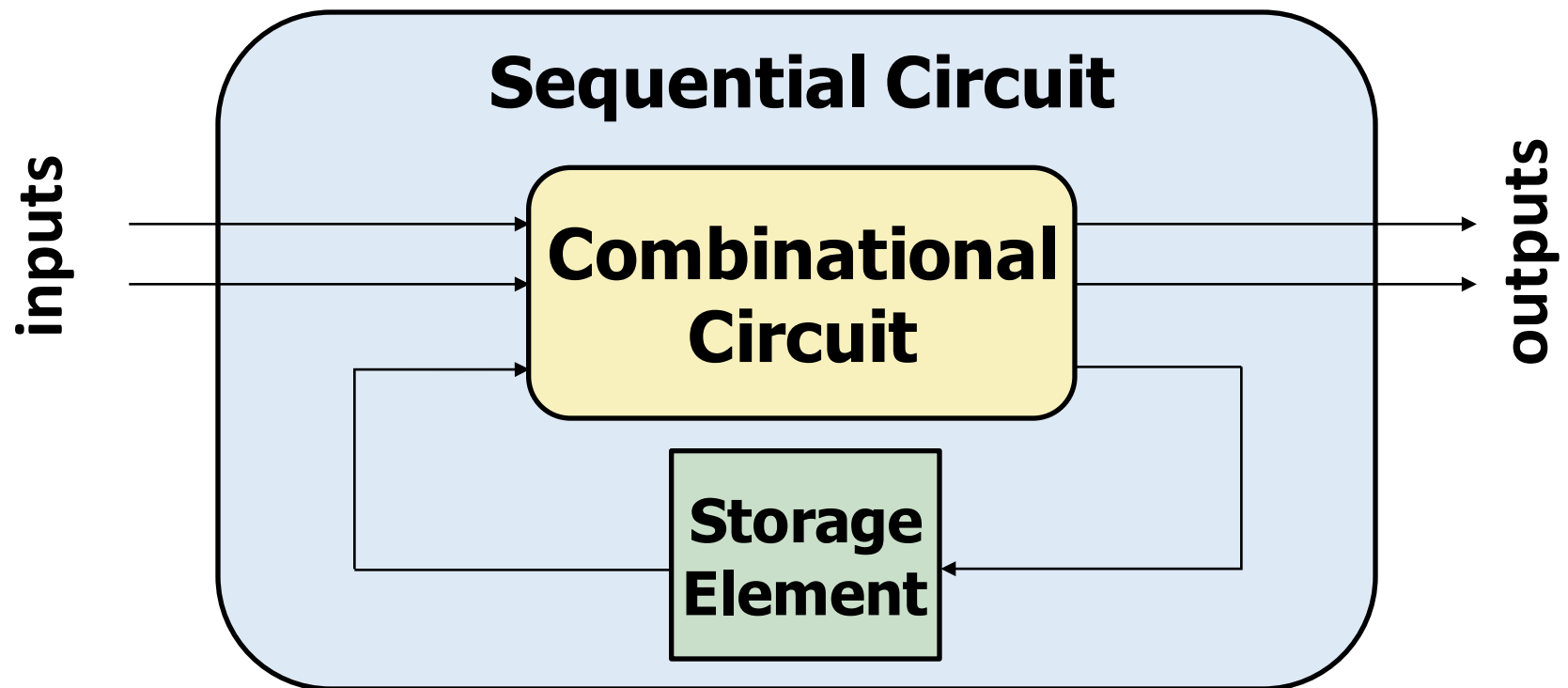
# Introduction

---


- Combinational circuit output depends **only** on **current** input
- We want circuits that produce output depending on **current** and **past** input values – circuits with **memory**
- How can we design a circuit that **stores information**?



# Basic Storage Element: The R-S Latch

 
# The R-S (Reset-Set) Latch

- The simplest implementation of the **R-S Latch**
  - Two **NAND gates** with outputs feeding into each other's input
  - Data is stored at **Q** (inverse at **Q'**)
  - **S** and **R** inputs are held at 1 in *quiescent (idle) state*
    - **S (set)**: drive **S** to 0 (keeping **R** at 1) to change **Q** to 1
    - **R (reset)**: drive **R** to 0 (keeping **S** at 1) to change **Q** to 0
- **S** and **R** should never **both** be 0 at the same time



Input		Output
R	S	Q
1	1	$Q_{\text{prev}}$
1	0	1
0	1	0
0	0	Invalid

# Why not $R=S=0$ ?

 

Input		Output
R	S	Q
1	1	$Q_{\text{prev}}$
1	0	1
0	1	0
0	0	Invalid

1. If  $R=S=0$ ,  $Q$  and  $Q'$  will both settle to 1, which **breaks** our invariant that  $Q = !Q'$
2. If  $S$  and  $R$  transition back to 1 at the same time,  $Q$  and  $Q'$  begin to oscillate between 1 and 0 because their final values depend on each other (**metastability**)
  - This eventually settles depending on **variation in the circuits** (more **metastability** to come in **Lecture 8**)




# The Gated D Latch
 
# The Gated D Latch


---

- How do we **guarantee** correct operation of an R-S Latch?



 
# The Gated D Latch

- How do we **guarantee** correct operation of an R-S Latch?
  - Add two more NAND gates!



- **Q** takes the value of **D**, when **write enable (WE)** is set to 1
- **S** and **R** can never be 0 at the same time!

# The Gated D Latch

 


Input		Output
WE	D	Q
0	0	$Q_{\text{prev}}$
0	1	$Q_{\text{prev}}$
1	0	0
1	1	1

# The Register
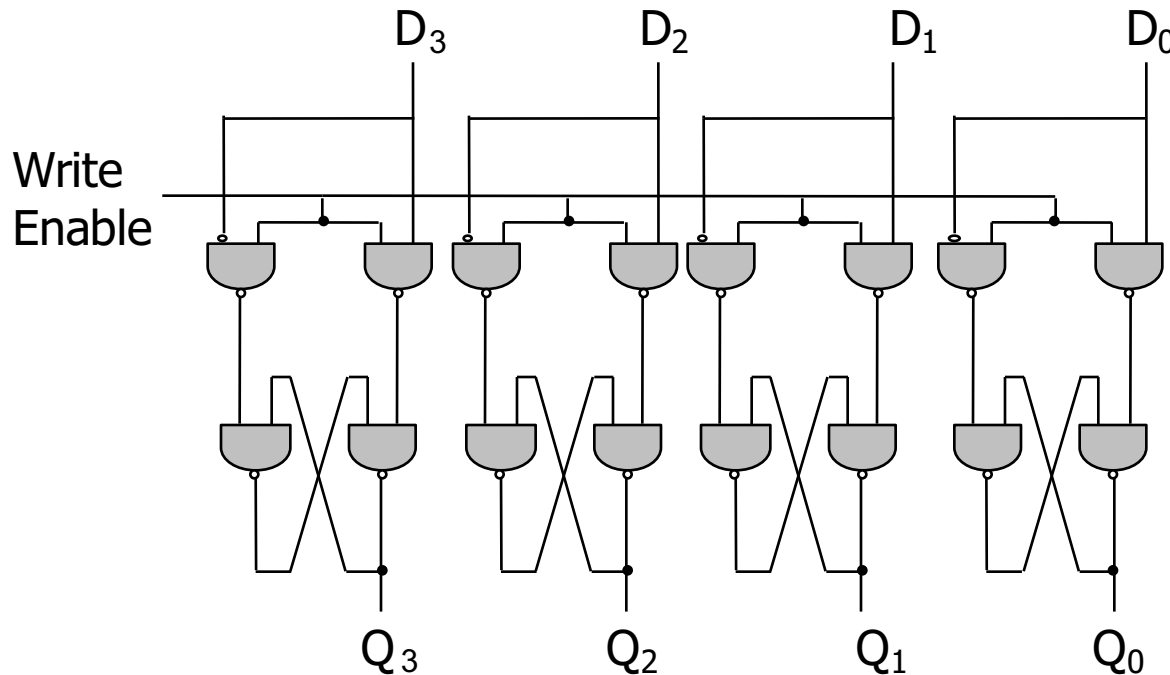
# The Register

How can we use D latches to store **more** data?

- Use **more** D latches!
- A single WE signal for all latches for simultaneous writes



Here we have a **register**, or a structure that stores more than one bit and can be read from and written to


This **register** holds 4 bits, and its data is referenced as Q[3:0]

# The Register

---

How can we use D latches to store **more** data?

 - Use **more** D latches!
- A single WE signal for all latches for simultaneous writes



Here we have a **register**, or a structure that stores more than one bit and can be read from and written to

This **register** holds 4 bits, and its data is referenced as  $Q[3:0]$

# Memory



# Memory

---

- **Memory** is comprised of locations that can be written to or read from. An example memory array with 4 locations:

<b>Addr(00):</b> 0100 1001	<b>Addr(01):</b> 0100 1011
<b>Addr(10):</b> 0010 0010	<b>Addr(11):</b> 1100 1001


- Every unique location in memory is indexed with a unique **address**. 4 locations require 2 address bits ( $\log[\text{\#locations}]$ ).
- **Addressability**: the number of bits of information stored in each location. This example: addressability is 8 bits.
- The full set of unique locations in memory is referred to as the **address space**.
- Typical memory is **MUCH** larger (billions of locations)

# Addressing Memory

**Let's implement a simple memory array with:**

- 3-bit addressability & address space size of 2 (total of 6 bits)

## 1 Bit

 

## 6-Bit Memory Array


	Bit <sub>2</sub>	Bit <sub>1</sub>	Bit <sub>0</sub>
Addr(0)	Bit <sub>2</sub>	Bit <sub>1</sub>	Bit <sub>0</sub>
Addr(1)	Bit <sub>2</sub>	Bit <sub>1</sub>	Bit <sub>0</sub>

# Reading from Memory

---
 
## How can we select the address to read?

- Because there are 2 addresses, address size is  $\log(2)=1$  bit




# Reading from Memory

---
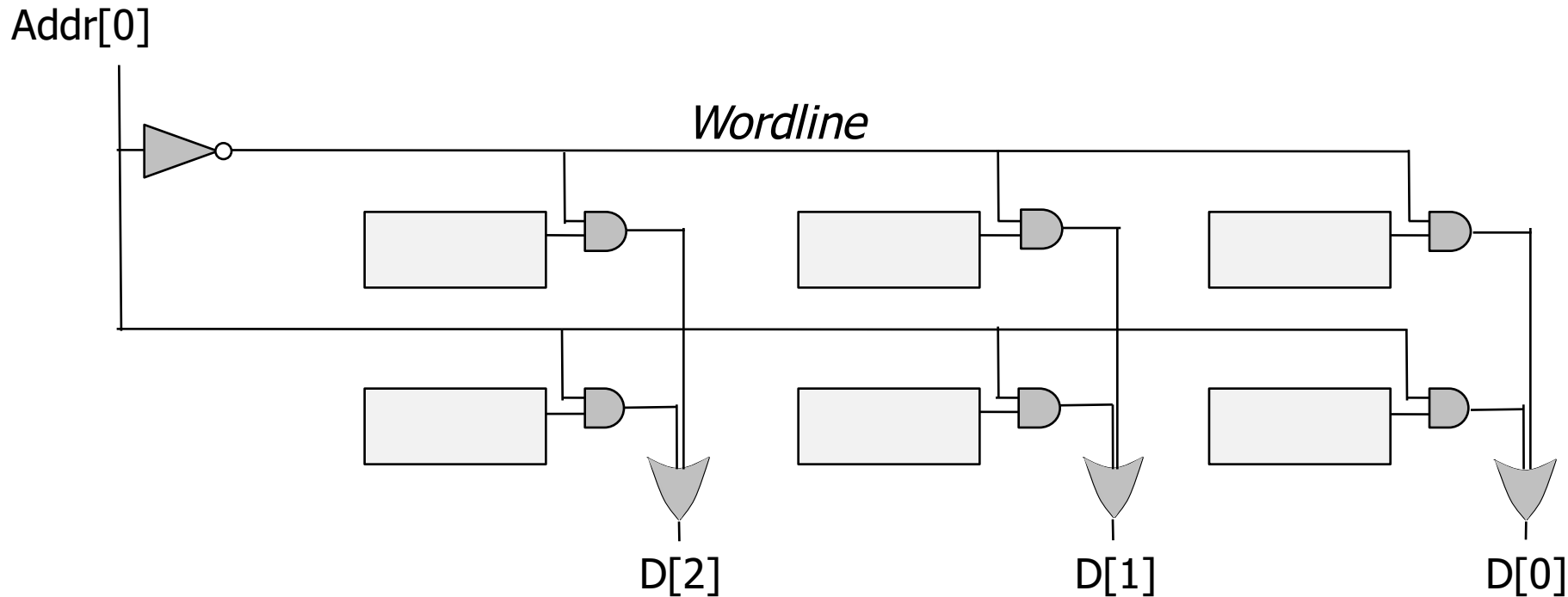
## How can we select the address to read?


- Because there are 2 addresses, address size is  $\log(2)=1$  bit



# Reading from Memory
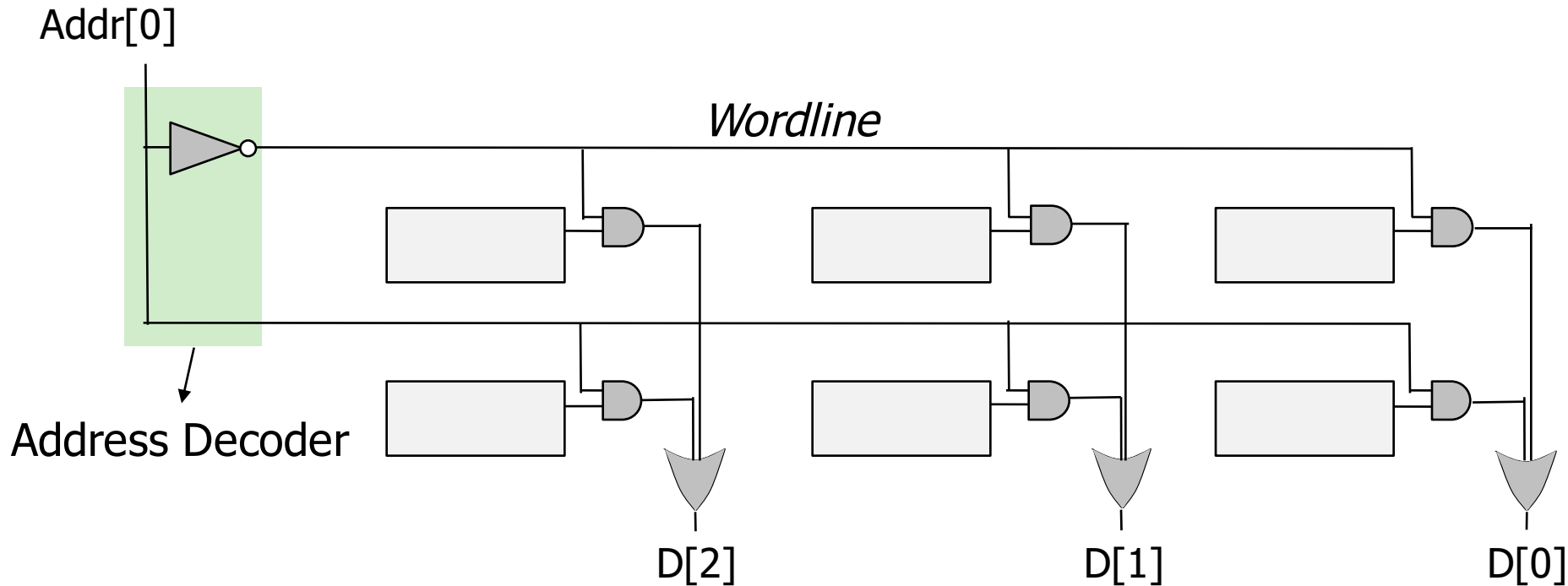
## How can we select the address to read?


- Because there are 2 addresses, address size is  $\log(2)=1$  bit



# Reading from Memory
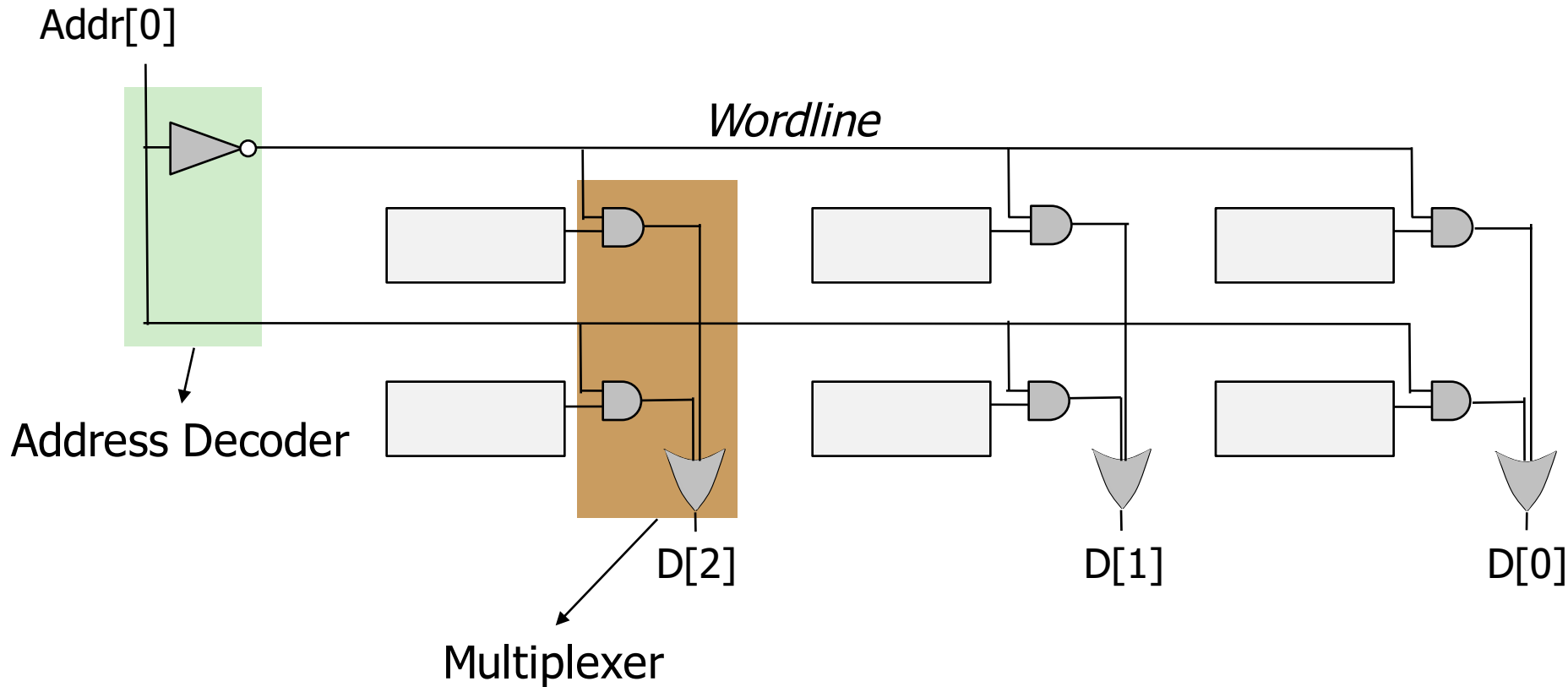
## How can we select the address to read?


- Because there are 2 addresses, address size is  $\log(2)=1$  bit



# Writing to Memory

---

 
**How can we select the address and write to it?**



# Writing to Memory

## How can we select the address and write to it?


- Input is indicated with  $D_i$

 




# Putting it all Together
 
## Enable reading and writing to a memory array





# A Bigger Memory Array

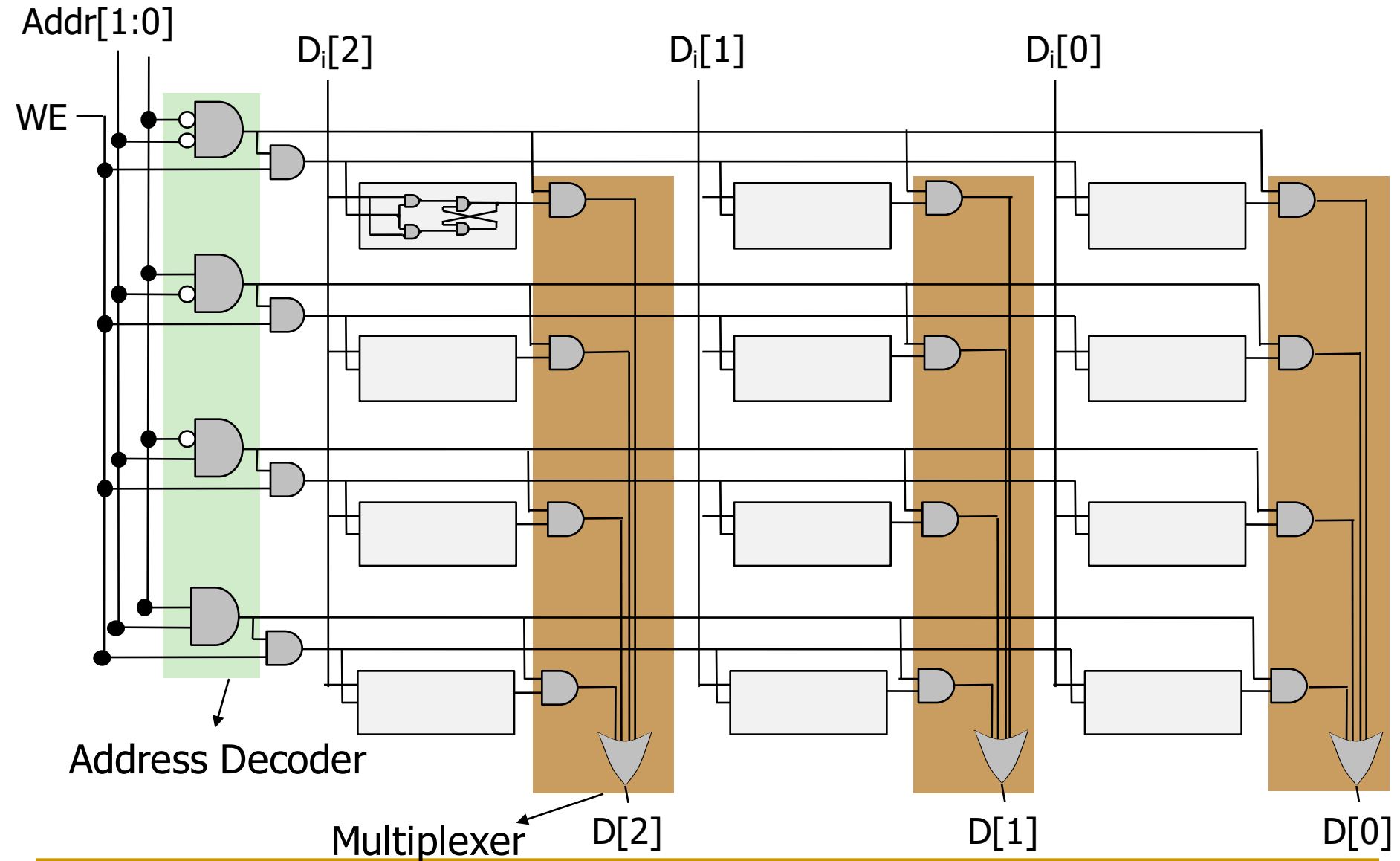

# Sequential Logic Circuits

# Sequential Logic Circuits

---

- We have looked at designs of circuit elements that can **store information**
- Now, we will use these elements to build circuits that **remember** past inputs



## Combinational

Only depends on current inputs



## Sequential

Opens depending on past inputs

# State

---

- In order for this lock to work, it has to keep track (**remember**) of the past events!
- If passcode is **R13-L22-R3**, sequence of **states** to unlock:
  - A. The lock is not open (locked), and no relevant operations have been performed
  - B. Locked but user has completed R13
  - C. Locked but user has completed L22
  - D. Locked but user has completed R3
  - E. The lock can now be opened
- The **state** of a system is a snapshot of all relevant elements of the system at the moment of the snapshot
  - ❑ To open the lock, **states A-E must be completed in order**
  - ❑ If anything else happens (e.g., L5), lock **returns** to state A




# Another Simple Example of State


---

- A standard Swiss traffic light has **4 states**

 - A. Green
- B. Yellow
- C. Red
- D. Red and Yellow




 - The sequence of these states are always as follows



# Changing State: The Notion of Clock (I)

---

 

- When should the light change from one state to another?
- We need a **clock** to dictate when to change state
  - Clock signal alternates between 0 & 1



- At the start of a clock cycle ( ), system state changes
  - During a clock cycle, the state stays constant
  - In this traffic light example, we are assuming the traffic light stays in each state an equal amount of time



# Changing State: The Notion of Clock (II)

---

- **Clock** is a general mechanism that **triggers transition from one state to another** in a sequential circuit
- Clock **synchronizes state changes** across many sequential circuit elements
- Combinational logic evaluates for the length of the clock cycle
- Clock cycle should be chosen to accommodate maximum combinational circuit delay
  - More on this later, when we discuss timing

# Finite State Machines

# Finite State Machines

---

- What is a **Finite State Machine** (FSM)?
  - **A discrete-time model** of a stateful system
  - Each state represents a snapshot of the system at a given time
- An FSM pictorially shows
  - the set of all possible **states** that a system can be in
  - how the system transitions from one state to another
- An FSM can model
  - A traffic light, an elevator, fan speed, a microprocessor, etc.
- **An FSM enables us to pictorially think of a stateful system using simple diagrams**

# Finite State Machines (FSMs) Consist of:

---


## ■ Five elements:

1. A **finite** number of states
  - **State**: snapshot of all relevant elements of the system at the time of the snapshot
2. A **finite** number of external inputs
3. A **finite** number of external outputs
4. An explicit specification of all state transitions
  - How to get from one state to another
5. An explicit specification of what determines each external output value
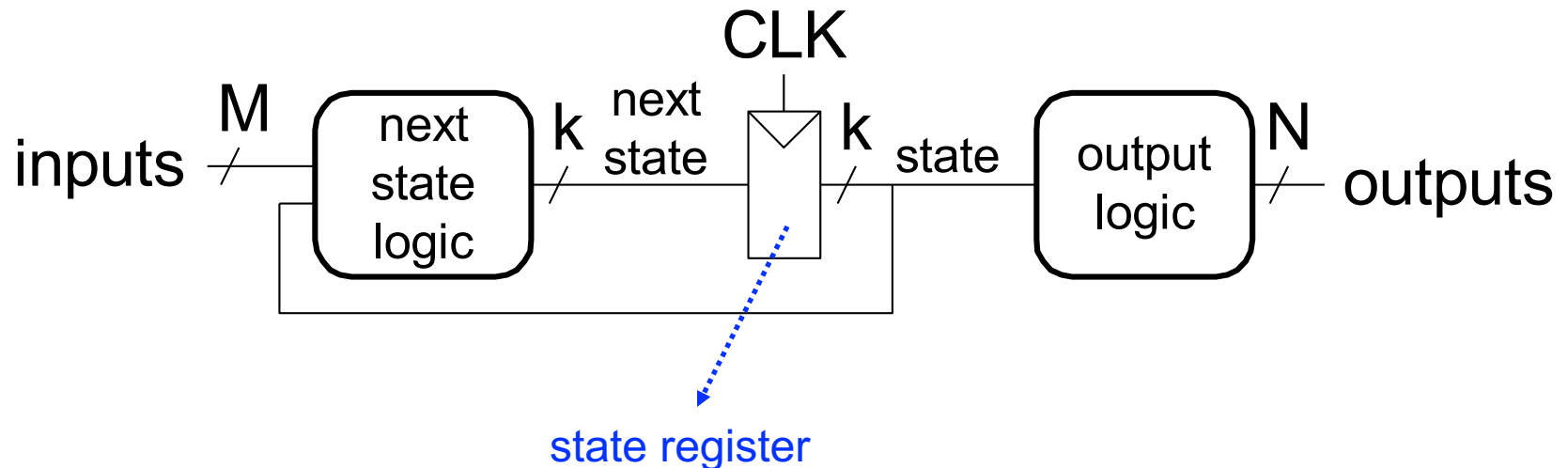
# Finite State Machines (FSMs)

---

- Each FSM consists of three separate parts:
  - next state logic
  - state register
  - output logic




At the beginning of the clock cycle, next state is latched into the state register

# Finite State Machines (FSMs) Consist of:

---


 
## ■ Sequential circuits

- State register(s)
  - Store the current state and
  - Load the next state at the clock edge


  
## ■ Combinational Circuits


- Next state logic
  - Determines what the next state will be
- Output logic
  - Generates the outputs



# Finite State Machines (FSMs) Consist of:


 
## ■ Sequential circuits

- State register(s)
  - Store the current state and
  - Load the next state at the clock edge



  
## ■ Combinational Circuits

- Next state logic
  - Determines what the next state will be
- Output logic
  - Generates the outputs



 
# State Register Implementation

- How can we implement a **state register**? Two properties:
  - We need to store data at the **beginning** of every clock cycle



 
- The data must be **available** during the entire clock cycle






# The Problem with Latches

Recall the  
Gated D Latch

 


 - Currently, we **cannot** simply wire a clock to WE of a latch
  - ❑ **When the clock is high,** Q will not take on D's value AND
  - ❑ **When the clock is low,** the latch will propagate D to Q




# The Problem with Latches

Recall the  
Gated D Latch

 


 - Currently, we **cannot** simply wire a clock to WE of a latch
  - ❑ **When the clock is high,** Q will not take on D's value AND
  - ❑ **When the clock is low,** the latch will propagate D to Q



# The Problem with Latches

Recall the  
Gated D Latch

 


How can we change the latch, so that

**1) D** (input) is **observable** at **Q** (output) **only** at the **beginning of next** clock cycle?

**2) Q** is **available for the full clock cycle**

# The D Flip-Flop

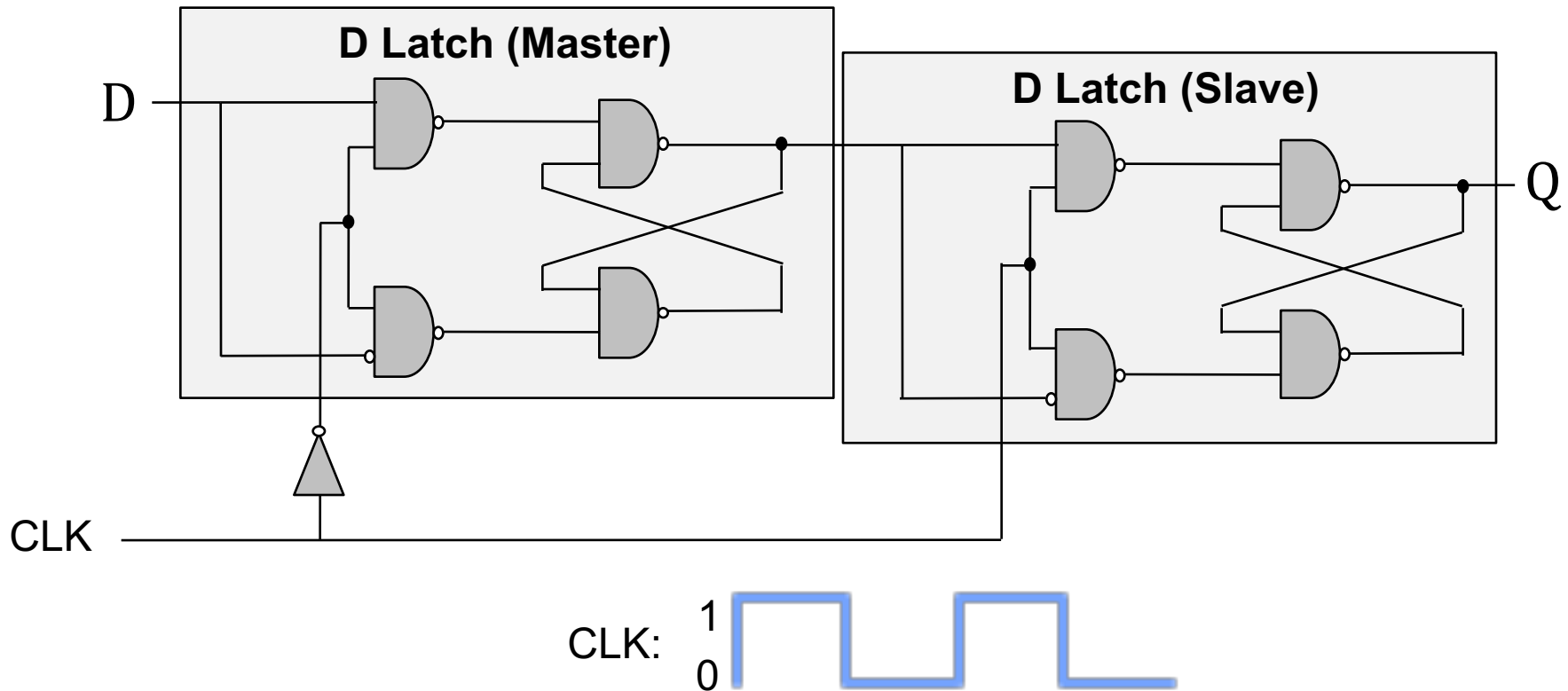
- 1) state change on clock edge, 2) data available for full cycle



- When the clock is low, master propagates **D** to the input of slave (**Q** unchanged)
- Only when the clock is high, slave latches **D** (**Q stores D**)
  - At the rising edge of clock (clock going from 0→1), **Q** gets assigned **D**

# The D Flip-Flop

 
- 1) state change on clock edge, 2) data available for full cycle



- At the rising edge of clock (clock going from 0->1), **Q** gets assigned **D**
- At all other times, Q is unchanged

# The D Flip-Flop

- How do we implement this?

 

We can use these **Flip-Flops** to implement the state register!

- At the rising edge of clock (clock going from 0->1), **Q** gets assigned **D**
- At all other times, Q is unchanged


# Rising-Edge Triggered Flip-Flop

---

- **Two inputs:** CLK, D

- **Function**


 
- The flip-flop “samples” **D** on the rising edge of CLK (**positive edge**)
- When CLK rises from 0 to 1, **D** passes through to **Q**
- Otherwise, **Q** holds its previous value
- **Q** changes **only** on the rising edge of CLK



- A flip-flop is called an **edge-triggered device** because it is activated on the clock edge
  
# Register

- Multiple parallel flip-flops, each of which store 1 bit



**This line represents 4 wires**

**This register stores 4 bits**




# Finite State Machines (FSMs)

---

- Next state is determined by the current state and the inputs
- Two types of finite state machines differ in the **output logic**:
  - **Moore FSM**: outputs depend only on the current state


Moore FSM

 


# Finite State Machines (FSMs)

- Next state is determined by the current state and the inputs
- Two types of finite state machines differ in the **output logic**:
  - **Moore FSM**: outputs depend only on the current state
  - **Mealy FSM**: outputs depend on the current state and the inputs

Moore FSM

 


Mealy FSM

 
 
# Finite State Machine Example


- “Smart” traffic light controller
  - **2 inputs:**
    - Traffic sensors:  $T_A$ ,  $T_B$  (TRUE when there's traffic)
  - **2 outputs:**
    - Lights:  $L_A$ ,  $L_B$  (Red, Yellow, Green)


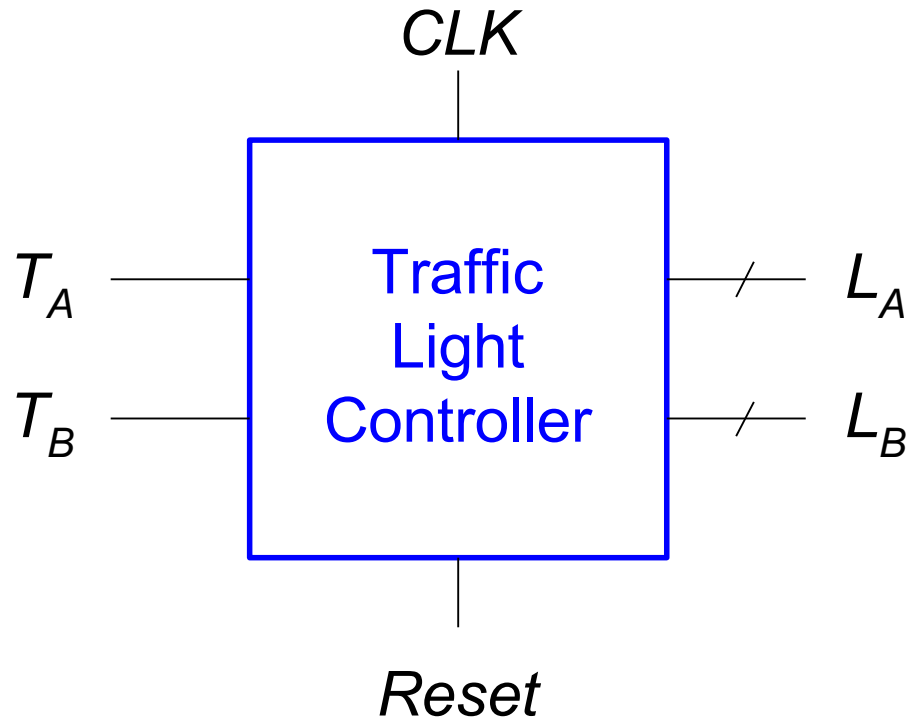
# Finite State Machine Black Box


---

- **Inputs:** CLK, Reset,  $T_A$ ,  $T_B$
- **Outputs:**  $L_A$ ,  $L_B$




 
# Finite State Machine Transition Diagram

- **Moore FSM:** outputs labeled in each state
  - **States:** Circles
  - **Transitions:** Arcs



 
 
# Finite State Machine Transition Diagram

- **Moore FSM:** outputs labeled in each state
  - **States:** Circles
  - **Transitions:** Arcs



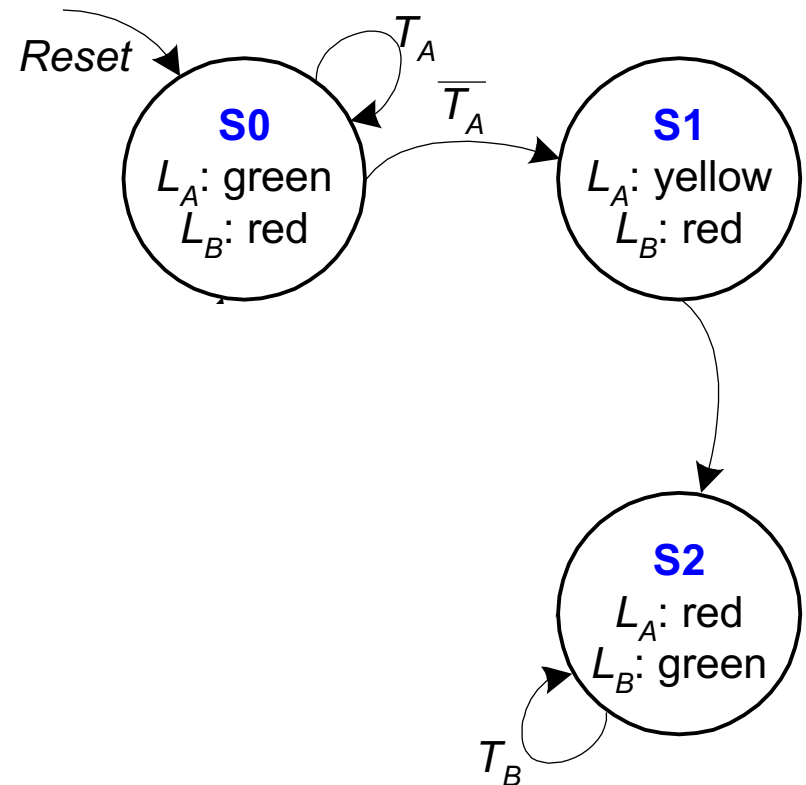
 
# Finite State Machine Transition Diagram

- **Moore FSM:** outputs labeled in each state
  - **States:** Circles
  - **Transitions:** Arcs


  
# Finite State Machine Transition Diagram



- **Moore FSM:** outputs labeled in each state
  - **States:** Circles
  - **Transitions:** Arcs




  
# Finite State Machine Transition Diagram


- **Moore FSM:** outputs labeled in each state
  - **States:** Circles
  - **Transitions:** Arcs



# Finite State Machines


## State Transition Table

# FSM State Transition Table

 


Current State	Inputs		Next State
S	$T_A$	$T_B$	S'
S0	0	X	
S0	1	X	
S1	X	X	
S2	X	0	
S2	X	1	
S3	X	X	

# FSM State Transition Table

 

Current State	Inputs		Next State
S	$T_A$	$T_B$	S'
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0


# FSM State Transition Table

 

Current State	Inputs		Next State
S	$T_A$	$T_B$	S'
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

State	Encoding
S0	00
S1	01
S2	10
S3	11


# FSM State Transition Table

 

Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

# FSM State Transition Table

 


Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$S'_1 = ?$

# FSM State Transition Table

 


Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = (\overline{S_1} \cdot S_0) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B}) + (S_1 \cdot \overline{S_0} \cdot T_B)$$



# FSM State Transition Table

 


Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = (\overline{S_1} \cdot S_0) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B}) + (S_1 \cdot \overline{S_0} \cdot T_B)$$

$$S'_0 = ?$$

# FSM State Transition Table

 


Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = (\overline{S_1} \cdot S_0) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B}) + (S_1 \cdot \overline{S_0} \cdot T_B)$$

$$S'_0 = (\overline{S_1} \cdot \overline{S_0} \cdot \overline{T_A}) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B})$$

# FSM State Transition Table

 

Current State		Inputs		Next State	
S <sub>1</sub>	S <sub>0</sub>	T <sub>A</sub>	T <sub>B</sub>	S' <sub>1</sub>	S' <sub>0</sub>
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11


$$S'_1 = S_1 \text{ xor } S_0 \quad \textbf{(Simplified)}$$

$$S'_0 = (\overline{S}_1 \cdot \overline{S}_0 \cdot \overline{T}_A) + (S_1 \cdot \overline{S}_0 \cdot \overline{T}_B)$$

# Finite State Machines


## Output Table

# FSM Output Table

 

Current State		Outputs	
$S_1$	$S_0$	$L_A$	$L_B$
0	0	green	red
0	1	yellow	red
1	0	red	green
1	1	red	yellow


# FSM Output Table

 

Current State		Outputs	
$S_1$	$S_0$	$L_A$	$L_B$
0	0	green	red
0	1	yellow	red
1	0	red	green
1	1	red	yellow

Output	Encoding
green	00
yellow	01
red	10

# FSM Output Table

 


$$L_{A1} = S_1$$

Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

# FSM Output Table

 

$$L_{A1} = S_1$$


$$L_{A0} = \overline{S_1} \cdot S_0$$

Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10



# FSM Output Table

 


$$\begin{aligned}
 L_{A1} &= S_1 \\
 L_{A0} &= \overline{S_1} \cdot S_0 \\
 L_{B1} &= \overline{S_1}
 \end{aligned}$$

Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

# FSM Output Table

 

Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

$$\begin{aligned}
 L_{A1} &= S_1 \\
 L_{A0} &= \overline{S_1} \cdot S_0 \\
 L_{B1} &= \overline{S_1} \\
 L_{B0} &= S_1 \cdot S_0
 \end{aligned}$$


Output	Encoding
green	00
yellow	01
red	10

# Finite State Machines

## Schematic


# FSM Schematic: State Register

---

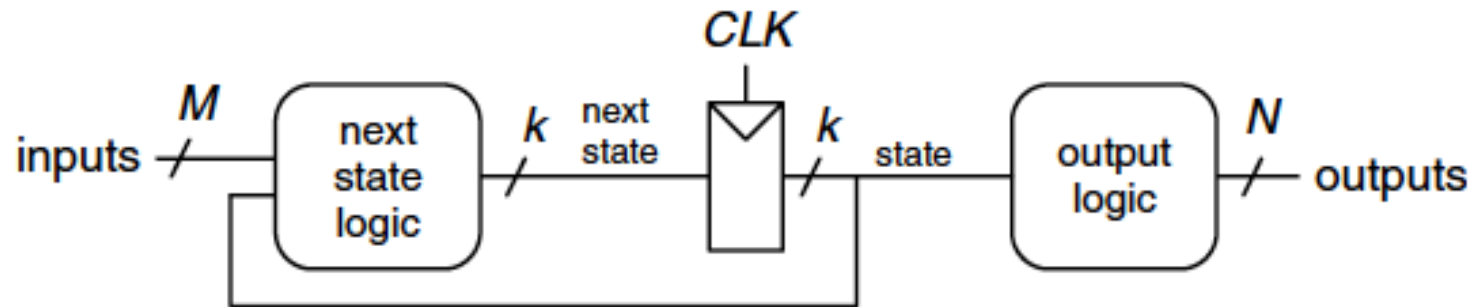


# FSM Schematic: State Register

---

 


# FSM Schematic: Next State Logic

 

$$S'_1 = S_1 \text{ xor } S_0$$


$$S'_0 = (\overline{S_1} \cdot \overline{S_0} \cdot \overline{T_A}) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B})$$

# FSM Schematic: Output Logic

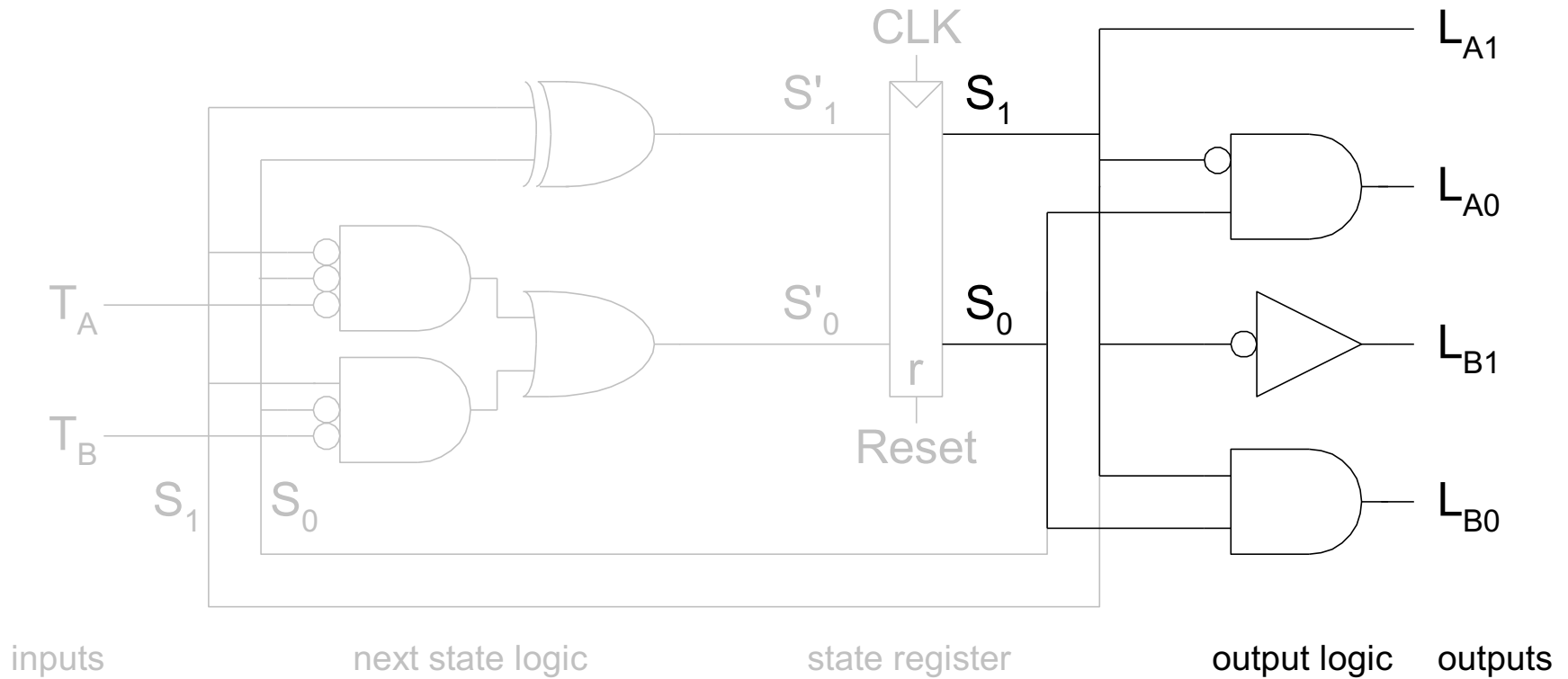

$$\begin{aligned}L_{A1} &= S_1 \\L_{A0} &= \overline{S_1} \cdot S_0 \\L_{B1} &= \overline{S_1} \\L_{B0} &= S_1 \cdot S_0\end{aligned}$$

# FSM Timing Diagram

 

CLK\_

Reset\_

$T_A$  \_

$T_B$  \_

S' \_



S \_

L<sub>A</sub>1:0 \_



L<sub>B</sub>1:0 \_





# FSM Timing Diagram

  



# FSM Timing Diagram

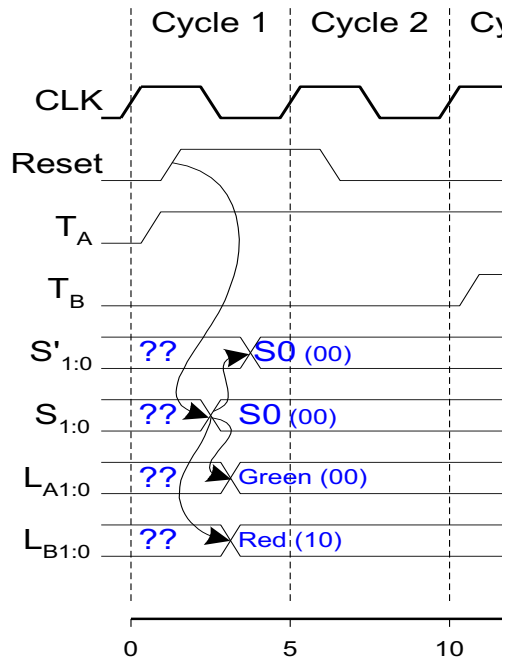 



# FSM Timing Diagram

  



# FSM Timing Diagram

  



# FSM Timing Diagram

  



# FSM Timing Diagram

  

# FSM Timing Diagram

 
 


# FSM Timing Diagram

  




# FSM Timing Diagram

  
 
# FSM State Encoding

---

- 3 common state binary encodings with different tradeoffs
  1. **Fully Encoded**
  2. **1-Hot Encoded**
  3. **Output Encoded**
- Let's see an example **Swiss** traffic light with 4 states
  - Green, Yellow, Red, Yellow+Red



# FSM State Encoding

---

## 1. Fully Encoded:

- ❑ **Minimizes** # flip-flops, but not necessarily output logic or next state logic
- ❑ Use  $\log_2(num\_states)$  bits to represent the states
- ❑ *Example states:* 00, 01, 10, 11

## 2. 1-Hot Encoded:

- ❑ **Maximizes** # flip-flops, **minimizes** next state logic
- ❑ Simplest design process – very automatable
- ❑ Use  $num\_states$  bits to represent the states
- ❑ *Example states:* 0001, 0010, 0100, 1000

# FSM State Encoding

---

## 3. Output Encoded:

- ❑ **Minimizes** output logic
- ❑ Only works for Moore Machines
- ❑ Each state has to be encoded **uniquely**, but the outputs must be **directly accessible** in the state encoding
- ❑ For example, since we have **3 outputs** (light color), encode state with **3 bits**, where each bit represents a color
- ❑ *Example states:* 001, 010, 100, 110
  - Bit<sub>0</sub> encodes **green** light output,
  - Bit<sub>1</sub> encodes **yellow** light output
  - Bit<sub>2</sub> encodes **red** light output

# FSM State Encoding

---

## 3. Output Encoded:

- ❑ **Minimizes** output logic
- ❑ Only works for Moore Machines
- ❑ Each state has to be encoded **uniquely**, but the outputs

The **designer** must **carefully** choose an encoding scheme to **optimize** the design under given constraints



- Bit<sub>1</sub> encodes **yellow** light output
- Bit<sub>2</sub> encodes **red** light output

# Moore vs. Mealy Machines

# Moore vs. Mealy FSM

- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it.
- The snail smiles whenever the last four digits it has crawled over are **1101**.
- Design Moore and Mealy FSMs of the snail's brain.


## Moore FSM

  



# Moore vs. Mealy FSM

- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it.
- The snail smiles whenever the last four digits it has crawled over are **1101**.
- Design Moore and Mealy FSMs of the snail's brain.

Moore FSM

 


Mealy FSM

  





# State Transition Diagrams

Moore FSM

 

What are the tradeoffs?

Mealy FSM

  

# FSM Design Procedure

---

- **Determine** all possible states of your machine
- **Develop** a **state transition diagram**
  - Generally this is done from a textual description
  - You need to 1) determine the **inputs** and **outputs** for each **state** and 2) figure out how to get from one state to another
- **Approach**
  - Start by defining the **reset state** and what happens from it – this is typically an easy point to start from
  - Then continue to add **transitions** and **states**
  - Picking **good state names** is very important
  - Building an FSM is **like** programming (but it *is not* programming!)
    - An FSM has a sequential “control-flow” like a program with conditionals and goto’s
    - The if-then-else construct is controlled by one or more inputs
    - The outputs are controlled by the state or the inputs
  - In hardware, we typically have many concurrent FSMs

# Implementing Sequential Logic Using Verilog

# Verilog: Last Week vs. This Week

---


- We have seen an overview of Verilog
- Discussed **structural** and **behavioral** modeling
- Showed **combinational logic** constructs

## **This week**

- **Sequential** logic constructs in Verilog
- **Developing testbenches** for simulation

# Combinational + Memory = Sequential

---

 

# Sequential Logic in Verilog

---

- Define blocks that have memory
  - *Flip-Flops, Latches, Finite State Machines*
- Sequential Logic state transition is triggered by a 'CLOCK' event
  - Latches are sensitive to level of the signal
  - Flip-flops are sensitive to the transitioning of clock
- Combinational constructs are **not** sufficient
  - We need **new constructs**:
    - **always**
    - **posedge/negedge**

# The “always” Block

---

```
always @ (sensitivity list)  
    statement;
```

Whenever the event in the **sensitivity list** occurs,  
the statement is **executed**

# Example: D Flip-Flop

---

```
module flop(input          clk,
            input    [3:0] d,
            output reg [3:0] q);

    always @ (posedge clk)
        q <- d;                // pronounced “q gets d”

endmodule
```

- **posedge** defines a rising edge (transition from 0 to 1).
- Statement executed when the **clk signal rises (posedge of clk)**
- Once the clk signal rises: the value of **d** is copied to **q**



# Example: D Flip-Flop

---

```
module flop(input          clk,
            input    [3:0] d,
            output reg [3:0] q);

    always @ (posedge clk)
        q <= d;                // pronounced “q gets d”

endmodule
```

- **assign** statement is **not** used within an always block
- **<=** describes a **non-blocking** assignment
  - We will see the difference between **blocking assignment** and **non-blocking** assignment soon

# Example: D Flip-Flop

---

```
module flop(input          clk,
            input          [3:0] d,
            output reg [3:0] q);

    always @ (posedge clk)
        q <= d;                // pronounced “q gets d”

endmodule
```

- Assigned variables need to be declared as **reg**
- The name **reg** does not necessarily mean that the value is a register (It could be, but it does not have to be)
- We will see examples later

# Asynchronous and Synchronous Reset

---

- **Reset** signals are used to **initialize** the hardware to a known state
  - Usually activated **at system start** (on power up)
- **Asynchronous Reset**
  - The reset signal is sampled **independent** of the clock
  - Reset gets the highest priority
  - Sensitive to **glitches**, may have **metastability** issues
    - Will be discussed in Lecture 8
- **Synchronous Reset**
  - The reset signal is sampled **with respect to the clock**
  - The reset **should be active long enough** to get sampled at the clock edge
  - Results in **completely synchronous circuit**

# D Flip-Flop with Asynchronous Reset

---

```
module flop_ar (input          clk,
                input          reset,
                input  [3:0] d,
                output reg [3:0] q);

  always @ (posedge clk, negedge reset)
  begin
    if (reset == 0) q <= 0;    // when reset
    else           q <= d;    // when clk
  end
endmodule
```

- In this example: two events can trigger the process:
  - A **rising edge** on clk
  - A **falling edge** on reset

# D Flip-Flop with Asynchronous Reset

---

```
module flop_ar (input          clk,
                input          reset,
                input  [3:0] d,
                output reg [3:0] q);

  always @ (posedge clk, negedge reset)
    begin
      if (reset == 0) q <= 0;    // when reset
      else           q <= d;    // when clk
    end
endmodule
```

- For longer statements, a **begin-end** pair can be used
  - ❑ To improve readability
  - ❑ In this example, it was not necessary, but it is a good idea

# D Flip-Flop with Asynchronous Reset

---

```
module flop_ar (input          clk,
                input          reset,
                input    [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk, negedge reset)
    begin
        if (reset == 0) q <= 0; // when reset
        else            q <= d;  // when clk
    end
endmodule
```

- First **reset** is checked: if **reset** is 0, **q** is set to 0.
  - This is an **asynchronous** reset as the reset can happen **independently** of the clock (on the negative edge of reset signal)
- If there is no reset, then regular assignment takes effect

# D Flip-Flop with Synchronous Reset

---

```
module flop_sr (input          clk,
                input          reset,
                input  [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk)
    begin
        if (reset == '0') q <= 0;    // when reset
        else               q <= d;    // when clk
    end
endmodule
```

- The process is only sensitive to clock
  - Reset **happens only** when the **clock rises**. This is a **synchronous** reset

# D Flip-Flop with Enable and Reset

---

```
module flop_en_ar (input          clk,
                  input          reset,
                  input          en,
                  input [3:0] d,
                  output reg [3:0] q);

    always @ (posedge clk, negedge reset)
    begin
        if (reset == '0') q <= 0;    // when reset
        else if (en)      q <= d;    // when en AND clk
    end
endmodule
```

- A flip-flop with **enable** and **reset**
  - Note that the **en** signal is **not** in the *sensitivity list*
- **q** gets **d** only when **clk** is rising **and** **en** is 1



# Example: D Latch

---

```
module latch (input          clk,
              input          [3:0] d,
              output reg [3:0] q);

    always @ (clk, d)
        if (clk) q <= d;           // latch is transparent when
                                   // clock is 1

endmodule
```

# Summary: Sequential Statements So Far

---

- Sequential statements are within an `always` block
- The sequential block is triggered with a change in the `sensitivity list`
- Signals assigned within an **`always`** must be declared as `reg`
- We use `<=` for (non-blocking) assignments and do not use `assign` within the `always` block.

# Basics of **always** Blocks

---

```
module example (input          clk,
                input    [3:0] d,
                output reg [3:0] q);

    wire [3:0] normal;           // standard wire
    reg  [3:0] special;          // assigned in always

    always @ (posedge clk)
        special <= d;            // first FF array

    assign normal = ~ special; // simple assignment

    always @ (posedge clk)
        q <= normal;             // second FF array
endmodule
```

You can have as many **always** blocks as needed

Assignment to the same signal in different always blocks is not allowed!

# Why Does an **always** Block Memorize?

---

```
module flop (input          clk,
              input    [3:0] d,
              output reg [3:0] q);

    always @ (posedge clk)
        begin
            q <= d;    // when clk rises copy d to q
        end
endmodule
```

- This statement describes what happens to signal **q**
- ... but what happens when the clock is not rising?
- The value of **q** is preserved (memorized)

# An **always** Block Does **NOT** Always Memorize

---

```
module comb (input          inv,
              input    [3:0] data,
              output reg [3:0] result);

  always @ (inv, data)      // trigger with inv, data
    if (inv) result <= ~data; // result is inverted data
    else   result <= data;   // result is data

endmodule
```

- This statement describes what happens to signal **result**
  - When **inv** is 1, **result** is **~data**
  - When **inv** is not 1, **result** is **data**
- The circuit is combinational (no memory)
  - **result** is assigned a value in all cases of the **if .. else** block, always

# always Blocks for Combinational Circuits

---

- An **always** block defines **combinational logic** if:
  - All outputs are always (**continuously**) updated
    1. All right-hand side signals are in the sensitivity list
      - You can use **always @\*** for short
    2. All left-hand side signals get assigned in every possible condition of **if .. else** and **case** blocks
- It is easy to make mistakes and **unintentionally describe memorizing elements** (latches)
  - **Vivado** will most likely warn you. Make sure you check the warning messages
- **Always** blocks allow powerful combinational logic statements
  - **if .. else**
  - **case**

# Sequential or Combinational?

---

```
wire enable, data;
reg out_a, out_b;

always @ (*) begin
    out_a = 1'b0;
    if(enable) begin
        out_a = data;
        out_b = data;
    end
end
```

*No assignment for ~enable*

**Sequential**

```
wire enable, data;
reg out_a, out_b;

always @ (data) begin
    out_a = 1'b0;
    out_b = 1'b0;
    if(enable) begin
        out_a = data;
        out_b = data;
    end
end
```

*Not in the sensitivity list*

**Sequential**

# The **always** Block is **NOT** Always Practical/Nice

---

```
reg [31:0] result;  
wire [31:0] a, b, comb;  
wire      sel,  
  
always @ (a, b, sel)    // trigger with a, b, sel  
    if (sel) result <= a; // result is a  
    else      result <= b; // result is b  
  
assign comb = sel ? a : b;
```

- Both statements describe the **same** multiplexer
- In this case, the **always** block is more work



# always Block for Case Statements (Handy!)

---

```
module sevensegment (input      [3:0] data,
                      output reg [6:0] segments);

  always @ ( * )                // * is short for all signals
  case (data)                    // case statement
    4'd0: segments = 7'b111_1110; // when data is 0
    4'd1: segments = 7'b011_0000; // when data is 1
    4'd2: segments = 7'b110_1101;
    4'd3: segments = 7'b111_1001;
    4'd4: segments = 7'b011_0011;
    4'd5: segments = 7'b101_1011;
    // etc etc
    default: segments = 7'b000_0000; // required
  endcase

endmodule
```

# Summary: `always` Block

---

- If `.. else` can only be used in `always` blocks
- The `always` block is `combinational` only if all `regs` within the block are always assigned to a signal
  - Use the `default` case to make sure you do not forget an unimplemented case, which may otherwise result in a latch
- Use `casex` statement to be able to check for don't cares

# Non-Blocking and Blocking Assignments

---

## Non-blocking (<=)

```
always @ (a)
begin
    a <= 2'b01;
    b <= a;
// all assignments are made here
// b is not (yet) 2'b01
end
```

- All assignments are made at the end of the block
- All assignments are made in parallel, process flow is **not-blocked**

## Blocking (=)

```
always @ (a)
begin
    a = 2'b01;
// a is 2'b01
    b = a;
// b is now 2'b01 as well
end
```

- Each assignment is made immediately
- Process waits until the first assignment is complete, it **blocks** progress

# Why use (Non)-Blocking Statements

---

- There are technical reasons why both are required
  - It is out of the scope of this course to discuss these
- Blocking statements allow sequential descriptions
  - More like a programming language
- If the sensitivity list is correct, blocks with non-blocking statements will always evaluate to the same result
  - This may require some additional iterations

# Example: Blocking Assignment

---

- Assume all inputs are initially '0'

```
always @ ( * )  
begin  
    p    = a ^ b ;           // p    = 0    1  
    g    = a & b ;           // g    = 0    0  
    s    = p ^ cin ;        // s    = 0    1  
    cout = g | (p & cin) ;   // cout = 0    0  
end
```

- If **a** changes to '1'
  - All values are updated in order

# The Same Example: Non-Blocking Assignment

---

- Assume all inputs are initially '0'

```
always @ ( * )
begin
    p    <= a ^ b ;           // p    = 0  1
    g    <= a & b ;           // g    = 0  0
    s    <= p ^ cin ;        // s    = 0  0
    cout <= g | (p & cin) ;  // cout = 0  0
end
```

- If **a** changes to '1'
  - All assignments are concurrent
  - When **s** is being assigned, **p** is still 0

# The Same Example: Non-Blocking Assignment

---

- After the first iteration, **p** has changed to '1' as well

```
always @ ( * )  
begin  
    p    <= a ^ b ;           // p    = 1    1  
    g    <= a & b ;           // g    = 0    0  
    s    <= p ^ cin ;        // s    = 0    1  
    cout <= g | (p & cin) ;   // cout = 0    0  
end
```

- Since there is a change in **p**, the process triggers again
- This time **s** is calculated with **p=1**

# Rules for Signal Assignment

---

- Use `always @(posedge clk)` and `non-blocking` assignments (`<=`) to model `synchronous sequential logic`

```
always @ (posedge clk)
    q <= d; // non-blocking
```

- Use continuous assignments (`assign`) to model simple combinational logic.


```
assign y = a & b;
```



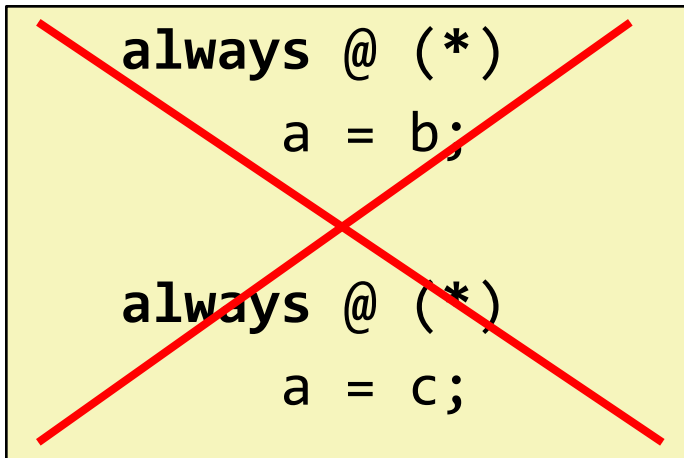
# Rules for Signal Assignment (Cont.)

---

- Use **always @ (\*)** and **blocking** assignments (=) to model more **complicated combinational logic**.
- You **cannot** make assignments to the **same** signal in more than one always block or in a *continuous assignment*



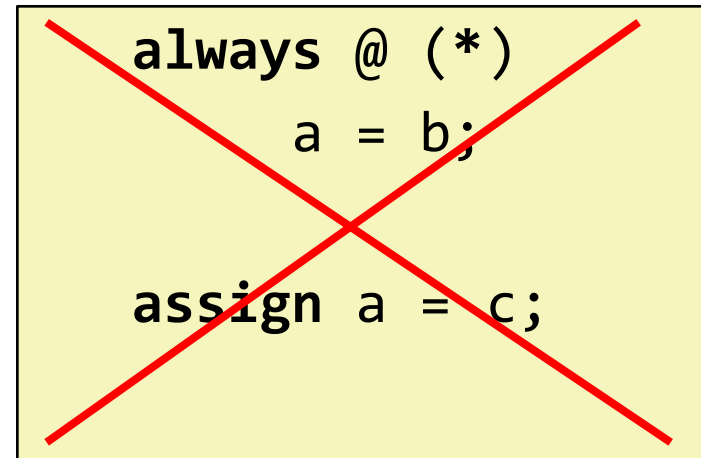~~**always @ (\*)**  
a = b;  
  
**always @ (\*)**  
a = c;~~




~~**always @ (\*)**  
a = b;  
  
**assign a = c;**~~
 
# Recall: Finite State Machines (FSMs)

---

- Each FSM consists of three separate parts:
  - next state logic
  - state register
  - output logic




# Recall: Finite State Machines (FSMs) Comprise

---


 
## ■ Sequential circuits

- State register(s)
  - Store the current state and
  - Load the next state at the clock edge



  
## ■ Combinational Circuits

- Next state logic
  - Determines what the next state will be
- Output logic
  - Generates the outputs




# FSM Example 1: Divide the Clock Frequency by 3

---

 

 The output *Y* is HIGH for **one clock cycle out of every 3**. In other words, the output **divides the frequency of the clock by 3**.



# Implementing FSM Example 1: Definitions

---


```
module divideby3FSM (input clk,
                    input reset,
                    output q);

    reg [1:0] state, nextstate;

    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b10;
```

- We define `state` and `nextstate` as 2-bit reg
- The parameter descriptions are `optional`, it makes reading easier


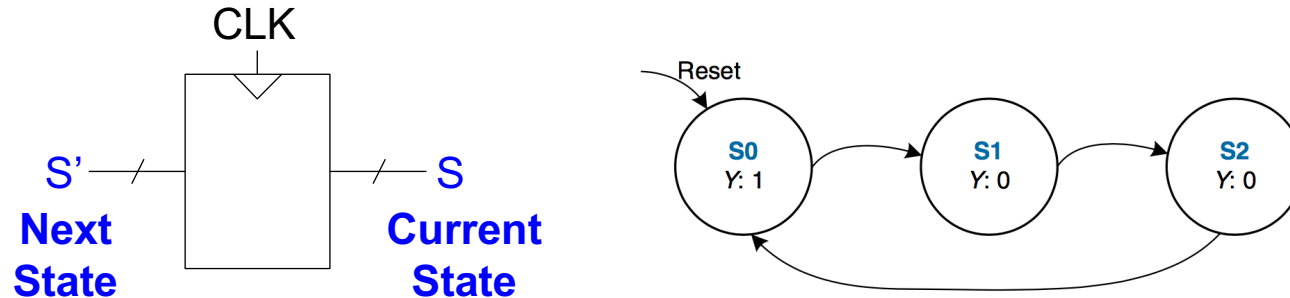
# Implementing FSM Example 1: State Register



```
// state register
always @ (posedge clk, posedge reset)
  if (reset) state <= S0;
  else      state <= nextstate;
```



- This part defines the **state register** (memorizing process)
- Sensitive to only **clk**, **reset**
- In this example, **reset** is active when it is '1' (active-high)
  
# Implementing FSM Example 1: Next State Logic



```
// next state logic
always @ (*)
  case (state)
    S0:      nextstate = S1;
    S1:      nextstate = S2;
    S2:      nextstate = S0;
    default: nextstate = S0;
  endcase
```
 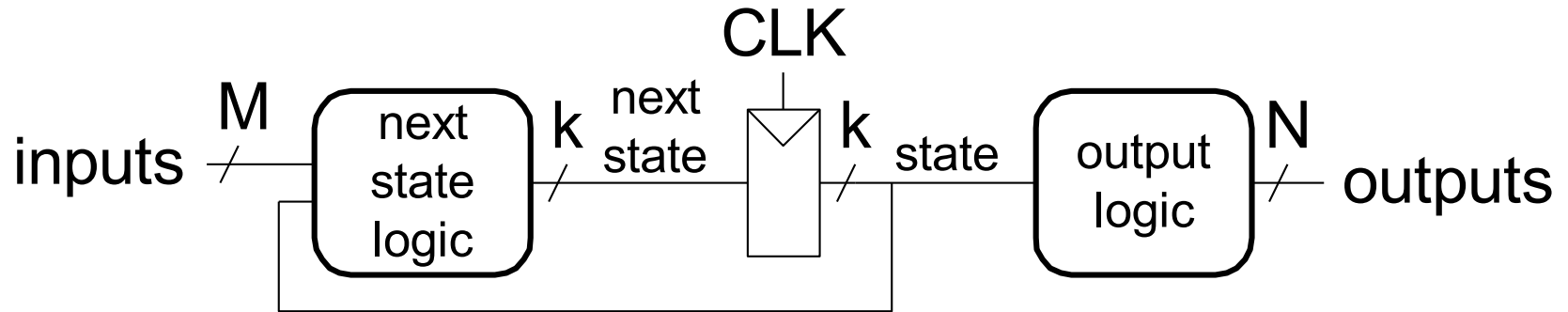
# Implementing FSM Example 1: Output Logic



```
// output logic  
assign q = (state == S0);
```

- In this example, output depends only on state
  - **Moore type FSM**



# Implementation of FSM Example 1

---

```
module divideby3FSM (input clk, input reset, output q);
    reg [1:0] state, nextstate;

    parameter S0 = 2'b00; parameter S1 = 2'b01; parameter S2 = 2'b10;


    always @ (posedge clk, posedge reset) // state register
        if (reset) state <= S0;
        else      state <= nextstate;

    always @ (*) // next state logic
        case (state)
            S0:      nextstate = S1;
            S1:      nextstate = S2;
            S2:      nextstate = S0;
            default: nextstate = S0;
        endcase


    assign q = (state == S0); // output logic
endmodule
```
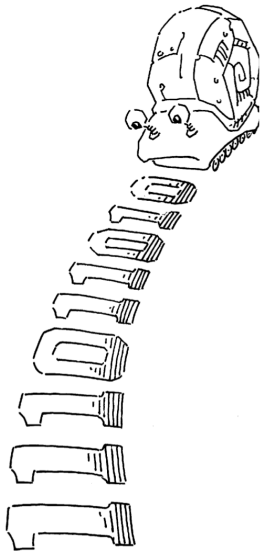
# FSM Example 2: Smiling Snail


- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it.
- The snail smiles whenever the last four digits it has crawled over are **1101**.
- Design Moore and Mealy FSMs of the snail's brain.



**Moore**

 

**Mealy**

 

We did not cover the following.  
They are for your preparation.

# Implementing FSM Example 2: Definitions

```
module SmilingSnail (input clk,  
                    input reset,  
                    input number,  
                    output smile);
```


```
    reg [1:0] state, nextstate;
```

```
    parameter S0 = 2'b00;
```

```
    parameter S1 = 2'b01;
```

```
    parameter S2 = 2'b10;
```

```
    parameter S3 = 2'b11;
```

 

# Implementing FSM Example 2: State Register


---

```
// state register
always @ (posedge clk, posedge reset)
    if (reset) state <= S0;
    else      state <= nextstate;
```

- This part defines the **state register** (memorizing process)
- Sensitive to only **clk**, **reset**
- In this example **reset** is active when '1' (active-high)
 
# Implementing FSM Example 2: Next State Logic

```
// next state logic
always @ (*)
  case (state)
    S0: if (number) nextstate = S1;
        else nextstate = S0;
    S1: if (number) nextstate = S2;
        else nextstate = S0;
    S2: if (number) nextstate = S2;
        else nextstate = S3;
    S3: if (number) nextstate = S1;
        else nextstate = S0;
    default: nextstate = S0;
  endcase
```



# Implementing FSM Example 2: Output Logic

---

```
// output logic
assign smile = (number & state == S3);
```

- In this example, output depends on state and input
  - **Mealy type FSM**
- We used a simple combinational assignment

# Implementation of FSM Example 2

```
module SmilingSnail (input clk,
                    input reset,
                    input number,
                    output smile);

    reg [1:0] state, nextstate;

    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b10;
    parameter S3 = 2'b11;

    // state register
    always @ (posedge clk, posedge
reset)
        if (reset) state <= S0;
        else      state <= nextstate;
```

```
    always @ (*) // next state logic
        case (state)
            S0: if (number)
                    nextstate = S1;
                else nextstate = S0;
            S1: if (number)
                    nextstate = S2;
                else nextstate = S0;
            S2: if (number)
                    nextstate = S2;
                else nextstate = S3;
            S3: if (number)
                    nextstate = S1;
                else nextstate = S0;
            default: nextstate = S0;
        endcase
    // output logic
    assign smile = (number & state==S3);

endmodule
```



# What Did We Learn?

---

- Basics of defining **sequential circuits** in Verilog
- The **always** statement
  - Needed for defining memorizing elements (**flip-flops, latches**)
  - Can also be used to define **combinational circuits**
- **Blocking** vs **Non-blocking** statements
  - **=** assigns the value **immediately**
  - **<=** assigns the value **at the end of the block**
- Writing FSMs
  - Next state logic
  - State assignment
  - Output logic

# Next Lecture: Timing and Verification

# Design of Digital Circuits

## Lecture 7: Sequential Logic Design

Prof. Onur Mutlu

ETH Zurich

Spring 2018

15 March 2018

# Backup Slides

---

- Different types of flip flops

# The D Flip-Flop

# Enabled Flip-Flops


---

- **Inputs:** CLK, D, EN

- The enable input (EN) controls when new data (D) is stored

- **Function:**

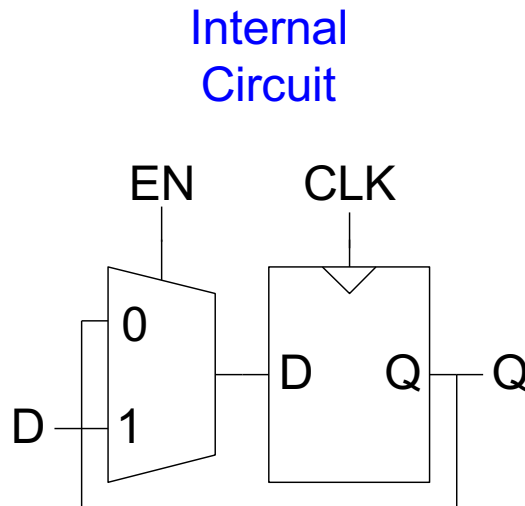- **EN = 1:** D passes through to Q on the clock edge
  - **EN = 0:** the flip-flop retains its previous state





# Resettable Flip-Flop

---

- **Inputs:** CLK, D, Reset
  - The Reset is used to set the output to 0.
- **Function:**
  - **Reset = 1:** Q is forced to 0
  - **Reset = 0:** the flip-flop behaves like an ordinary D flip-flop


## Symbols

  
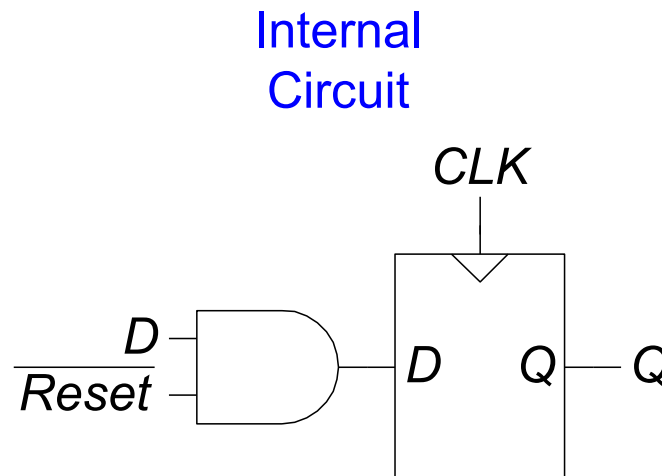
# Resettable Flip-Flops

---

- Two types:
  - **Synchronous:** resets at the clock edge only
  - **Asynchronous:** resets immediately when Reset = 1
- Asynchronously resettable flip-flop requires changing the internal circuitry of the flip-flop (see Exercise 3.10)
- Synchronously resettable flip-flop?





# Settable Flip-Flop

---

- **Inputs:** CLK, D, Set
- **Function:**
  - **Set = 1:** Q is set to 1
  - **Set = 0:** the flip-flop behaves like an ordinary D flip-flop

## Symbols

