

# Design of Digital Circuits

## Lecture 13: Microprogramming

Prof. Onur Mutlu

ETH Zurich

Spring 2018

13 April 2018

# Readings

---

## ■ This week

- Multi-cycle microarchitecture
  - P&P, Appendices A and C
  - H&H, Chapter 7.4
- Microprogramming
  - P&P, Appendices A and C

## ■ Next week

- Pipelining
  - H&H, Chapter 7.5
- Pipelining Issues
  - H&H, Chapter 7.8.1-7.8.3

# Agenda for Today & Next Few Lectures

---

- Instruction Set Architectures (ISA): LC-3 and MIPS
- Assembly programming: LC-3 and MIPS
- Microarchitecture (principles & single-cycle uarch)
- Multi-cycle microarchitecture
- Microprogramming
- Pipelining
- Issues in Pipelining: Control & Data Dependence Handling, State Maintenance and Recovery, ...
- Out-of-Order Execution

# Recall: Performance Analysis Basics

---

- Execution time of an instruction
  - $\{\text{CPI}\} \times \{\text{clock cycle time}\}$ 
    - CPI: Number of cycles it takes to execute an instruction
- Execution time of a program
  - Sum over all instructions  $[\{\text{CPI}\} \times \{\text{clock cycle time}\}]$
  - **$\{\# \text{ of instructions}\} \times \{\text{Average CPI}\} \times \{\text{clock cycle time}\}$**



# Recall: (Micro)architecture Design Principles

---

## ■ Critical path design

- Find and **decrease the maximum combinational logic delay**
- Break a path into multiple cycles if it takes too long

## ■ Bread and butter (common case) design

- **Spend time and resources on where it matters most**
  - i.e., improve what the machine is really designed to do
- Common case vs. uncommon case


## ■ Balanced design

- **Balance** instruction/data flow through hardware components
- **Design to eliminate bottlenecks:** balance the hardware for the work

 
# Recall: Multi-Cycle Microarchitecture

---


AS = Architectural (programmer visible) state  
at the beginning of an instruction



 
Step 1: Process part of instruction in one clock cycle



 Step 2: Process part of instruction in the next clock cycle



...

 


AS' = Architectural (programmer visible) state  
at the end of a clock cycle

# Recall: A Basic Multi-Cycle Microarchitecture

---


- Instruction processing cycle divided into “states”
  - A stage in the instruction processing cycle can take multiple states
- A multi-cycle microarchitecture sequences from state to state to process an instruction
  - The behavior of the machine in a state is completely determined by control signals in that state
- The behavior of the entire processor is specified fully by a *finite state machine*
- In a state (clock cycle), control signals control two things:
  - How the datapath should process the data
  - How to generate the control signals for the (next) clock cycle

# Recall: Multi-Cycle MIPS FSM

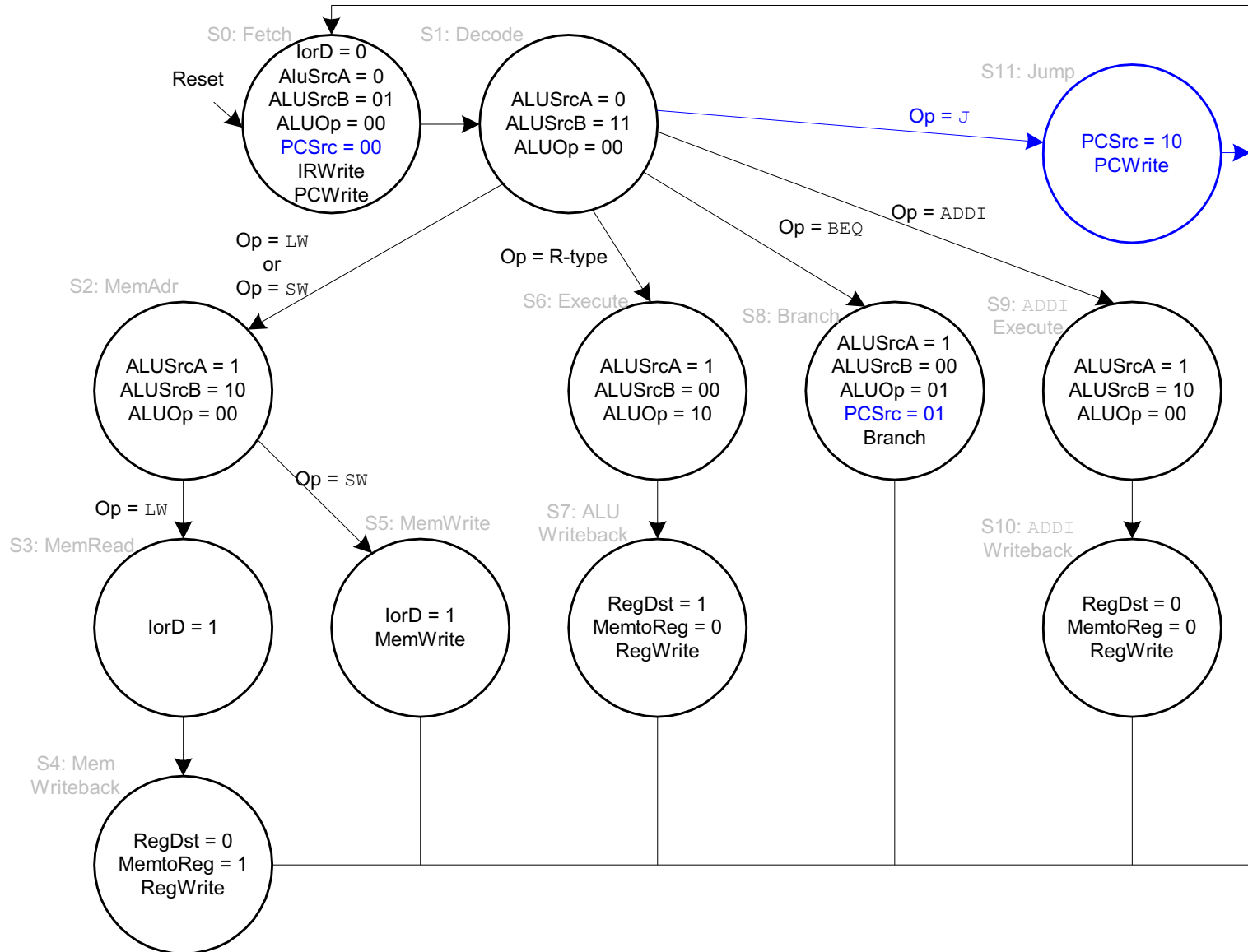
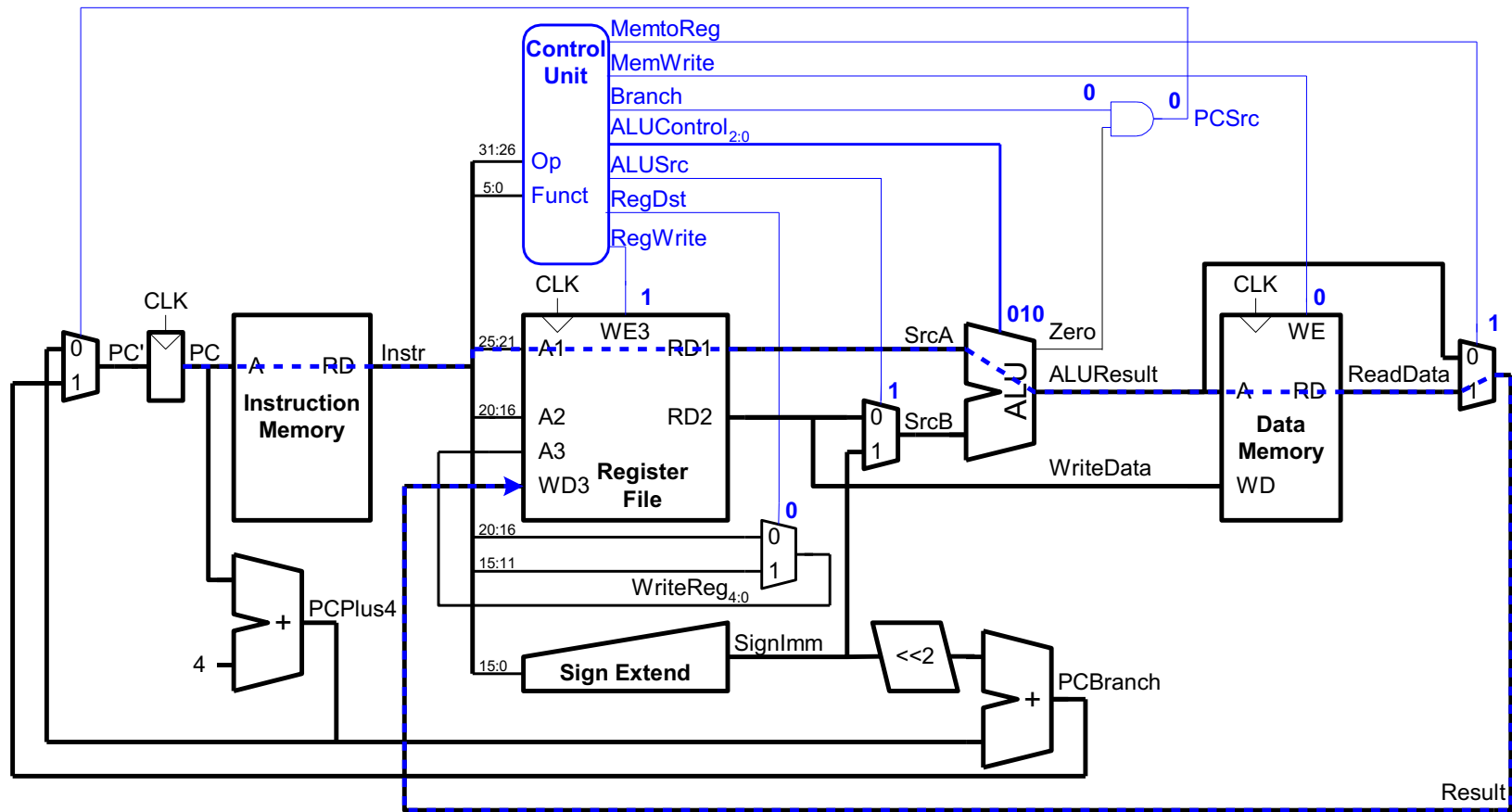
# Single-Cycle Performance

- $T_C$  is limited by the critical path (1w)



# Single-Cycle Performance


- Single-cycle critical path:

- $$T_c = t_{pcq\_PC} + t_{mem} + \max(t_{RRead}, t_{sext} + t_{mux}) + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- In most implementations, limiting paths are:

- memory, ALU, register file.

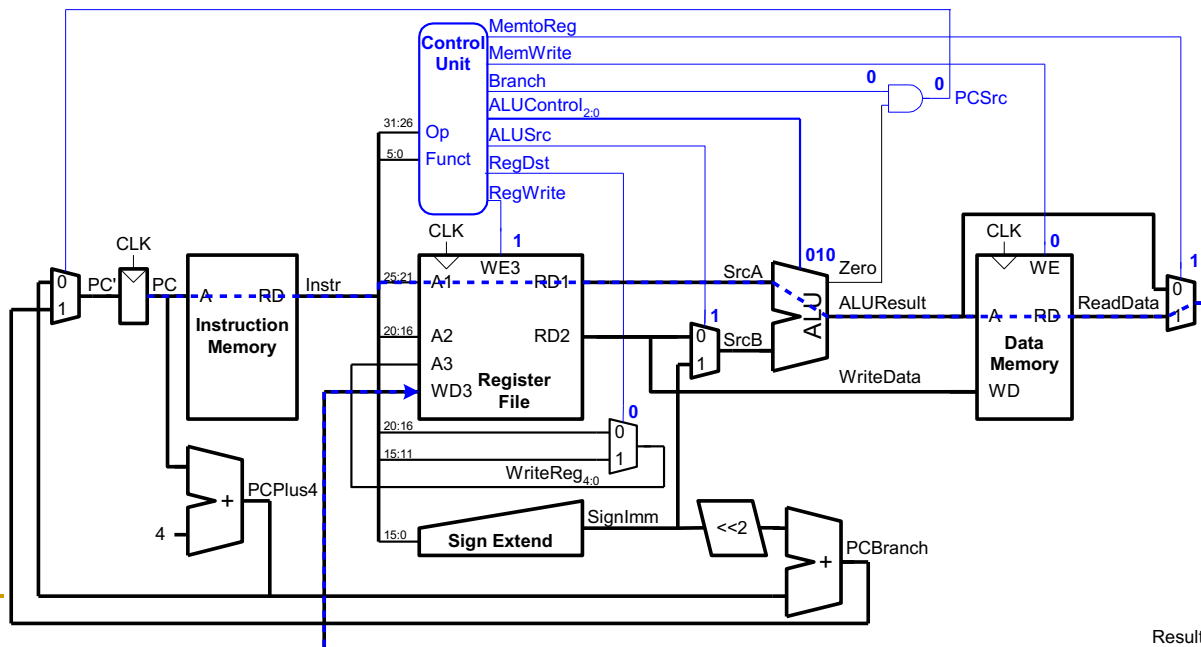- $$T_c = t_{pcq\_PC} + 2t_{mem} + t_{RRead} + t_{mux} + t_{ALU} + t_{RFsetup}$$



# Single-Cycle Performance Example

---

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	30
Register setup	$t_{setup}$	20
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	200
Memory read	$t_{mem}$	250
Register file read	$t_{RFread}$	150
Register file setup	$t_{RFsetup}$	20

$$T_c =$$

# Single-Cycle Performance Example

---

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	30
Register setup	$t_{setup}$	20
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	200
Memory read	$t_{mem}$	250
Register file read	$t_{RFread}$	150
Register file setup	$t_{RFsetup}$	20

$$\begin{aligned}T_c &= t_{pcq\_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup} \\&= [30 + 2(250) + 150 + 25 + 200 + 20] \text{ ps} \\&= 925 \text{ ps}\end{aligned}$$



# Single-Cycle Performance Example

---

- Example:

For a program with 100 billion instructions executing on a single-cycle MIPS processor:

# Single-Cycle Performance Example

---

## ■ Example:

For a program with 100 billion instructions executing on a single-cycle MIPS processor:

$$\begin{aligned}\textbf{Execution Time} &= \# \text{ instructions} \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(1)(925 \times 10^{-12} \text{ s}) \\ &= 92.5 \text{ seconds}\end{aligned}$$

# Multi-Cycle Performance: CPI


---

- Instructions take different number of cycles:
  - ❑ 3 cycles: beq, j
  - ❑ 4 cycles: R-Type, sw, addi
  - ❑ 5 cycles: lw **Realistic?**
- CPI is weighted average, e.g. SPECINT2000 benchmark:
  - ❑ 25% loads
  - ❑ 10% stores
  - ❑ 11% branches
  - ❑ 2% jumps
  - ❑ 52% R-type
- *Average CPI* =  $(0.11 + 0.02) 3 + (0.52 + 0.10) 4 + (0.25) 5$   
= 4.12

# Multi-cycle Performance: Cycle Time

## ■ Multi-cycle critical path:


$$T_c =$$

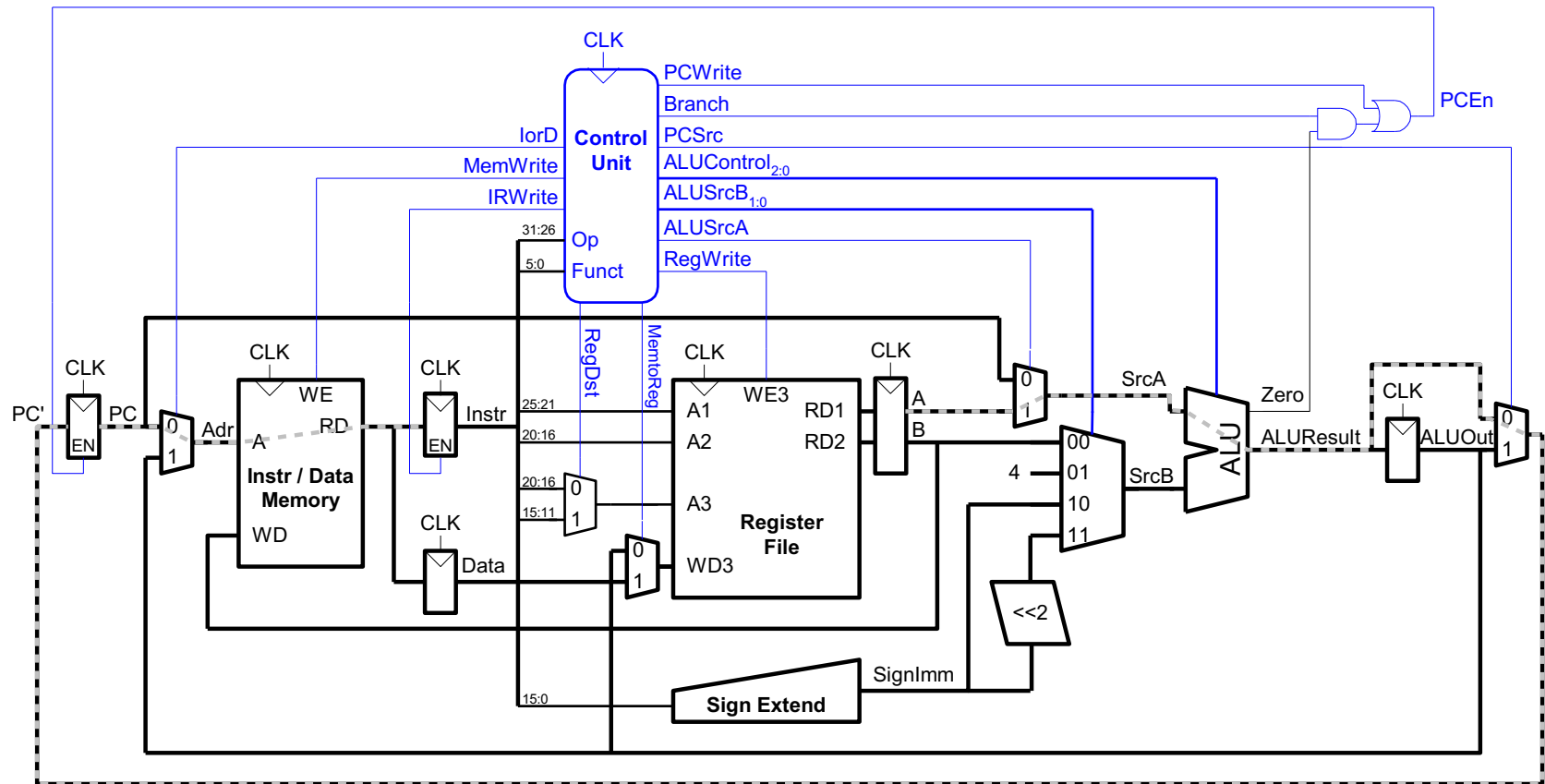
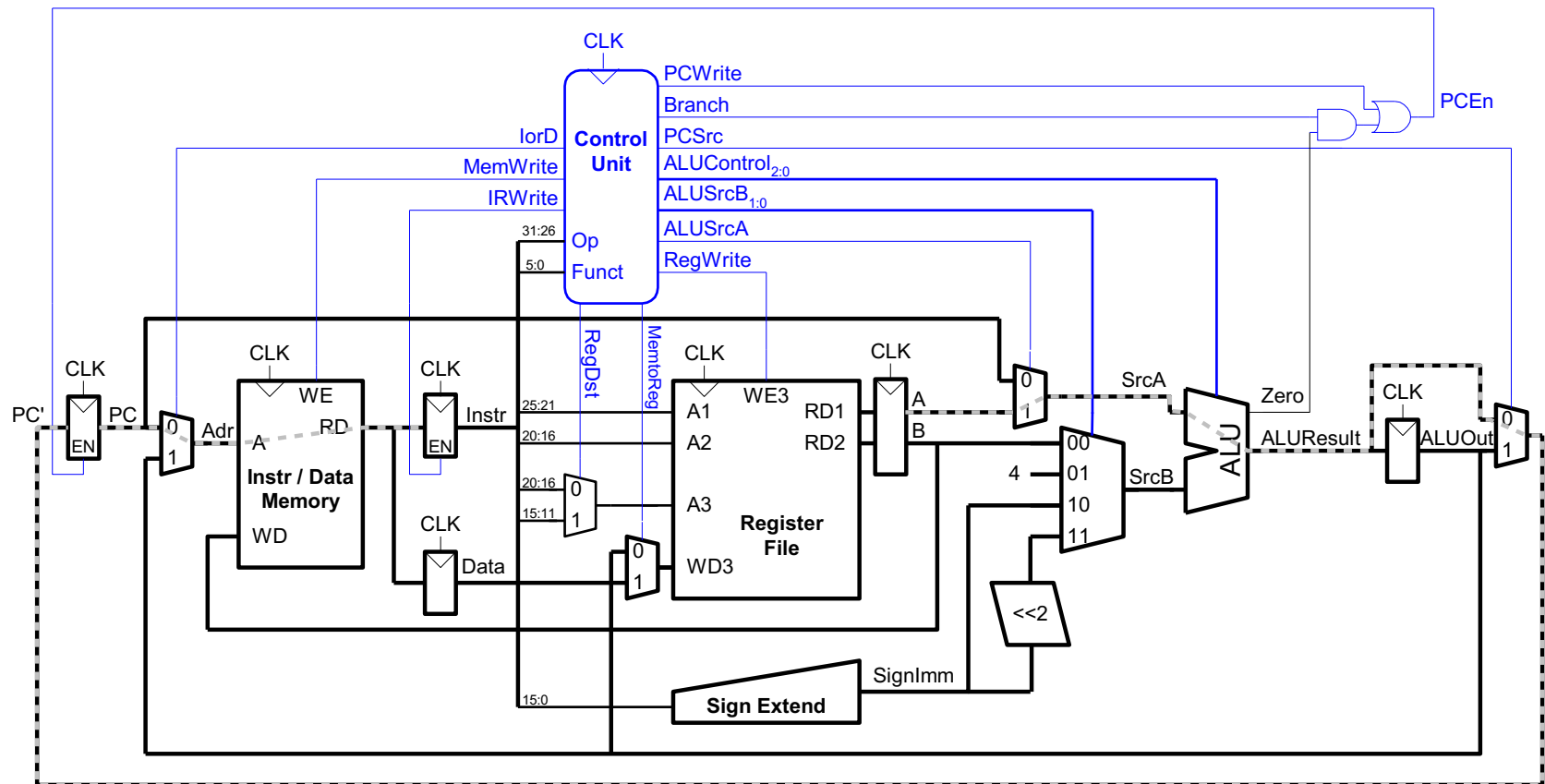
# Multi-cycle Performance: Cycle Time

- Multi-cycle critical path:

$$T_c = t_{pcq} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup}$$



# Multi-Cycle Performance Example

---

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	30
Register setup	$t_{setup}$	20
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	200
Memory read	$t_{mem}$	250
Register file read	$t_{RFread}$	150
Register file setup	$t_{RFsetup}$	20

$T_c$  =

# Multi-Cycle Performance Example

---

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	30
Register setup	$t_{setup}$	20
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	200
Memory read	$t_{mem}$	250
Register file read	$t_{RFread}$	150
Register file setup	$t_{RFsetup}$	20

$$\begin{aligned}T_c &= t_{pcq\_PC} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup} \\&= [30 + 25 + 250 + 20] \text{ ps} \\&= 325 \text{ ps}\end{aligned}$$


# Multi-Cycle Performance Example

---


- For a program with 100 billion instructions executing on a multi-cycle MIPS processor
  - $CPI = 4.12$
  - $T_c = 325 \text{ ps}$
- *Execution Time*  $= (\# \text{ instructions}) \times CPI \times T_c$   
 $= (100 \times 10^9)(4.12)(325 \times 10^{-12})$   
 $= 133.9 \text{ seconds}$
- This is slower than the single-cycle processor (92.5 seconds). Why?
- Did we break the stages in a balanced manner?
- Overhead of register setup/hold paid many times
- How would the results change with different assumptions on memory latency and instruction mix?




# Review: Single-Cycle MIPS Processor

 

# Review: Multi-Cycle MIPS Processor

 

# Review: Multi-Cycle MIPS FSM

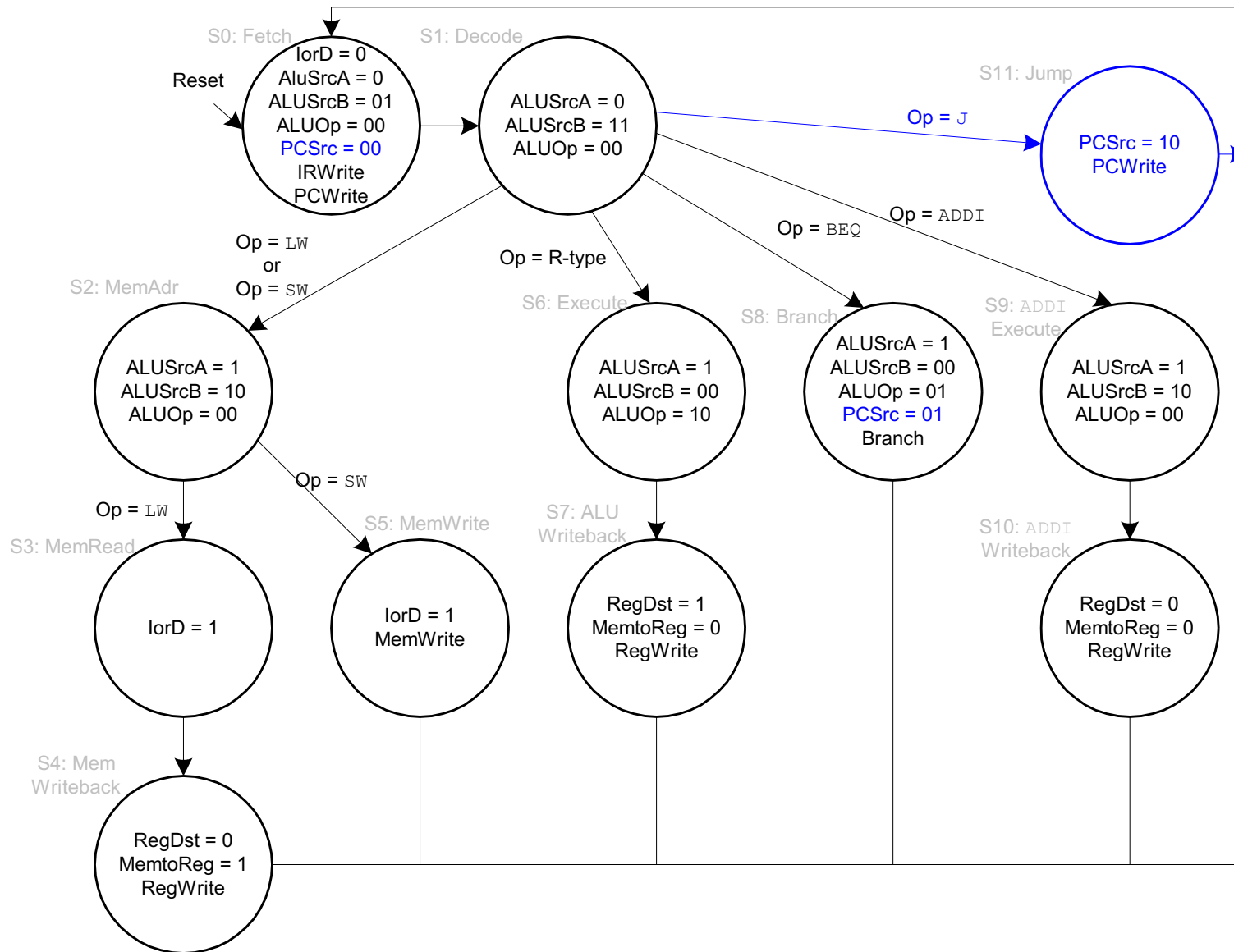

**What is the  
shortcoming of  
this design?**

**What does  
this design  
assume  
about memory?**

# What If Memory Takes $>$ One Cycle?

---

- Stay in the same “memory access” state until memory returns the data
- “Memory Ready?” bit is an input to the control logic that determines the next state

Another Example:

**Microprogrammed Multi-Cycle  
Microarchitecture**

# How Do We Implement This?

---

- Maurice Wilkes, “[The Best Way to Design an Automatic Calculating Machine](#),” Manchester Univ. Computer Inaugural Conf., 1951.

## THE BEST WAY TO DESIGN AN AUTOMATIC CALCULATING MACHINE

By M. V. Wilkes, M.A., Ph.D., F.R.A.S.



- An elegant implementation:
  - [The concept of microcoded/microprogrammed machines](#)

# Recall: A Basic Multi-Cycle Microarchitecture

---

- Instruction processing cycle divided into “states”
  - A stage in the instruction processing cycle can take multiple states
- A multi-cycle microarchitecture sequences from state to state to process an instruction
  - The behavior of the machine in a state is completely determined by control signals in that state
- The behavior of the entire processor is specified fully by a *finite state machine*
- In a state (clock cycle), control signals control two things:
  - How the datapath should process the data
  - How to generate the control signals for the (next) clock cycle

# Microprogrammed Control Terminology


---

- Control signals associated with the current state
  - Microinstruction
- Act of transitioning from one state to another
  - Determining the next state and the microinstruction for the next state
  - Microsequencing
- Control store stores control signals for every possible state
  - Store for microinstructions for the entire FSM
- Microsequencer determines which set of control signals will be used in the next clock cycle (i.e., next state)



# Example Control Structure

Simple Design  
of the Control Structure

 


# What Happens In A Clock Cycle?

---

- The control signals (microinstruction) for the current state control two things:
  - ❑ Processing in the data path
  - ❑ Generation of control signals (microinstruction) for the next cycle
  - ❑ *See Supplemental Figure 1 (next-next slide)*
- Datapath and microsequencer operate concurrently
- Question: why not generate control signals for the current cycle in the current cycle?
  - ❑ This could lengthen the clock cycle
  - ❑ Why could it lengthen the clock cycle?
  - ❑ *See Supplemental Figure 2*
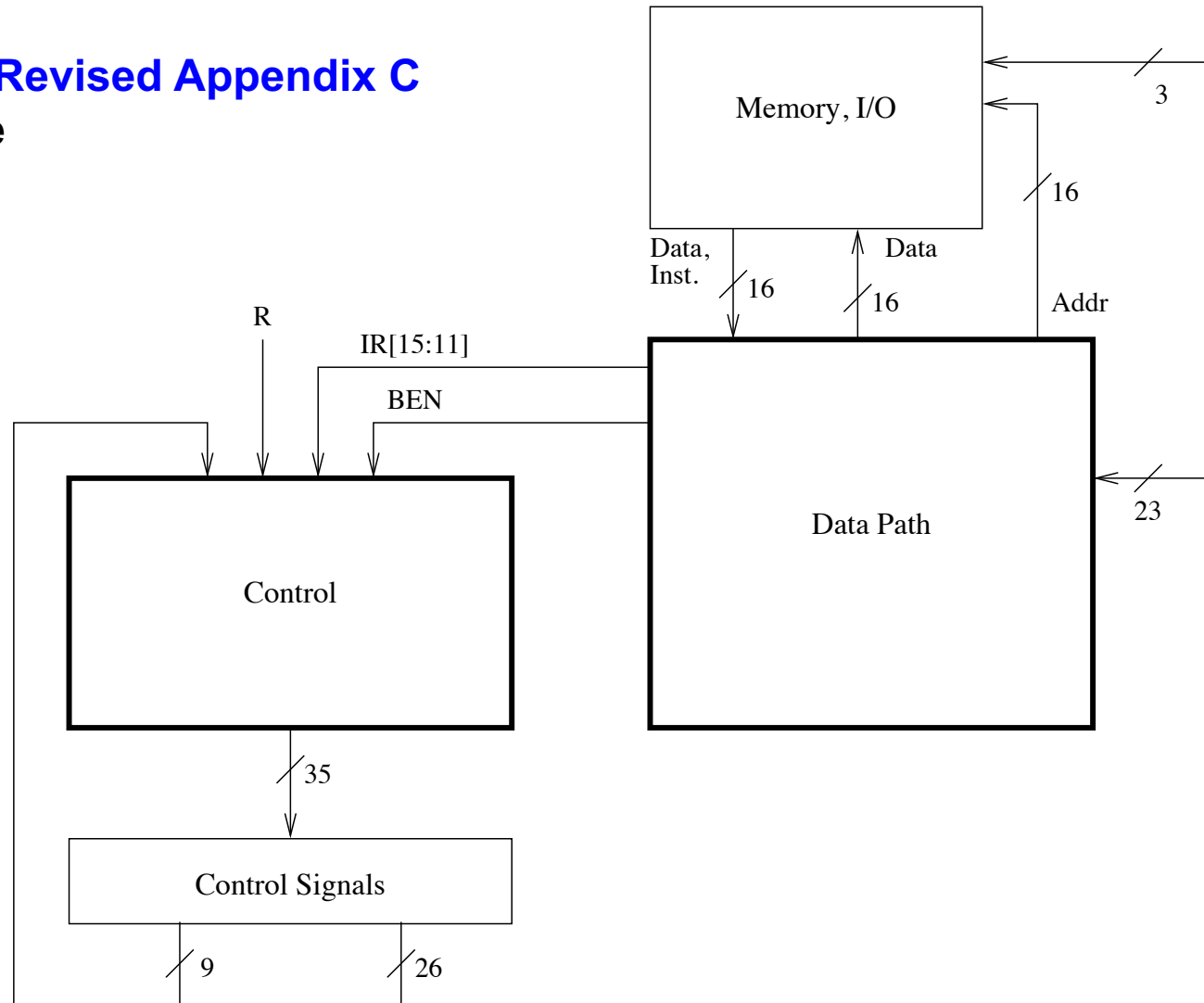
# Example uProgrammed Control & Datapath


**Read P&P Revised Appendix C**  
**On website**



(J, COND, IRD)


Microarchitecture of the LC-3b, major components

# A Clock Cycle

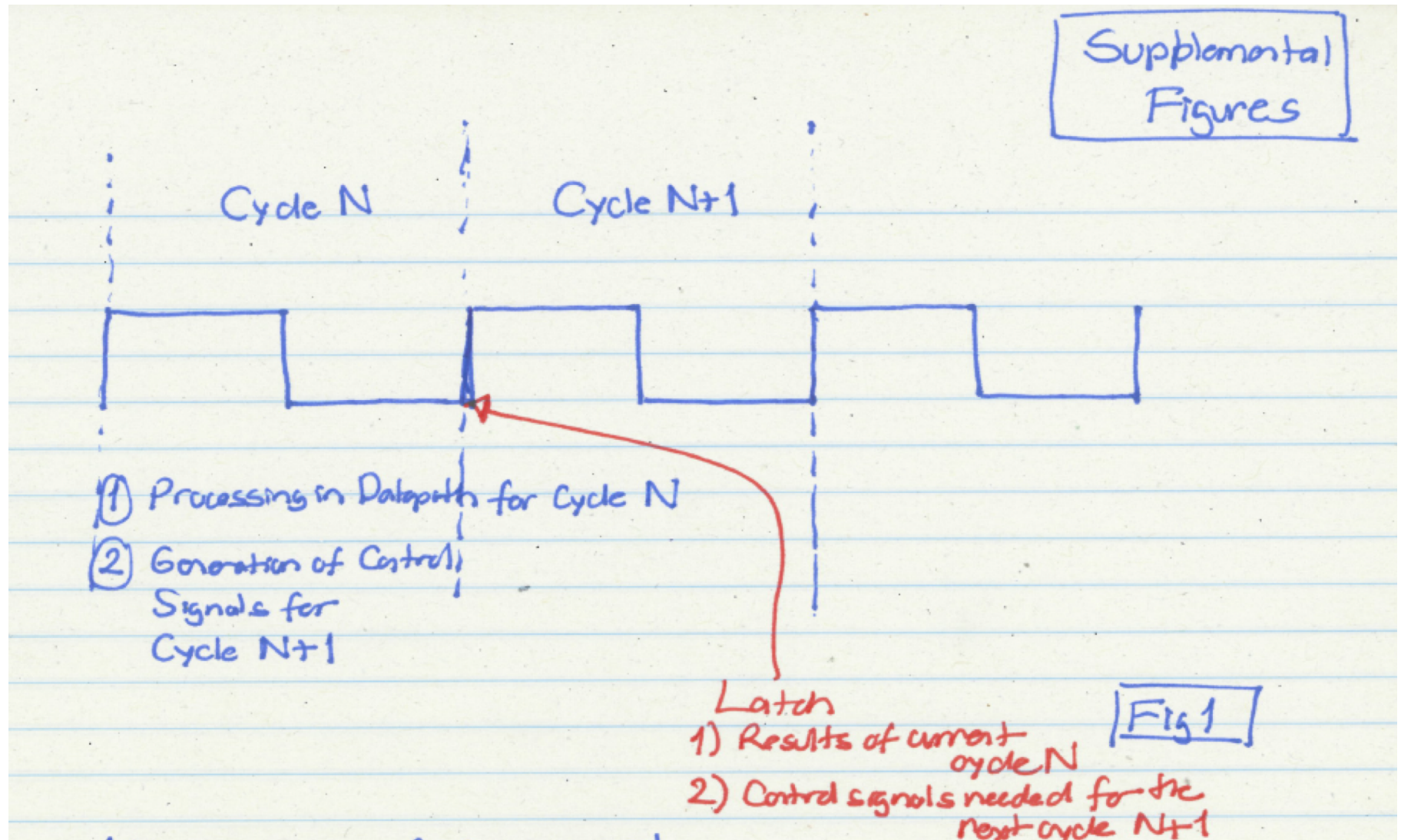

# A Bad Clock Cycle!

Alternative - A BAD ONE!

 

Step ① is dependent on Step ①


If Step ① takes non-zero time (it does!), clock cycle increases unnecessarily

→ Violates the "Critical Path Design" principle

Fig 2
 
# A Simple LC-3b Control and Datapath

**Read P&P Revised Appendix C**  
**On website**



Microarchitecture of the LC-3b, major components




# What Determines Next-State Control Signals?

---

- What is happening in the current clock cycle
  - See the 9 control signals coming from “Control” block
    - What are these for?
- The instruction that is being executed
  - IR[15:11] coming from the Data Path
- Whether the condition of a branch is met, if the instruction being processed is a branch
  - BEN bit coming from the datapath
- Whether the memory operation is completing in the current cycle, if one is in progress
  - R bit coming from memory

# A Simple LC-3b Control and Datapath

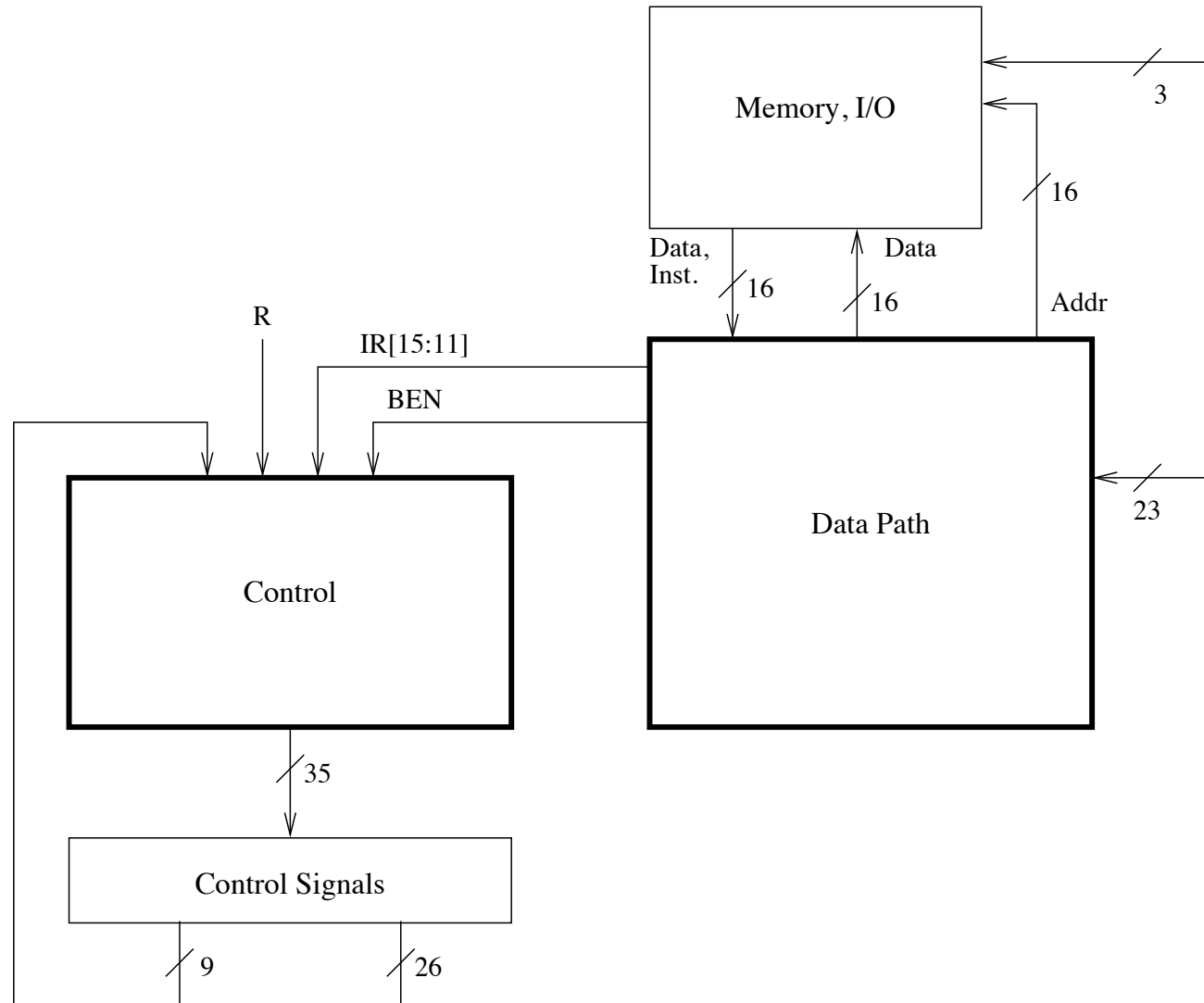

(J, COND, IRD)

Microarchitecture of the LC-3b, major components



# The State Machine for Multi-Cycle Processing


---

- The behavior of the LC-3b uarch is completely determined by
  - the 35 control signals and
  - additional 7 bits that go into the control logic from the datapath
- 35 control signals completely describe the state of the control structure
- We can completely describe the behavior of the LC-3b as a state machine, i.e. a directed graph of
  - Nodes (one corresponding to each state)
  - Arcs (showing flow from each state to the next state(s))
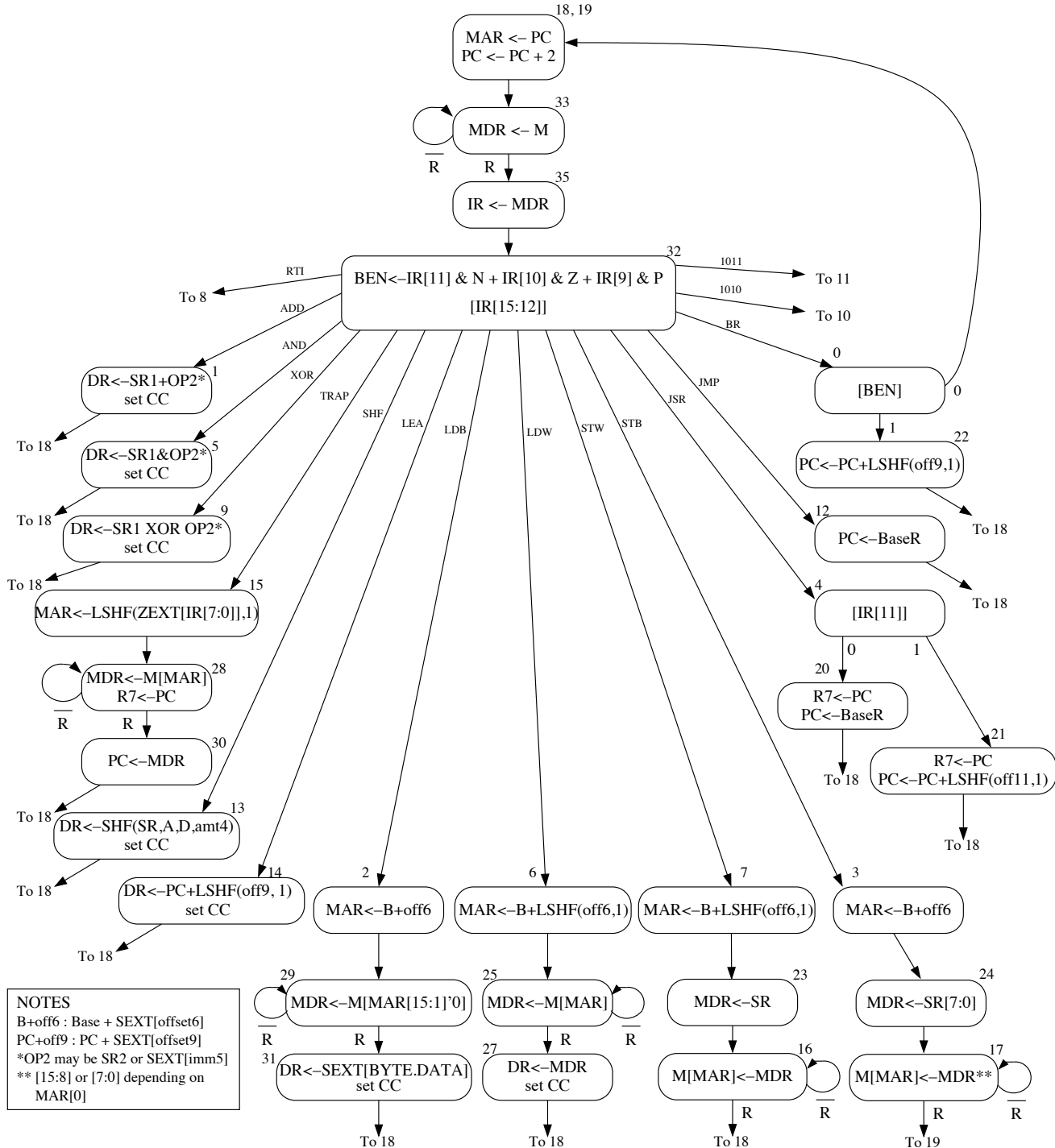
# An LC-3b State Machine

---

- Patt and Patel, [Revised Appendix C, Figure C.2](#)
- Each state must be uniquely specified
  - Done by means of *state variables*
- 31 distinct states in this LC-3b state machine
  - Encoded with 6 state variables
- Examples
  - State 18,19 correspond to the beginning of the instruction processing cycle
  - Fetch phase: state 18, 19 → state 33 → state 35
  - Decode phase: state 32



# The FSM Implements the LC-3b ISA

	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
ADD <sup>+</sup>	0001				DR			SR1			A	op.spec				
AND <sup>+</sup>	0101				DR			SR1			A	op.spec				
BR	0000				n	z	p	PCOffset9								
JMP	1100				000			BaseR			000000					
JSR(R)	0100				A	operand.specifier										
LDB <sup>+</sup>	0010				DR			BaseR			boffset6					
LDW <sup>+</sup>	0110				DR			BaseR			offset6					
LEA <sup>+</sup>	1110				DR			PCOffset9								
RTI	1000				000000000000											
SHF <sup>+</sup>	1101				DR			SR			A	D	amount4			
STB	0011				SR			BaseR			boffset6					
STW	0111				SR			BaseR			offset6					
TRAP	1111				0000			trapvect8								
XOR <sup>+</sup>	1001				DR			SR1			A	op.spec				
not used	1010															
not used	1011															

## ■ P&P Appendix A (revised):

- <https://safari.ethz.ch/digitaltechnik/spring2018/lib/exe/fetch.php?media=pp-appendixa.pdf>

# LC-3b State Machine: Some Questions

---


- How many cycles does the fastest instruction take?
- How many cycles does the slowest instruction take?
- Why does the BR take as long as it takes in the FSM?
- What determines the clock cycle time?
 
# LC-3b Datapath


---

- Patt and Patel, [Revised Appendix C, Figure C.3](#)
- Single-bus datapath design
  - At any point only one value can be “gated” on the bus (i.e., can be driving the bus)
  - **Advantage**: Low hardware cost: one bus
  - **Disadvantage**: Reduced concurrency – if instruction needs the bus twice for two different things, these need to happen in different states
- Control signals (26 of them) determine what happens in the datapath in one clock cycle
  - Patt and Patel, [Revised Appendix C, Table C.1](#)






(a)

 

(b)

Remember the MIPS datapath

 

(c)



Signal Name	Signal Values	
LD.MAR/1:	NO, LOAD	
LD.MDR/1:	NO, LOAD	
LD.IR/1:	NO, LOAD	
LD.BEN/1:	NO, LOAD	
LD.REG/1:	NO, LOAD	
LD.CC/1:	NO, LOAD	
LD.PC/1:	NO, LOAD	
GatePC/1:	NO, YES	
GateMDR/1:	NO, YES	
GateALU/1:	NO, YES	
GateMARMUX/1:	NO, YES	
GateSHF/1:	NO, YES	
PCMUX/2:	PC+2 BUS ADDER	;select pc+2 ;select value from bus ;select output of address adder
DRMUX/1:	11.9 R7	;destination IR[11:9] ;destination R7
SR1MUX/1:	11.9 8.6	;source IR[11:9] ;source IR[8:6]
ADDR1MUX/1:	PC, BaseR	
ADDR2MUX/2:	ZERO offset6 PCoffset9 PCoffset11	;select the value zero ;select SEXT[IR[5:0]] ;select SEXT[IR[8:0]] ;select SEXT[IR[10:0]]
MARMUX/1:	7.0 ADDER	;select LSHF(ZEXT[IR[7:0]],1) ;select output of address adder
ALUK/2:	ADD, AND, XOR, PASSA	
MIO.EN/1:	NO, YES	
R.W/1:	RD, WR	
DATA.SIZE/1:	BYTE, WORD	
LSHF1/1:	NO, YES	

Table C.1: Data path control signals

# LC-3b Datapath: Some Questions


---

- How does instruction fetch happen in this datapath according to the state machine?
- What is the difference between gating and loading?
  - Gating: Enable/disable an input to be connected to the bus
    - Combinational: during a clock cycle
  - Loading: Enable/disable an input to be written to a register
    - Sequential: e.g., at a clock edge (assume at the end of cycle)
- Is this the smallest hardware you can design?

 
# LC-3b Microprogrammed Control Structure

---

- Patt and Patel, Appendix C, Figure C.4
- Three components:
  - Microinstruction, control store, microsequencer
- **Microinstruction**: control signals that control the datapath (26 of them) and help determine the next state (9 of them)
- Each microinstruction is stored in a *unique location* in the **control store** (a special memory structure)
- *Unique location*: address of the state corresponding to the microinstruction
  - Remember each state corresponds to one microinstruction
- **Microsequencer** determines the address of the next microinstruction (i.e., next state)



Simple Design  
of the Control Structure

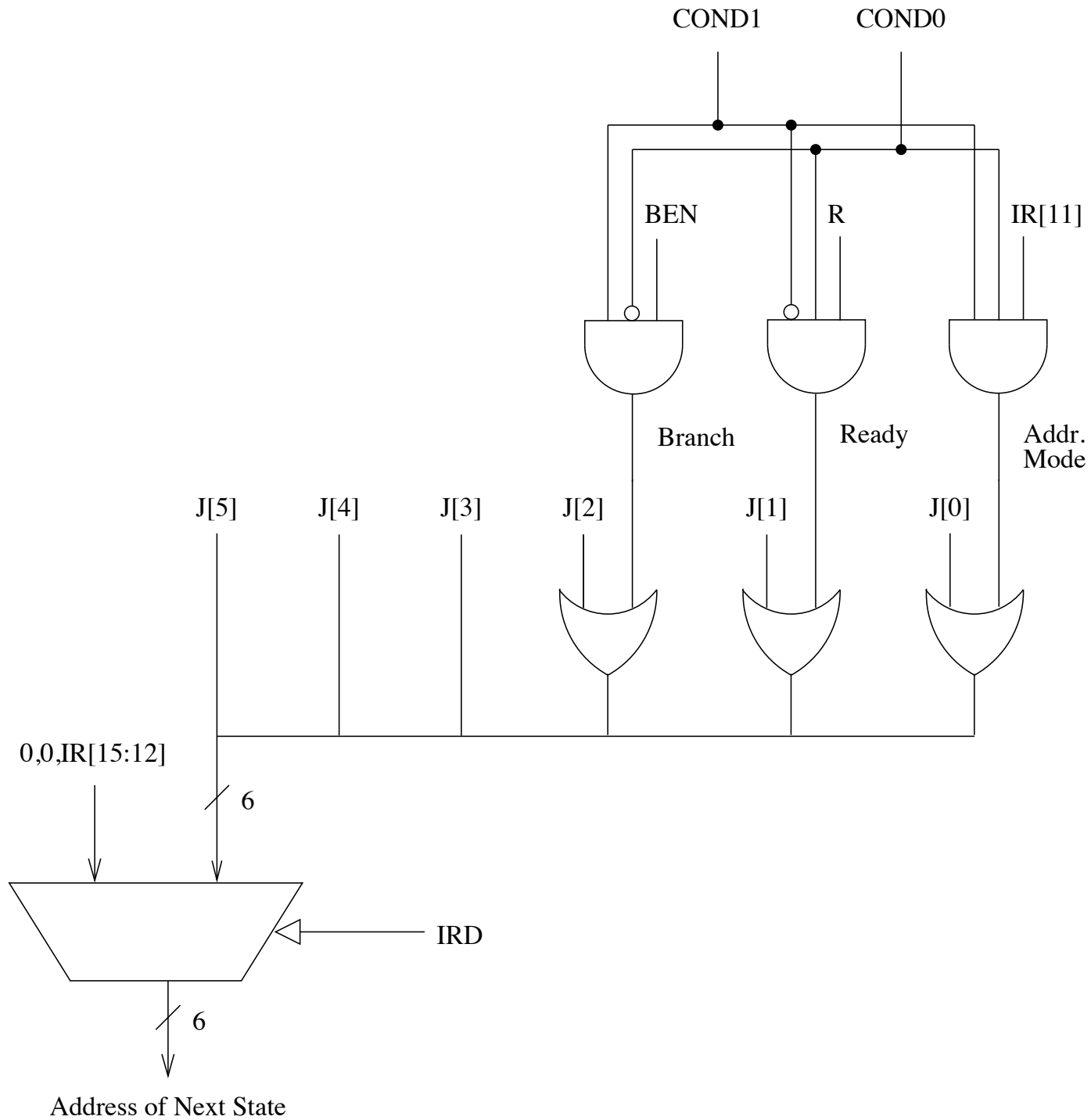

IRD	Cond	J	LDMAR	LDMDR	LDJIR	LD BEN	LD REG	LD CC	LD PC	GasePC	GaseMDR	GaseALLU	GaseMARMID	GaseSHE	PCMUX	DRMIX	SRIMUX	ADDR1MUX	ADDR2MUX	MARMUX	ALUK	MIOLEN	RW	DATASIZE	LSHF1
																									000000 (State 0)
																									000001 (State 1)
																									000010 (State 2)
																									000011 (State 3)
																									000100 (State 4)
																									000101 (State 5)
																									000110 (State 6)
																									000111 (State 7)
																									001000 (State 8)
																									001001 (State 9)
																									001010 (State 10)
																									001011 (State 11)
																									001100 (State 12)
																									001101 (State 13)
																									001110 (State 14)
																									001111 (State 15)
																									010000 (State 16)
																									010001 (State 17)
																									010010 (State 18)
																									010011 (State 19)
																									010100 (State 20)
																									010101 (State 21)
																									010110 (State 22)
																									010111 (State 23)
																									011000 (State 24)
																									011001 (State 25)
																									011010 (State 26)
																									011011 (State 27)
																									011100 (State 28)
																									011101 (State 29)
																									011110 (State 30)
																									011111 (State 31)
																									100000 (State 32)
																									100001 (State 33)
																									100010 (State 34)
																									100011 (State 35)
																									100100 (State 36)
																									100101 (State 37)
																									100110 (State 38)
																									100111 (State 39)
																									101000 (State 40)
																									101001 (State 41)
																									101010 (State 42)
																									101011 (State 43)
																									101100 (State 44)
																									101101 (State 45)
																									101110 (State 46)
																									101111 (State 47)
																									110000 (State 48)
																									110001 (State 49)
																									110010 (State 50)
																									110011 (State 51)
																									110100 (State 52)
																									110101 (State 53)
																									110110 (State 54)
																									110111 (State 55)
																									111000 (State 56)
																									111001 (State 57)
																									111010 (State 58)
																									111011 (State 59)
																									111100 (State 60)

# LC-3b Microsequencer


---

- Patt and Patel, Appendix C, Figure C.5
- The purpose of the microsequencer is to determine the address of the next microinstruction (i.e., next state)
  - Next state could be conditional or unconditional
- Next state address depends on 9 control signals (plus 7 data signals)

Signal Name	Signal Values
J/6:	
COND/2:	COND <sub>0</sub> ;Unconditional
	COND <sub>1</sub> ;Memory Ready
	COND <sub>2</sub> ;Branch
	COND <sub>3</sub> ;Addressing Mode
IRD/1:	NO, YES

---

Table C.2: Microsequencer control signals

 



# The Microsequencer: Some Questions

---

- When is the IRD signal asserted?
- What happens if an illegal instruction is decoded?
- What are condition (COND) bits for?
- How is variable latency memory handled?
- How do you do the state encoding?
  - Minimize number of state variables ( $\sim$  control store size)
  - Start with the 16-way branch
  - Then determine constraint tables and states dependent on COND


# An Exercise in Microprogramming

# Handouts

---


- 7 pages of Microprogrammed LC-3b design
- <https://safari.ethz.ch/digitaltechnik/spring2018/lib/exe/fetch.php?media=lc3b-figures.pdf>


# A Simple LC-3b Control and Datapath

 

(J, COND, IRD)

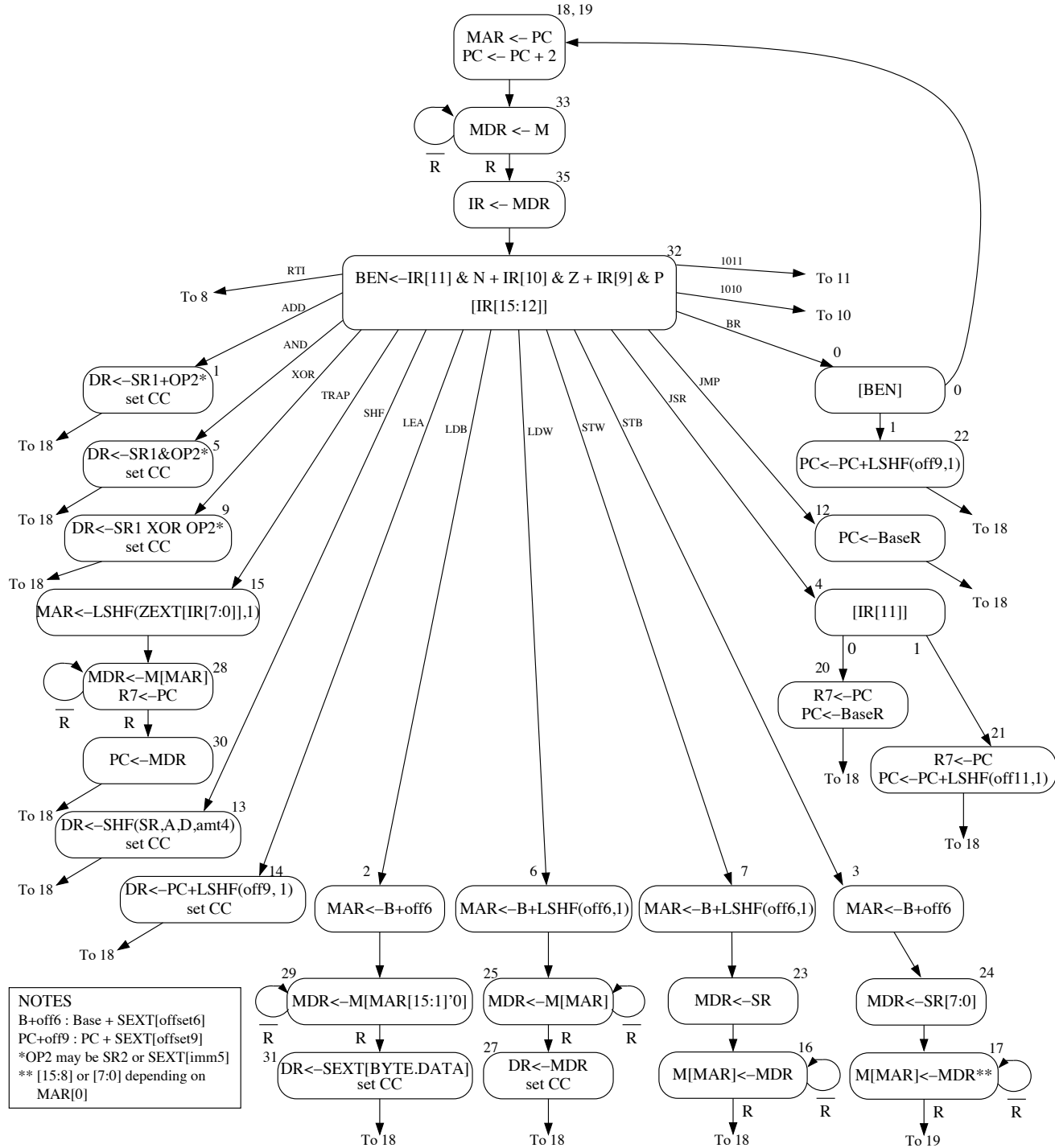
Microarchitecture of the LC-3b, major components



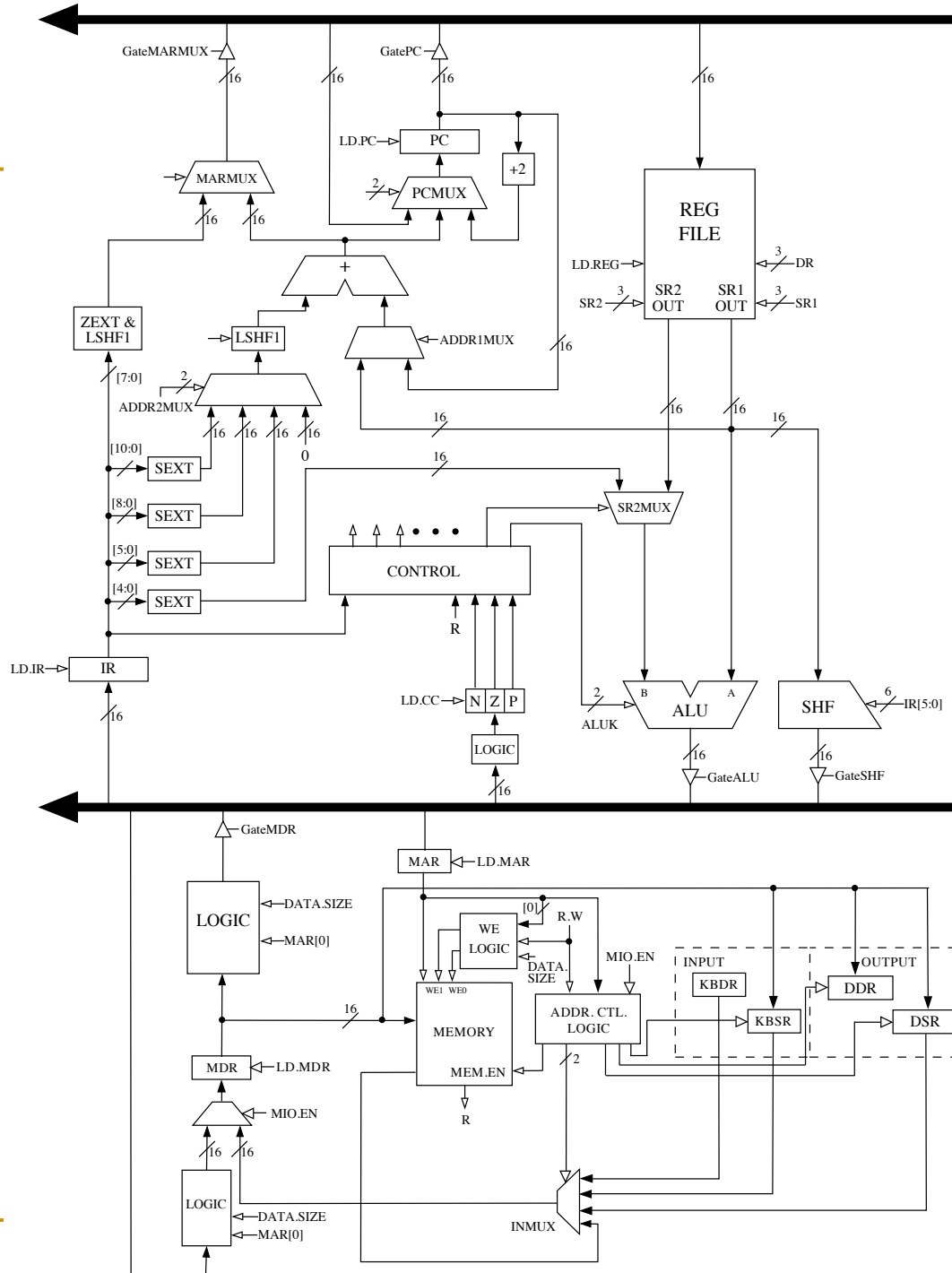


A Simple Datapath  
Can Become  
Very Powerful

## State Machine for LDW

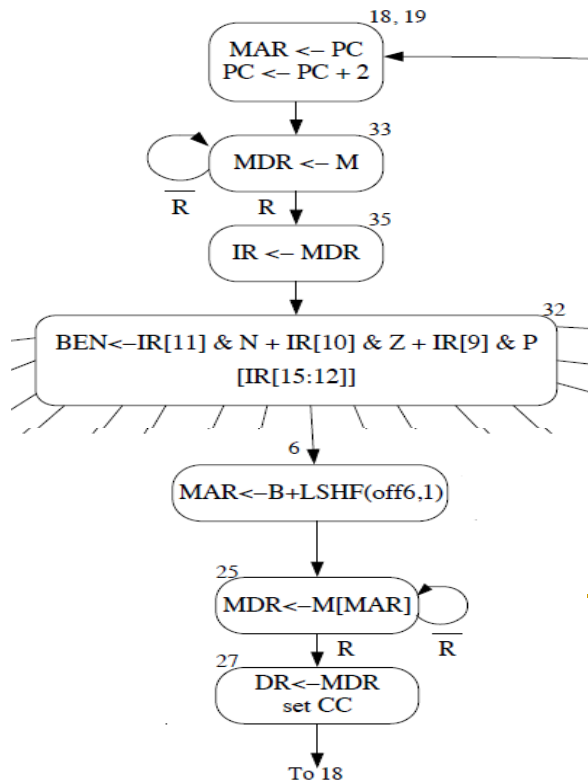


## Microsequencer

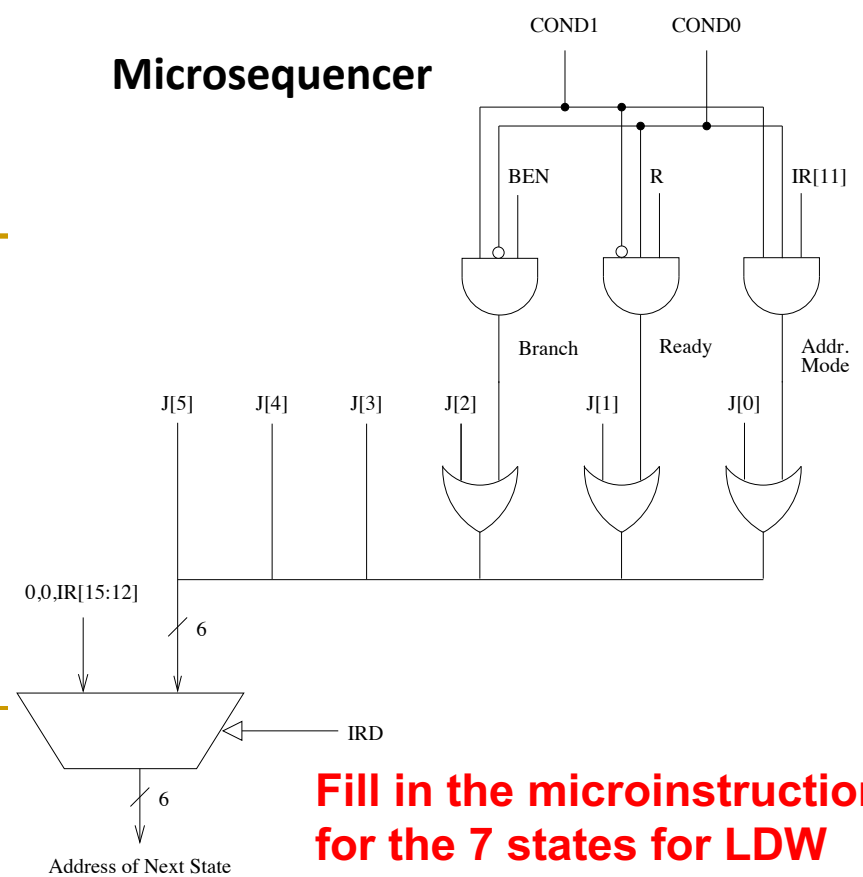


## Fill in the microinstructions for the 7 states for LDW


	IRD	Cond	J					LD.MAR	LD.MDR	LD.IR	LD.BEN	LD.REG	LD.CC	LD.PC	GatePC	GateMDR	GateALU	GateMARMUX	GateSHF	PCMUX	DRMUX	SRIOMUX	ADDR1MUX	ADDR2MUX	MARMUX	ALUK	MIO.EN	R.W	DATA.SIZE	LSHF1
State 18 (010010)																														
State 33 (100001)																														
State 35 (100011)																														
State 32 (100000)																														
State 6 (000110)																														
State 25 (011001)																														
State 27 (011011)																														

 

(a)

 

(b)

 


(c)




Signal Name	Signal Values	
LD.MAR/1:	NO, LOAD	
LD.MDR/1:	NO, LOAD	
LD.IR/1:	NO, LOAD	
LD.BEN/1:	NO, LOAD	
LD.REG/1:	NO, LOAD	
LD.CC/1:	NO, LOAD	
LD.PC/1:	NO, LOAD	
GatePC/1:	NO, YES	
GateMDR/1:	NO, YES	
GateALU/1:	NO, YES	
GateMARMUX/1:	NO, YES	
GateSHF/1:	NO, YES	
PCMUX/2:	PC+2 BUS ADDER	;select pc+2 ;select value from bus ;select output of address adder
DRMUX/1:	11.9 R7	;destination IR[11:9] ;destination R7
SR1MUX/1:	11.9 8.6	;source IR[11:9] ;source IR[8:6]
ADDR1MUX/1:	PC, BaseR	
ADDR2MUX/2:	ZERO offset6 PCoffset9 PCoffset11	;select the value zero ;select SEXT[IR[5:0]] ;select SEXT[IR[8:0]] ;select SEXT[IR[10:0]]
MARMUX/1:	7.0 ADDER	;select LSHF(ZEXT[IR[7:0]],1) ;select output of address adder
ALUK/2:	ADD, AND, XOR, PASSA	
MIO.EN/1:	NO, YES	
R.W/1:	RD, WR	
DATA.SIZE/1:	BYTE, WORD	
LSHF1/1:	NO, YES	

Table C.1: Data path control signals

 

Simple Design  
of the Control Structure

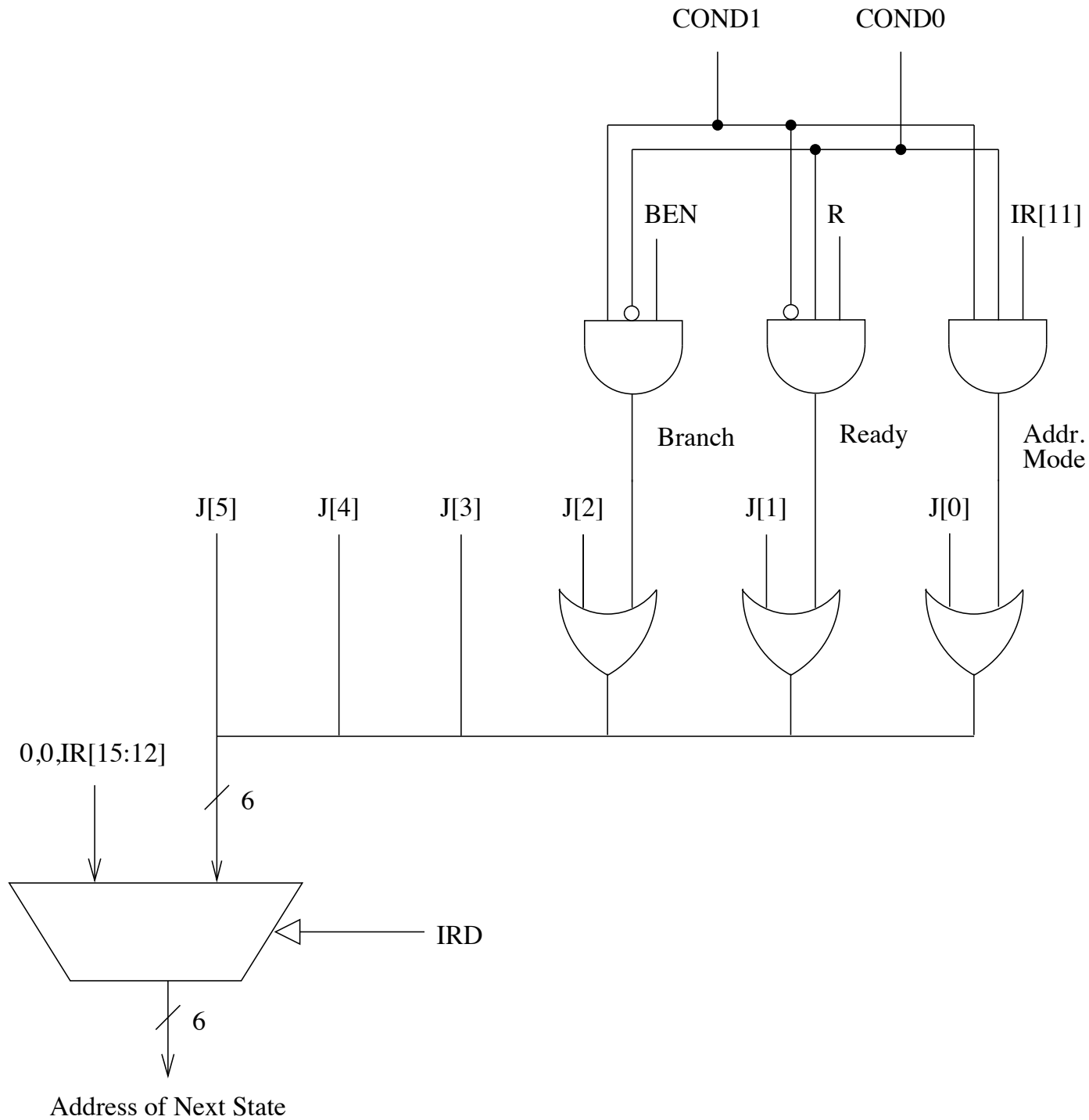

64

# End of the Exercise in Microprogramming

# Variable-Latency Memory

---

- The ready signal (R) enables memory read/write to execute correctly
  - Example: transition from state 33 to state 35 is controlled by the R bit asserted by memory when memory data is available
- Could we have done this in a single-cycle microarchitecture?
- What did we assume about memory and registers in a single-cycle microarchitecture?

# The Microsequencer: Advanced Questions

---

- What happens if the machine is interrupted?
- What if an instruction generates an exception?
- How can you implement a complex instruction using this control structure?
  - Think REP MOVS instruction in x86
    - string copy of N elements starting from address A to address B

# The Power of Abstraction

---

- The concept of a control store of microinstructions enables the hardware designer with a new abstraction:  
microprogramming
- The designer can translate any desired operation to a sequence of microinstructions
- All the designer needs to provide is
  - The sequence of microinstructions needed to implement the desired operation
  - The ability for the control logic to correctly sequence through the microinstructions
  - Any additional datapath elements and control signals needed (no need if the operation can be “translated” into existing control signals)



# Let's Do Some More Microprogramming

---

- Implement REP MOVS in the LC-3b microarchitecture
- What changes, if any, do you make to the
  - state machine?
  - datapath?
  - control store?
  - microsequencer?
- Show all changes and microinstructions
- Optional HW Assignment

# x86 REP MOVSB (String Copy) Instruction

## REP MOVSB (DEST SRC)

```
IF AddressSize = 16
    THEN
        Use CX for CountReg;
    ELSE IF AddressSize = 64 and REX.W used
        THEN Use RCX for CountReg; FI;
    ELSE
        Use ECX for CountReg;
FI;
WHILE CountReg ≠ 0
    DO
        Service pending interrupts (if any);
        Execute associated string instruction;
        CountReg ← (CountReg - 1);
        IF CountReg = 0
            THEN exit WHILE loop; FI;
        IF (Repeat prefix is REPZ or REPE) and (ZF = 0)
        or (Repeat prefix is REPNZ or REPNE) and (ZF = 1)
            THEN exit WHILE loop; FI;
    OD;
```

```
DEST ← SRC;
IF (Byte move)
    THEN IF DF = 0
        THEN
            (R)ESI ← (R)ESI + 1;
            (R)EDI ← (R)EDI + 1;
        ELSE
            (R)ESI ← (R)ESI - 1;
            (R)EDI ← (R)EDI - 1;
        FI;
    ELSE IF (Word move)
        THEN IF DF = 0
            (R)ESI ← (R)ESI + 2;
            (R)EDI ← (R)EDI + 2;
            FI;
        ELSE
            (R)ESI ← (R)ESI - 2;
            (R)EDI ← (R)EDI - 2;
        FI;
    ELSE IF (Doubleword move)
        THEN IF DF = 0
            (R)ESI ← (R)ESI + 4;
            (R)EDI ← (R)EDI + 4;
            FI;
        ELSE
            (R)ESI ← (R)ESI - 4;
            (R)EDI ← (R)EDI - 4;
        FI;
    ELSE IF (Quadword move)
        THEN IF DF = 0
            (R)ESI ← (R)ESI + 8;
            (R)EDI ← (R)EDI + 8;
            FI;
        ELSE
            (R)ESI ← (R)ESI - 8;
            (R)EDI ← (R)EDI - 8;
        FI;
    FI;
```

FI;

*How many instructions does this take in MIPS ISA?*

*How many microinstructions does this take to add to the LC-3b microarchitecture?*

# Aside: Alignment Correction in Memory

---

- Unaligned accesses
- LC-3b has byte load and byte store instructions that move data not aligned at the word-address boundary
  - Convenience to the programmer/compiler
- How does the hardware ensure this works correctly?
  - Take a look at state 29 for LDB
  - States 24 and 17 for STB
  - Additional logic to handle unaligned accesses
- P&P, Revised Appendix C.5

# Aside: Memory Mapped I/O

---

- Address control logic determines whether the specified address of LDW and STW are to memory or I/O devices
- Correspondingly enables memory or I/O devices and sets up muxes
- An instance where the final control signals of some datapath elements (e.g., MEM.EN or INMUX/2) **cannot** be stored in the control store
  - These signals are dependent on memory address
- P&P, Revised Appendix C.6

# Advantages of Microprogrammed Control

---

- Allows a very simple design to do powerful computation by controlling the datapath (using a sequencer)
  - High-level ISA translated into microcode (sequence of u-instructions)
  - Microcode (u-code) enables a minimal datapath to emulate an ISA
  - Microinstructions can be thought of as a **user-invisible ISA (u-ISA)**
- Enables easy extensibility of the ISA
  - **Can support a new instruction by changing the microcode**
  - Can support complex instructions as a sequence of simple microinstructions (e.g., REP MOVS, INC [MEM])
- Enables update of machine behavior
  - **A buggy implementation of an instruction can be fixed by changing the microcode in the field**
    - Easier if datapath provides ability to do the same thing in different ways

# Update of Machine Behavior

---

- The ability to update/patch microcode in the field (after a processor is shipped) enables
  - Ability to add new instructions without changing the processor!
  - Ability to “fix” buggy hardware implementations
  
- Examples
  - IBM 370 Model 145: microcode stored in main memory, can be updated after a reboot
  - IBM System z: Similar to 370/145.
    - Heller and Farrell, “Millicode in an IBM zSeries processor,” IBM JR&D, May/Jul 2004.
  - B1700 microcode can be updated while the processor is running
    - User-microprogrammable machine!
    - Wilner, “Microprogramming environment on the Burroughs B1700”, CompCon 1972.

# Multi-Cycle vs. Single-Cycle uArch

---

- Advantages
- Disadvantages
- For you to fill in

Can We Do Better?



# Design of Digital Circuits

## Lecture 13: Microprogramming

Prof. Onur Mutlu

ETH Zurich

Spring 2018

13 April 2018