

# Design of Digital Circuits

Lab 2 Supplement:

Mapping Your Circuit to FPGA

Prof. Onur Mutlu

ETH Zurich

Spring 2019

12 March 2019

# What Will We Learn?

---

- In Lab 2, you will learn **how to map your circuits to an FPGA.**
- Design a 4-bit adder.
  - Design a **1-bit full-adder.**
  - Use full-adders to design a **4-bit adder.**
- Program your FPGA using Vivado software for HDL design.
- Work with your FPGA board and see the results of your designs on the FPGA output (in this case LEDs).

# Design an Adder (I)


---

- **Design a full-adder:** Receives two 1-bit numbers A and B and a 1-bit input carry (C\_in), and returns outputs S and C as sum and carry of the operation, respectively.

- Example: A = 1, B = 1, C\_in = 1

- S = 1

- C = 1

 


# Design an Adder (II)

---

- **Design a 4-bit adder:** Receives two 1-bit numbers A and B and a 1-bit input carry ( $C_{in}$ ), and returns outputs S and C as sum and carry of the operation, respectively.
  - Example:  $A = 1110$ ,  $B = 0001$ ,  $C_{in}=1$

- $S = 0000$
- $C = 1$

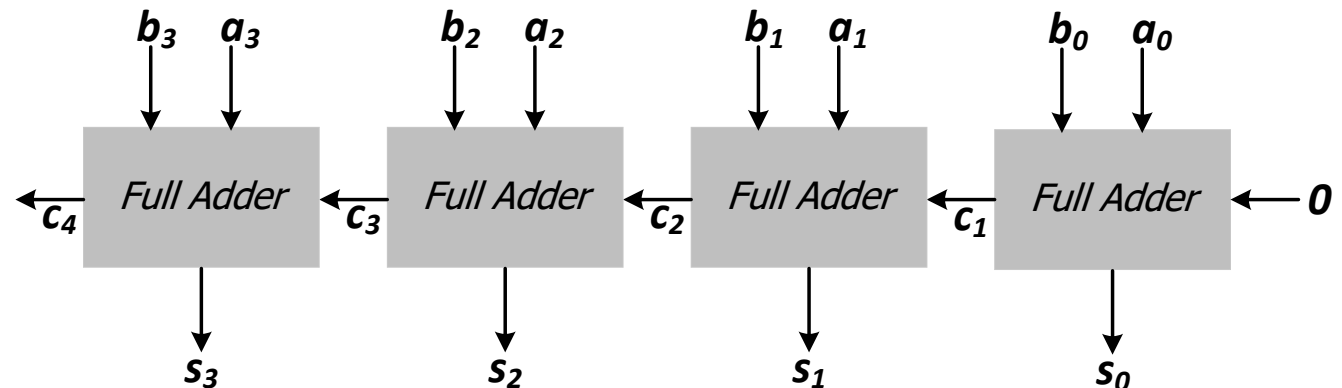

- **Hint:** Use four full-adders to design a 4-bit adder.

# Design an Adder (Overview)

---

1. You will use **truth tables** to derive the **Boolean equation** of the adder.
2. You will design the **schematic of the circuit** using logic gates.
3. In the next step, you will use Vivado to write your design in **Verilog**.
4. In the end, you will use Vivado to **program the FPGA**.

# Vivado

---


- For this course, we use the software Vivado for FPGA programming.
- The computers in the lab rooms are already installed with the necessary software.
- If you wish to use your own computer, you can refer to the following instructions:
  - <https://reference.digilentinc.com/learn/programmable-logic/tutorials/basys-3-getting-started/start>

# Verilog
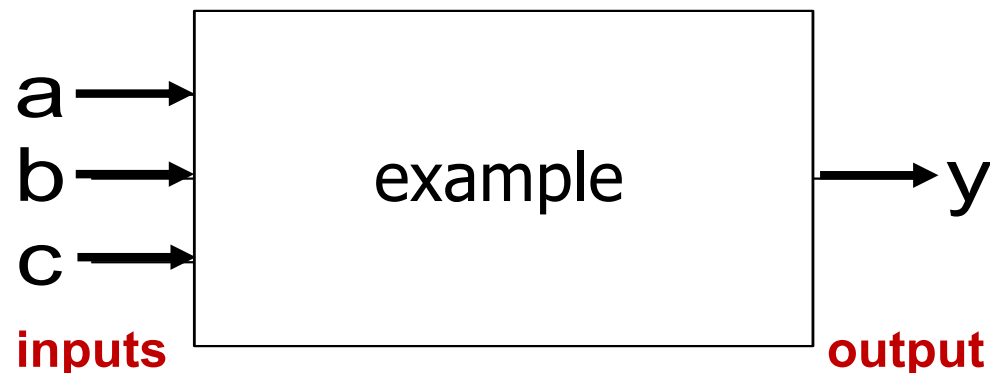
# Defining a Module in Verilog

---



- A **module** is the main building block in Verilog.
- We first need to define:
  - **Name** of the module
  - **Directions** of its **ports** (e.g., **input**, **output**)
  - **Names** of its **ports**
- Then:
  - Describe the **functionality** of the module.






# Implementing a Module in Verilog

---

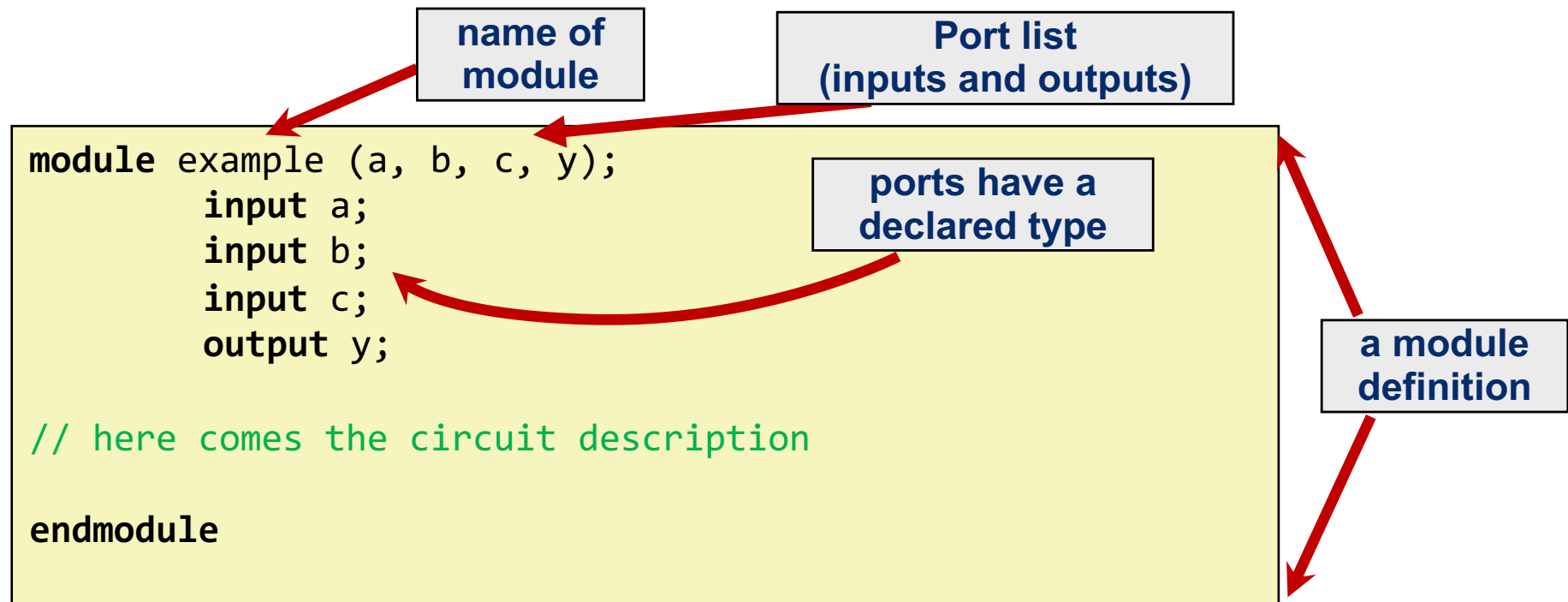 

# Structural HDL: Instantiating a Module

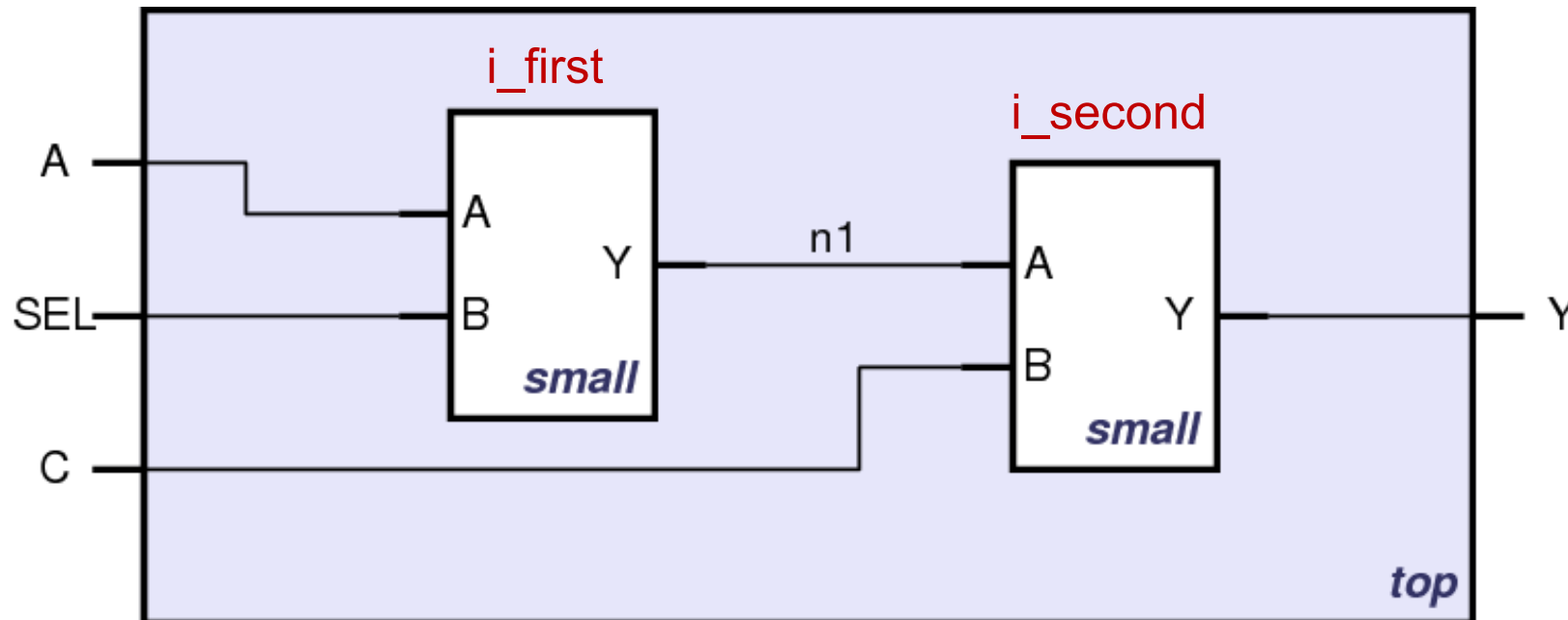


**Schematic of module "top" that is built from two instances of module "small"**

# Structural HDL Example (1)

## ■ Module Definitions in Verilog

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```


```
endmodule
```

# Structural HDL Example (2)

## ■ Defining wires (module interconnections)

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
endmodule
```

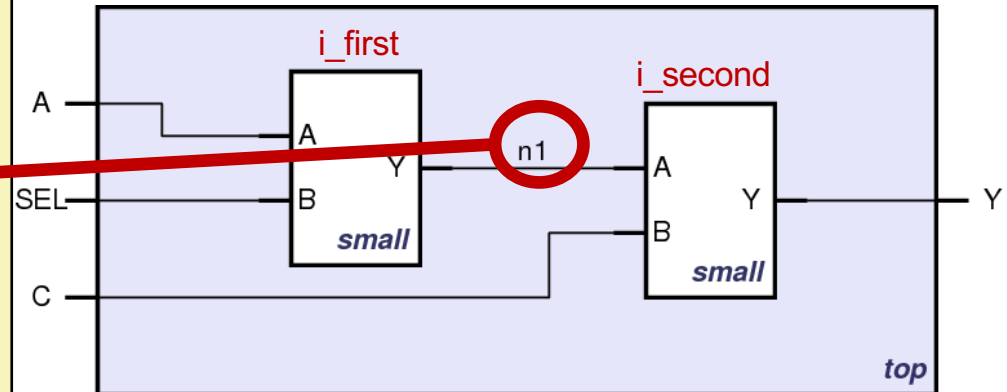

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```

```
endmodule
```


# Structural HDL Example (3)

## ■ The first instantiation of the "small" module

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
// instantiate small once  
small i_first ( .A(A),  
                .B(SEL),  
                .Y(n1) );
```

```
endmodule
```

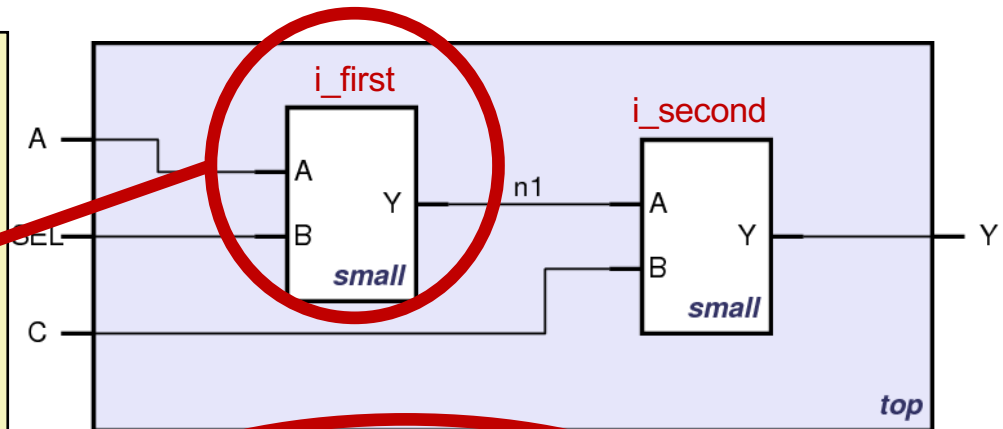

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```


```
// description of small
```

```
endmodule
```

# Structural HDL Example (4)
 
## ■ The second instantiation of the “small” module

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
  // instantiate small once  
  small i_first ( .A(A),  
                 .B(SEL),  
                 .Y(n1) );  
  
  // instantiate small second time  
  small i_second ( .A(n1),  
                 .B(C),  
                 .Y(Y) );  
  
endmodule
```




```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```

# Structural HDL Example (5)
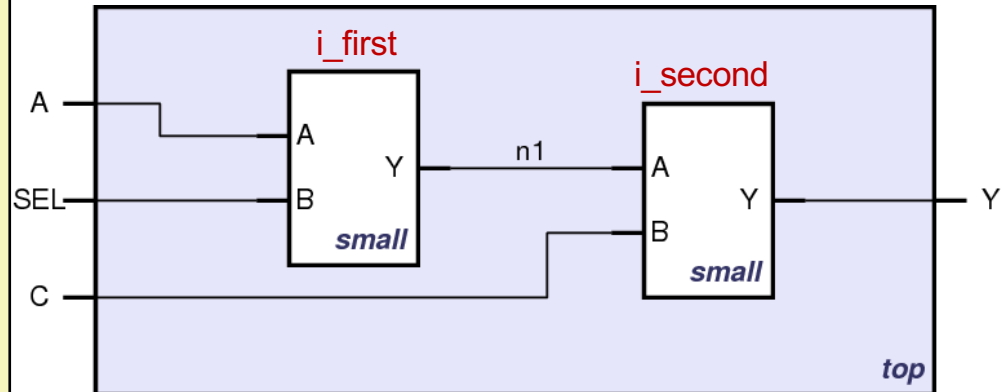
## ■ Short form of module instantiation

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
  // alternative  
  small i_first ( A, SEL, n1 );  
  
  /* Shorter instantiation,  
     pin order very important */  
  
  // any pin order, safer choice  
  small i_second ( .B(C),  
                  .Y(Y),  
                  .A(n1) );  
  
endmodule
```



```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```


# Basys 3 FPGA Board

---

In this course, we will be using the Basys 3 boards from Digilent, as shown below.

You can learn more about the Basys 3 Starter Board from:
 
<http://store.digilentinc.com/basys-3-artix-7-fpga-trainer-board-recommended-for-introductory-users/>





# Last Words

---

- In this lab, you will map your circuit to an FPGA.
- First you will design a 4-bit adder.
- Then, you will learn how to use Xilinx Vivado for writing Verilog and how to connect to the Basys 3 board.
- Finally, you will program the FPGA and get the circuit running on the FPGA board.
- You will find **more exercises in the lab report.**

# Design of Digital Circuits

Lab 2 Supplement:

Mapping Your Circuit to FPGA

Prof. Onur Mutlu

ETH Zurich

Spring 2019

12 March 2019