

Design of Digital Circuits

Lab 4 Supplement:

Finite State Machines

Prof. Onur Mutlu

ETH Zurich

Spring 2019


26 March 2019

What Will We Learn?

- In Lab 4, you will **implement a finite state machine using Verilog.**
- Design and implement a simple circuit that emulates the blinking lights of a Ford Thunderbird.
- Understand how the **clock signal is derived in the FPGA board.**
- **Write an FSM** that implements the Ford Thunderbird blinking sequence.

Tail Lights of a 1965 Ford Thunderbird

 - In this lab, you will design a finite state machine to control the tail lights of a 1965 Ford Thunderbird.




Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Tail Lights of a 1965 Ford Thunderbird

- There are three lights on each side that operate in sequence to indicate the direction of a turn.

 Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e



Copyright from ClassicLEDs.com



Part 1: FSM Design

- The job of an FSM is to do three things:
 - **Next State Logic:** Determine the next state from the **present state** and **the inputs**.
 - **Output Logic:** If a Mealy FSM is used, realize the output function based on the **present state** and **the input**.
 - **State Register:** Advance from the present state to next state **when a clock event arrives**.
 - **Note:** The manual contains the details of this FSM specifications.

Part 1: FSM Design


- The job of an FSM is to do three things:
 - **Next State Logic:** Determine the next state from the **present state** and **the inputs**.
 - **Output Logic:** If a Mealy FSM is used, realize the output function based on the **present state** and **the input**.
 - **State Register:** Advance from the present state to next state **when a clock event arrives**.

For more details on FSM designs (Mealy vs. Moore) please refer to lecture 7.1, slide 13:

[Link](#)


Part 2: Verilog Implementation

- Separate three parts of the code:

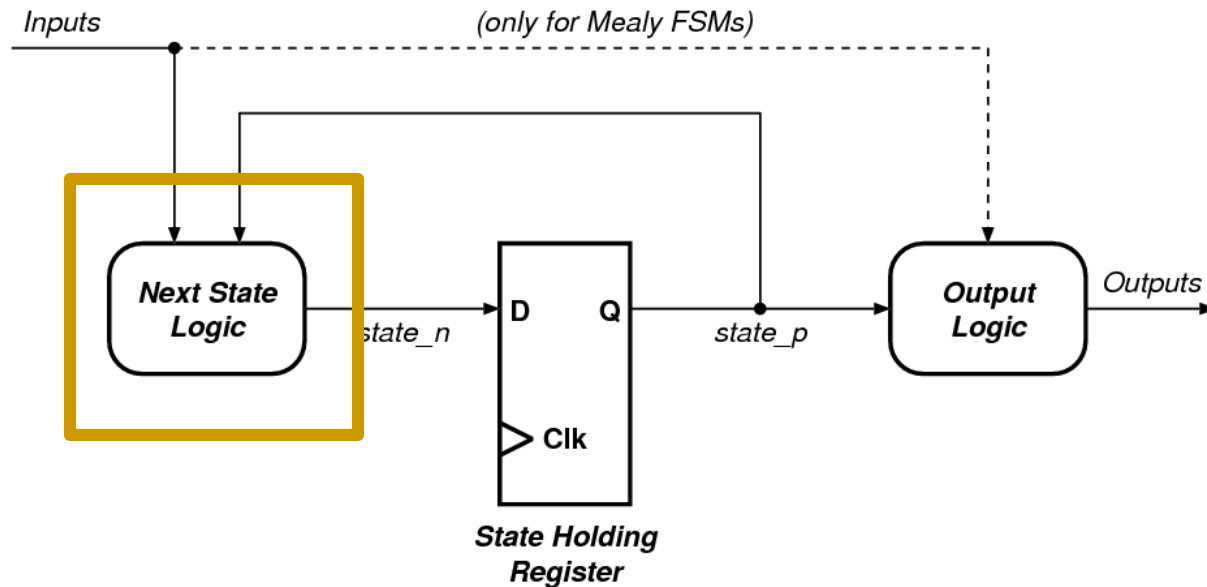


Part 2: Verilog Implementation

- Separate three parts of the code:

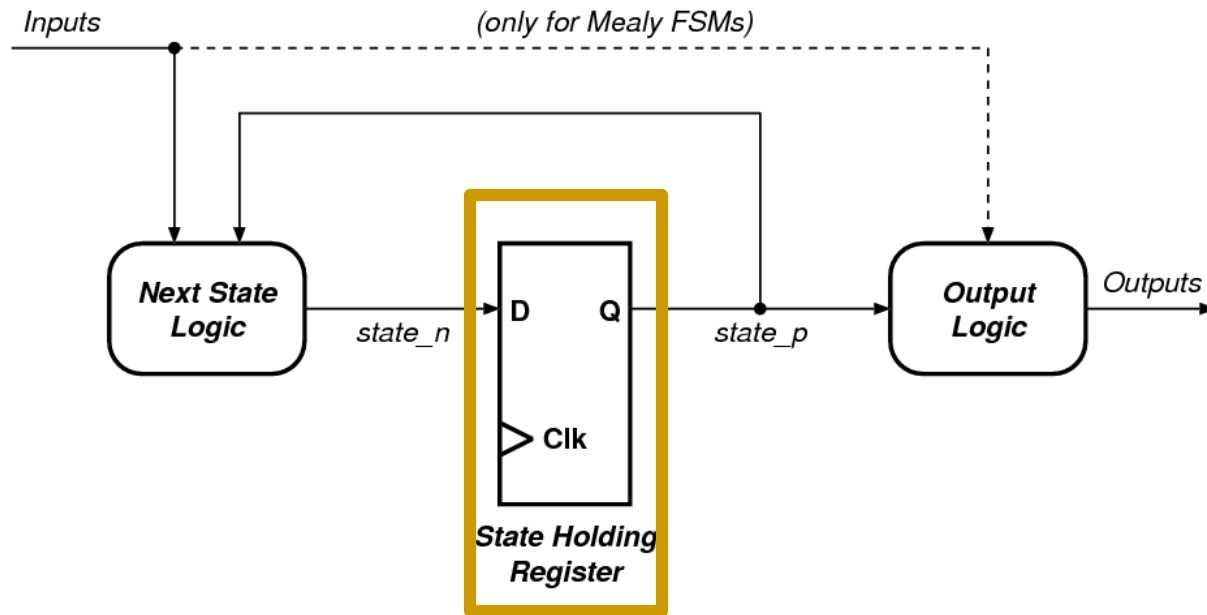


Part 2: Verilog Implementation

- Separate three parts of the code:

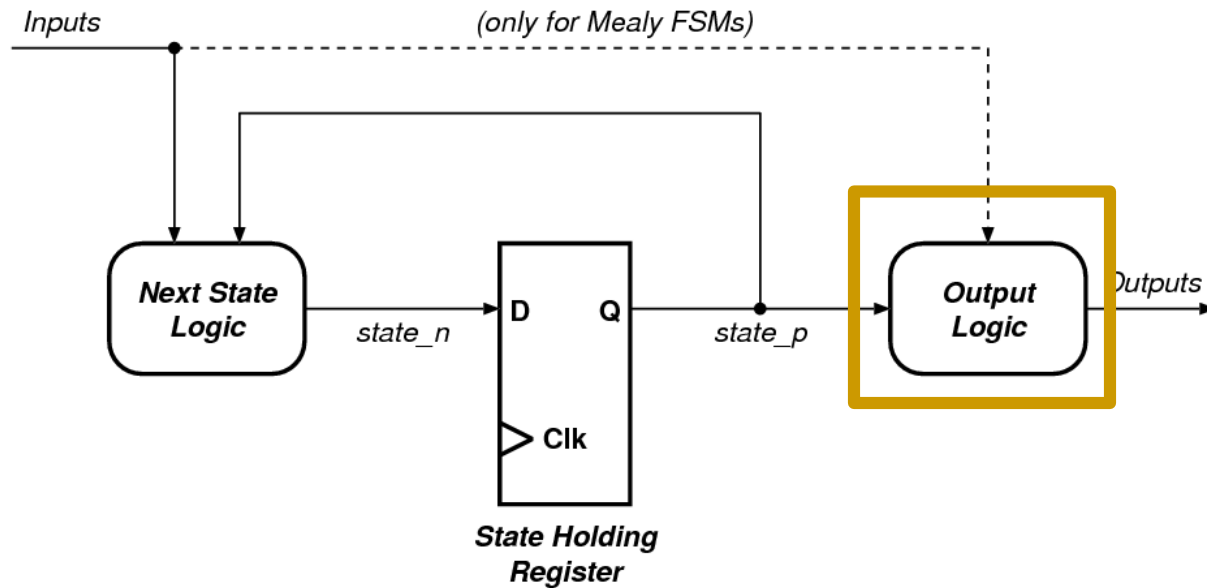

Part 4: Implementing the Clock (I)

- The problem of using push-buttons as clock:
 - ❑ Compared to the speed of the FPGA the change in a push button is very very slow (1million x)
 - ❑ During the slow transition, the FPGA will see many fast occurring transitions and would interpret each of them as a clock edge. (Bouncing)

 

Part 4: Implementing the Clock (II)

- **CLK100Mhz (W5):** Your board contains a 100Mhz crystal oscillator circuit.
- **Problem:** The clock is too fast.
- **Solution:** A clock divider:

```
module clk_div(input clk, input rst, output clk_en);  
    reg [24:0] clk_count;  
    always @ (posedge clk)  
        //posedge defines a rising edge (transition from 0 to 1)  
        begin  
            if (rst)  
                clk_count <= 0;  
            else  
                clk_count <= clk_count + 1;  
            end  
            assign clk_en = &clk_count;  
        endmodule
```

Part 4: Defining the Constraints

- Buttons for control
- LEDs for output lights
- Connections for clock

Last Words

- In Lab 4, you will **implement a finite state machine using Verilog**.
- Design and implement a simple circuit that emulates the blinking lights of a Ford Thunderbird.
- Understand how the **clock signal is derived in the FPGA board**.
- **Write an FSM** that implements the Ford Thunderbird blinking sequence.
- In the report, you will implement a **dimming function**, so that the lights are not only on and off, but can have intermediate levels

Design of Digital Circuits

Lab 4 Supplement:

Finite State Machines

Prof. Onur Mutlu

ETH Zurich

Spring 2019

26 March 2019