

DESIGN OF DIGITAL CIRCUITS (252-0028-00L), SPRING 2019  
OPTIONAL HW 2: COMBINATIONAL LOGIC

Instructor: Prof. Onur Mutlu

TAs: Mohammed Alser, Can Firtina, Hasan Hassan, Juan Gomez Luna, Lois Orosa, Giray Yaglikci

Released: Monday, Mar 11, 2019

## 1 Transistor-Level Circuit Design

In Lecture 4, we learned how to implement digital circuits using the CMOS technology (i.e., p-type and n-type MOS transistors). In this assignment, we ask you to schematically design circuits using CMOS transistors for the following logic gates:

- Exclusive OR Gate (XOR)
- Exclusive NOT OR Gate (XNOR)

## 2 Multiplexer (MUX)

Draw the following schematics for an 8-input (8:1) MUX.

- Gate level: as a combination of basic AND, OR, NOT gates. Use as few gates as possible.
- Module level: as a combination of 2-input (2:1) MUXes. Use as few 2-input MUXes as possible.

## 3 Logical Completeness

The set of {AND, OR, and NOT} gates is logically complete. We can build a circuit to carry out the specification of any truth table we wish, without using any other kind of gate. From Lecture 4, you know that the NOR gate by itself is also logically complete. Prove that you can build a circuit to carry out the specification of any truth table, by using only NOR gates.

## 4 Boolean Logic and Truth Tables

In this question we ask you to derive the boolean equations for two 4-input logic functions,  $X$  and  $Y$ . Please use the truth table below to answer the following three questions.

Inputs				Outputs	
$A_3$	$A_2$	$A_1$	$A_0$	$X$	$Y$
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

- (a) The output  $X$  is *one* when the input does **not** contain 3 consecutive 1's in the word  $A_3, A_2, A_1, A_0$ . The output  $X$  is *zero*, otherwise. **Fill in the truth table above** and use the *product of sums* form to **write the corresponding boolean equation** for  $X$ . (*No simplification needed.*)
- (b) The output  $Y$  is *one* when no two adjacent bits in the word  $A_3, A_2, A_1, A_0$  are the same (e.g., if  $A_2$  is 0 then  $A_3$  and  $A_1$  cannot be 0). The output  $Y$  is *zero*, otherwise (e.g., 0000). **Fill in the truth table above** and use the *sum of products* form to **write the corresponding boolean equation** for  $Y$ . (*No simplification needed.*)
- (c) Please represent the circuit of  $Y$  using *only* 2-input XOR and AND gates.

## 5 Boolean Algebra

- (a) Find the simplest sum-of-products representation of the following Boolean equation. Show your work step-by-step.

$$F = B + (A + \overline{C}).(\overline{A} + \overline{B} + \overline{C})$$

- (b) Convert the following Boolean equation so that it only contains NAND operations. Show your work step-by-step.

$$F = \overline{(A + B.C)} + \overline{C}$$

- (c) Using Boolean algebra, simplify the following min-terms:  $\sum(3, 5, 7, 11, 13, 15)$   
Show your work step-by-step.