

Digital Design and Computer Architecture: Lab Report		
Lab 1: Drawing Basic Circuits		
Date		Grade
Names		
		Lab session / lab room

You have to submit this report via Moodle.

Use a zip file or tarball that contains the report and other required material. Only one of the members of each group should submit. All members of the group will get the same grade.

The name of the submitted file should be *Lab1_LastName1_LastName2.zip* (or *.tar*), where *LastName1* and *LastName2* are the last names of the members of the group.

Note 1: Please include all the required material. No links/shortcuts are accepted.

Note 2: The deadline for the report is a hard deadline and it will not be extended.

Exercise 1

(a) Assume that we were only using 2-input AND gates and 2-input XNOR gates to create our comparator in Part 1 in this week's lab manual. How many of each gate would you use for a comparator of width 8, 16, 32 and 64 bits? What is the logic depth in each case?

Note: the logic depth of a combinational circuit is defined as the number of logic gates in the longest signal path (path from input to output).

<u>Comparator Width</u>	<u>2-input XNOR gates</u>	<u>2-input AND gates</u>	<u>Logic depth</u>
8 bits			
16 bits			
32 bits			
64 bits			

(b) Given the comparator width is N , derive general expressions for calculating the following:

(i) The number of 2-input XNOR gates

(ii) The number of 2-input AND gates

(iii) The logic depth

Exercise 2

Use two instances of the 1-bit comparator we designed in Part 2 in this week's lab to implement a 2-bit comparator. Draw the schematic of your design.

Exercise 3

What is the logic depth of each of the output ports in the circuit of Exercise 2?

Feedback

If you have any comments about the exercise please add them here: mistakes in the text, difficulty level of the exercise, anything that will help us improve it for the next time.