

# Design of Digital Circuits

## Lecture 7.2: Hardware Description Languages and Verilog

Prof. Onur Mutlu

ETH Zurich

Spring 2019

14 March 2019

# Required Readings (This Week)

---

- Hardware Description Languages and Verilog
  - H&H Chapter 4 in full
- Timing and Verification
  - H&H Chapters 2.9 and 3.5 + (start Chapter 5)
- By tomorrow, make sure you are done with
  - **P&P Chapters 1-3 + H&H Chapters 1-4**

# Required Readings (Next Week)

---

- Von Neumann Model, LC-3, and MIPS
  - P&P, Chapter 4, 5
  - H&H, Chapter 6
  - P&P, Appendices A and C (ISA and microarchitecture of LC-3)
  - H&H, Appendix B (MIPS instructions)
  
- Programming
  - P&P, Chapter 6
  
- **Recommended:** Digital Building Blocks
  - H&H, Chapter 5

# Agenda

---


- Hardware Description Languages
- Implementing Combinational Logic (in Verilog)
- Implementing Sequential Logic (in Verilog)
  
- The Verilog slides constitute a tutorial. We will not cover all.
- All slides will be beneficial for your labs.



# Hardware Description Languages & Verilog (Combinational Logic)

# 2017: Intel Kaby Lake

---

 

[https://en.wikichip.org/wiki/intel/microarchitectures/kaby\\_lake](https://en.wikichip.org/wiki/intel/microarchitectures/kaby_lake)

- **64-bit processor**
- **4 cores, 8 threads**
- **14-19 stage pipeline**
- **3.9 GHz clock**
- **1.75B transistors**
- **In ~47 years, about 1,000,000-fold growth in transistor count and performance!**

# How to Deal with This Complexity?

---

- **Hardware Description Languages!**
  - A fact of life in computer engineering
    - Need to be able to **specify complex designs**
      - communicate with others in your design group
    - ... and to **simulate** their behavior
      - *yes, it's what I want to build*
    - ... and to **synthesize** (automatically design) portions of it
      - have an error-free path to implementation
  - Hardware Description Languages
    - Many similarly featured **HDLs** (e.g., **Verilog**, VHDL, ...)
      - if you learn one, it is **not hard to learn** another
      - mapping between languages is typically **mechanical**, especially for the commonly used subset
-

# Hardware Description Languages

---


- **Two well-known hardware description languages**
- **Verilog**
  - Developed in 1984 by Gateway Design Automation
  - Became an IEEE standard (1364) in 1995
  - More popular in US
- **VHDL (VHSIC Hardware Description Language)**
  - Developed in 1981 by the US Department of Defense
  - Became an IEEE standard (1076) in 1987
  - More popular in Europe
- In this course we will use Verilog

# Hardware Design Using Verilog
 
# Hierarchical Design

<https://techreport.com/review/21987/intel-core-i7-3960x-processor>


- **Design hierarchy of modules is built using instantiation**
  - ❑ Predefined “primitive” gates (AND, OR, ...)
  - ❑ Simple modules are built by instantiating these gates (components like MUXes)
  - ❑ Other modules are built by instantiating simple components, ...
- **Hierarchy controls complexity**
  - ❑ Analogous to the use of function abstraction in SW
- **Complexity is a BIG deal**
  - ❑ In real world how big is size of one “blob” of random logic that we would describe as an HDL, then synthesize to gates?


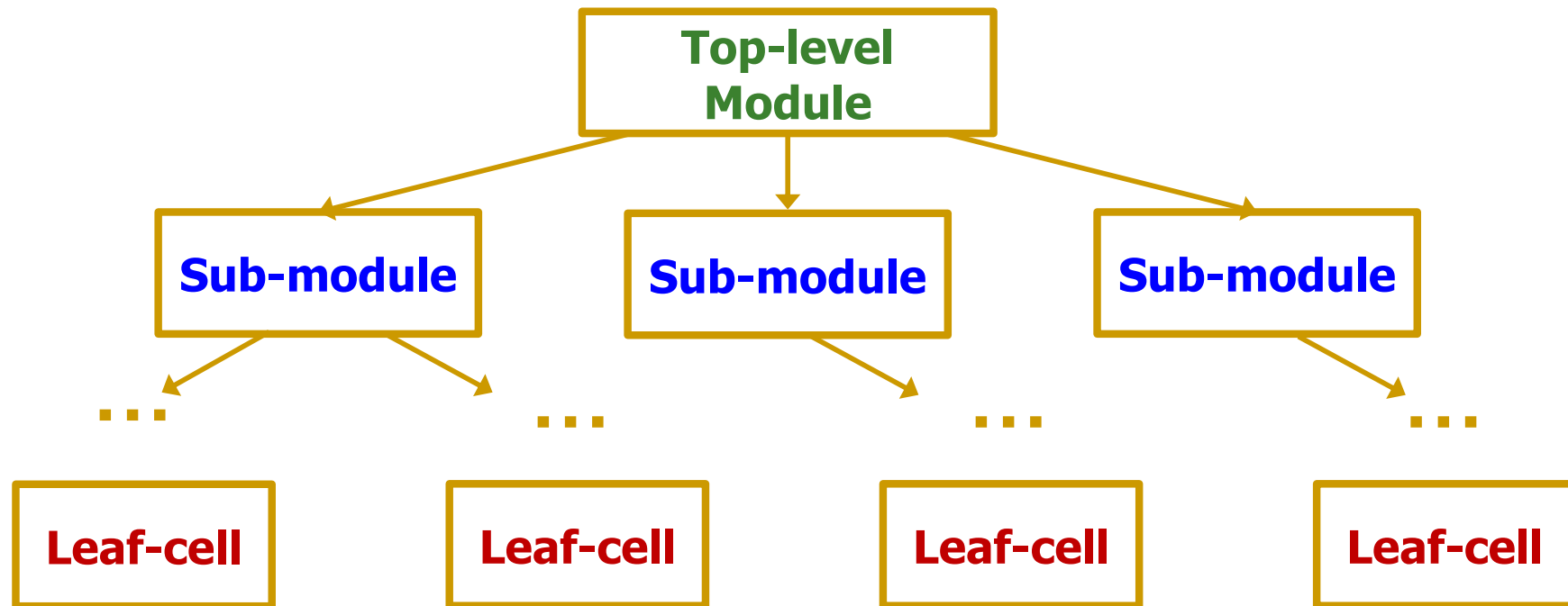
# Top-Down Design Methodology

---

- We define the **top-level module** and identify the **sub-modules** necessary to build the top-level module
- Subdivide the sub-modules until we come to **leaf cells**
  - **Leaf cell**: circuit components that cannot further be divided (e.g., *logic gates, cell libraries*)





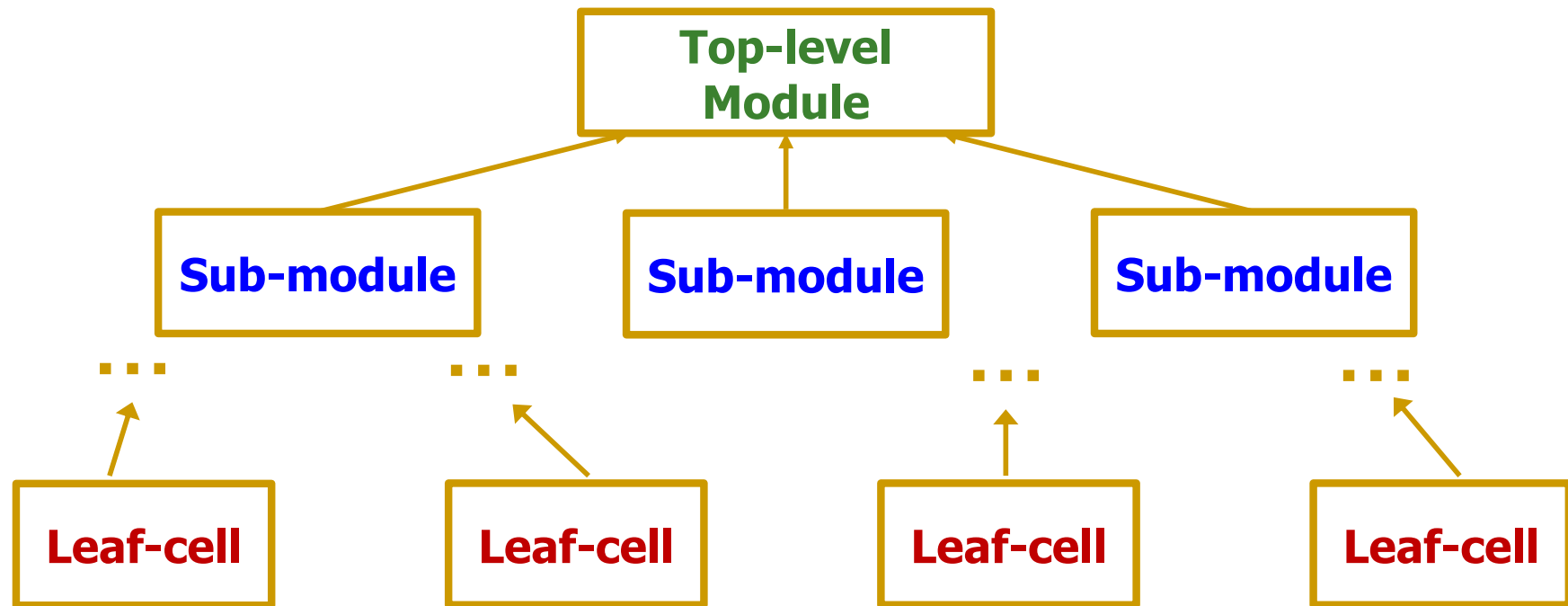
# Bottom-Up Design Methodology

---

- We first identify the **building blocks** that are available to us
- **Build bigger modules**, using these building blocks
- These modules are then used for higher-level modules until we build the **top-level module** in the design







 
# Defining a Module in Verilog

---

- A **module** is the main building block in Verilog
- We first need to define:
  - **Name** of the module
  - **Directions** of its **ports** (e.g., **input**, **output**)
  - **Names** of its **ports**
- Then:
  - Describe the **functionality** of the module



# Implementing a Module in Verilog

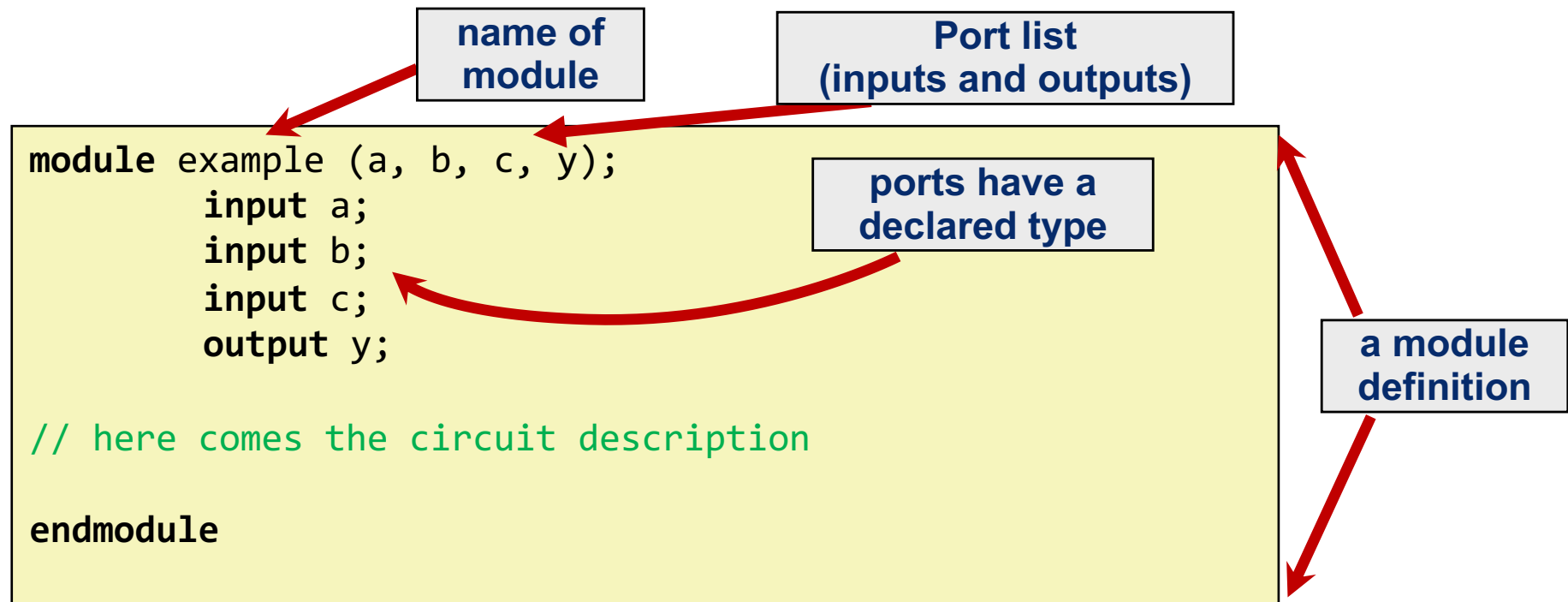 

# A Question of Style

---

- **The following two codes are functionally identical**

```
module test ( a, b, y );  
    input a;  
    input b;  
    output y;  
  
endmodule
```

```
module test ( input a,  
              input b,  
              output y );  
  
endmodule
```

port name and direction declaration  
can be combined

# What If We Have Multi-bit Input/Output?

---

- **You can also define multi-bit Input/Output (Bus)**

- [range\_end : range\_start]
- **Number of bits:** range\_end – range\_start + 1

- **Example:**

```
input  [31:0] a;    // a[31], a[30] .. a[0]
output [15:8] b1;  // b1[15], b1[14] .. b1[8]
output [7:0]  b2;  // b2[7], b2[6] .. b2[0]
input                c;  // single signal
```

- **a** represents a 32-bit value, so we prefer to define it as:  
[31:0] a
- It is preferred over [0:31] a which resembles *array* definition
- It is good practice to **be consistent** with the representation of multi-bit signals, i.e., always [31:0] or always [0:31]

# Manipulating Bits

---

- Bit Slicing
- Concatenation
- Duplication



# Basic Syntax

---

- Verilog is case sensitive
  - `SomeName` and `somename` are not the same!
- Names cannot start with numbers:
  - `2good` is not a valid name
- Whitespaces are ignored

```
// Single line comments start with a //  
  
/* Multiline comments  
   are defined like this */
```

# Two Main Styles of HDL Implementation

---

## ■ **Structural (Gate-Level)**

- ❑ The module body contains **gate-level description** of the circuit
- ❑ Describe how modules are interconnected
- ❑ Each module contains other modules (instances)
- ❑ ... and interconnections between these modules
- ❑ Describes a hierarchy

## ■ **Behavioral**

- ❑ The module body contains **functional description** of the circuit
- ❑ Contains logical and mathematical **operators**
- ❑ **Level of abstraction is higher than gate-level**
  - Many possible gate-level realizations of a behavioral description

## ■ **Practical circuits use a combination of both**


---

# Structural (Gate-Level) HDL



# Structural HDL: Instantiating a Module

---

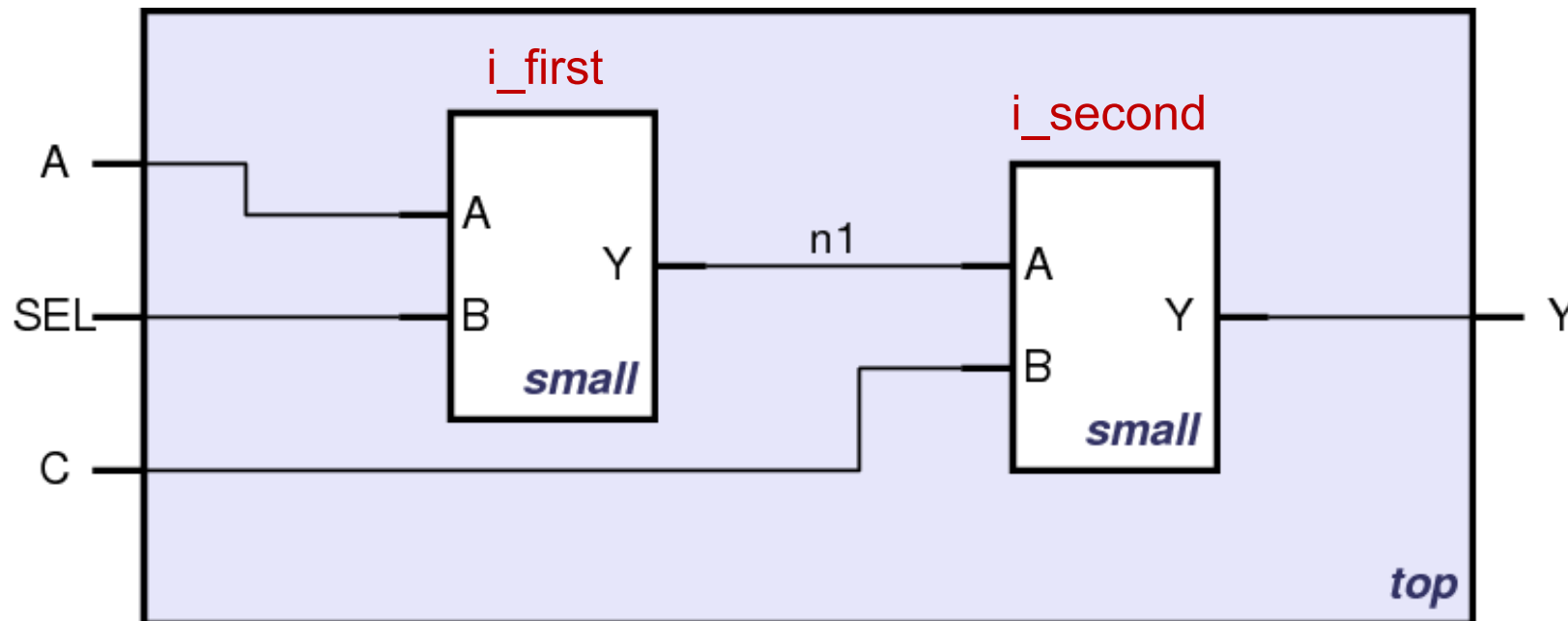


**Schematic of module "top" that is built from two instances of module "small"**

# Structural HDL Example

## ■ Module Definitions in Verilog

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```


```
endmodule
```

# Structural HDL Example

## ■ Defining wires (module interconnections)

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```

```
endmodule
```


# Structural HDL Example

- The first instantiation of the "small" module

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
// instantiate small once  
small i_first ( .A(A),  
                .B(SEL),  
                .Y(n1) );
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```

```
endmodule
```

# Structural HDL Example


## ■ The second instantiation of the “small” module

```
module top (A, SEL, C, Y);
  input A, SEL, C;
  output Y;
  wire n1;

  // instantiate small once
  small i_first ( .A(A),
                 .B(SEL),
                 .Y(n1) );

  // instantiate small second time
  small i_second ( .A(n1),
                  .B(C),
                  .Y(Y) );

endmodule
```

 

```
module small (A, B, Y);
  input A;
  input B;
  output Y;

  // description of small

endmodule
```

# Structural HDL Example

## ■ Short form of module instantiation


```
module top (A, SEL, C, Y);
  input A, SEL, C;
  output Y;
  wire n1;

  // alternative
  small i_first ( A, SEL, n1 );

  /* Shorter instantiation,
     pin order very important */

  // any pin order, safer choice
  small i_second ( .B(C),
                  .Y(Y),
                  .A(n1) );

endmodule
```

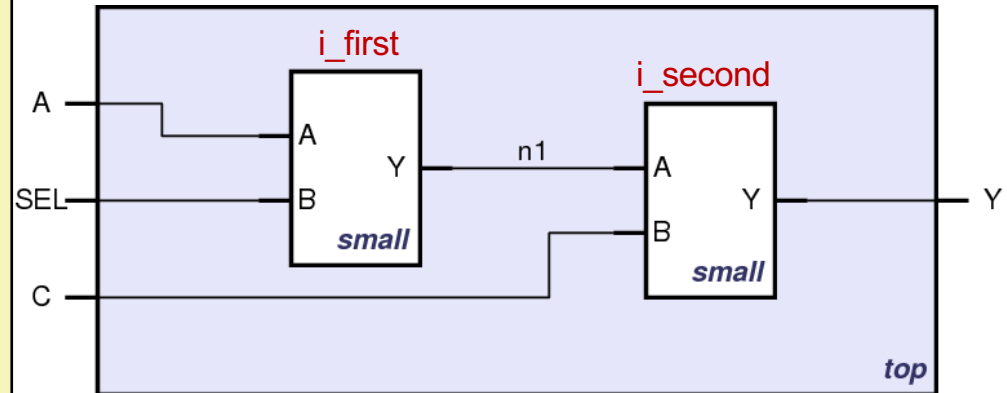

```
module small (A, B, Y);
  input A;
  input B;
  output Y;

  // description of small

endmodule
```

**Short form is not good practice  
as it reduces code maintainability**

# Structural HDL Example 2

---

- Verilog supports basic logic gates as predefined *primitives*
  - These primitives are **instantiated** like modules except that they are predefined in Verilog and *do not need a module definition*

```
module mux2(input d0, d1,
            input s,
            output y);
    wire ns, y1, y2;

    not    g1 (ns, s);
    and    g2 (y1, d0, ns);
    and    g3 (y2, d1, s);
    or     g4 (y, y1, y2);

endmodule
```

# Behavioral HDL



# Recall: Two Main Styles of HDL Implementation

---

## ■ **Structural (Gate-Level)**

- ❑ The module body contains **gate-level description** of the circuit
- ❑ Describe how modules are interconnected
- ❑ Each module contains other modules (instances)
- ❑ ... and interconnections between these modules
- ❑ Describes a hierarchy

## ■ **Behavioral**

- ❑ The module body contains **functional description** of the circuit
- ❑ Contains logical and mathematical **operators**
- ❑ **Level of abstraction is higher than gate-level**
  - Many possible gate-level realizations of a behavioral description

## ■ **Practical circuits would use a combination of both**

---

# Behavioral HDL: Defining Functionality


---

```
module example (a, b, c, y);  
    input a;  
    input b;  
    input c;  
    output y;  
  
    // here comes the circuit description  
    assign y = ~a & ~b & ~c |  
              a & ~b & ~c |  
              a & ~b & c;  
  
endmodule
```

# Behavioral HDL: Schematic View

---

 **A behavioral implementation still models a hardware circuit!**



# Bitwise Operators in Behavioral Verilog

---

```
module gates(input [3:0] a, b,
             output [3:0] y1, y2, y3, y4, y5);


    /* Five different two-input logic
       gates acting on 4 bit buses */

    assign y1 = a & b;      // AND
    assign y2 = a | b;      // OR
    assign y3 = a ^ b;      // XOR
    assign y4 = ~(a & b);  // NAND
    assign y5 = ~(a | b);  // NOR

endmodule
```

# Bitwise Operators: Schematic View

---

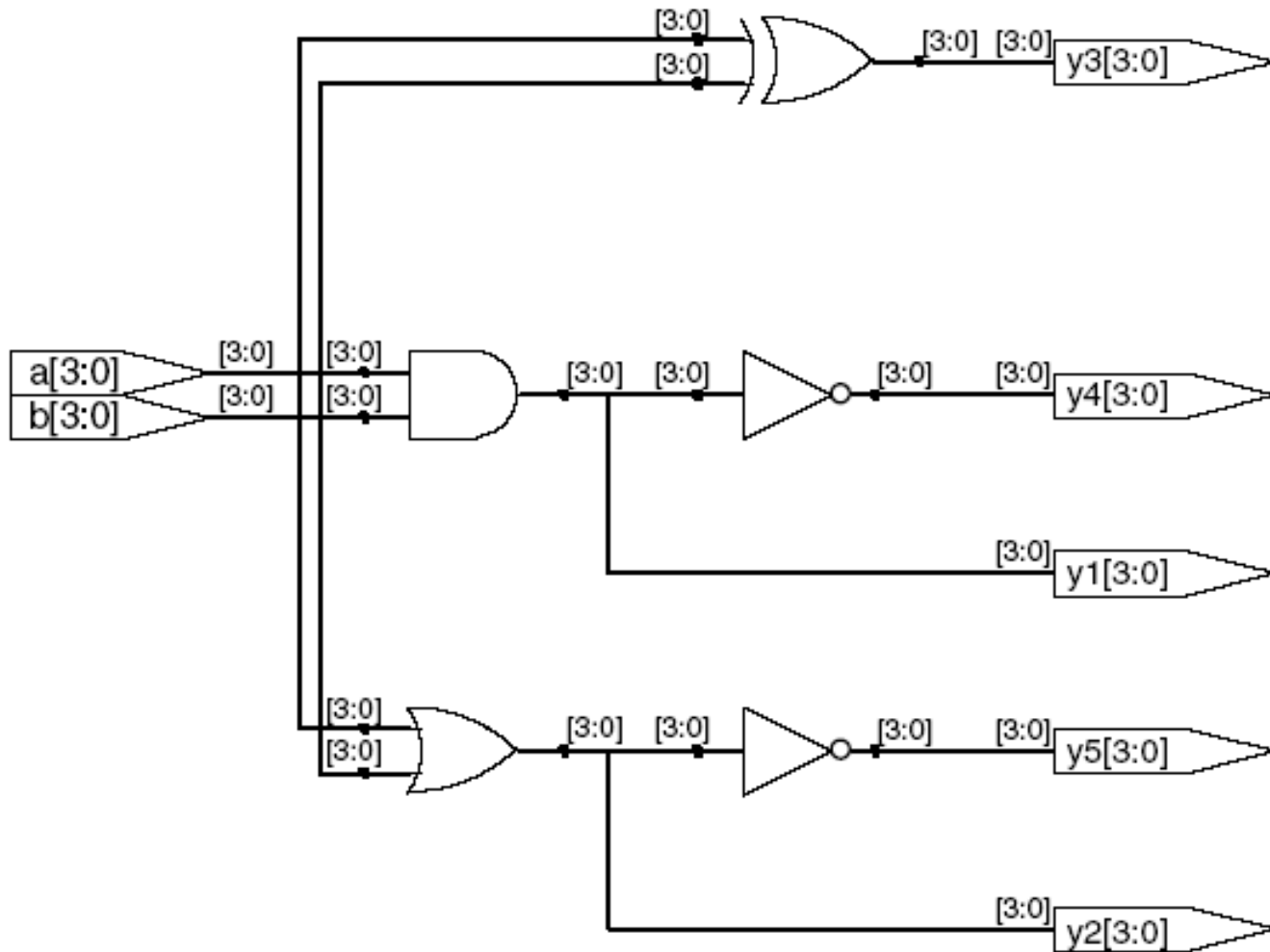

# Reduction Operators in Behavioral Verilog

---

```
module and8(input [7:0] a,
            output      y);


    assign y = &a;

    // &a is much easier to write than
    // assign y = a[7] & a[6] & a[5] & a[4] &
    //           a[3] & a[2] & a[1] & a[0];

endmodule
```

# Reduction Operators: Schematic View

---

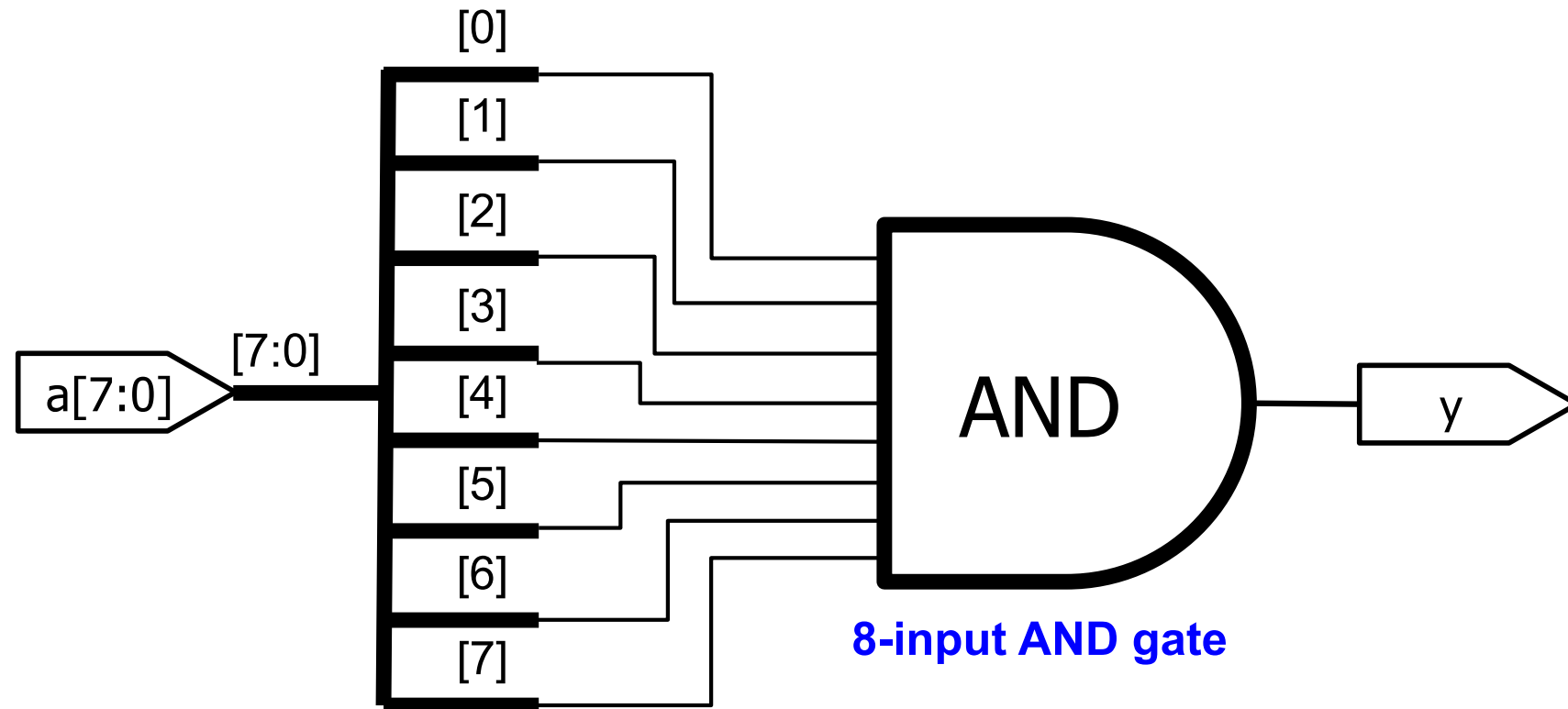

# Conditional Assignment in Behavioral Verilog

---


```
module mux2(input [3:0] d0, d1,  
            input      s,  
            output [3:0] y);  
  
    assign y = s ? d1 : d0;  
    // if (s) then y=d1 else y=d0;  
  
endmodule
```

- ? : is also called a **ternary operator** as it operates on three inputs:
  - s
  - d1
  - d0



# Conditional Assignment: Schematic View

---

 

# More Complex Conditional Assignments

---

```
module mux4(input [3:0] d0, d1, d2, d3
            input [1:0] s,
            output [3:0] y);

    assign y = s[1] ? ( s[0] ? d3 : d2)
              : ( s[0] ? d1 : d0);

    // if (s1) then
    //     if (s0) then y=d3 else y=d2
    // else
    //     if (s0) then y=d1 else y=d0

endmodule
```

# Even More Complex Conditional Assignments

---

```
module mux4(input [3:0] d0, d1, d2, d3
            input [1:0] s,
            output [3:0] y);

    assign y = (s == 2'b11) ? d3 :
               (s == 2'b10) ? d2 :
               (s == 2'b01) ? d1 :
               d0;

// if      (s = "11" ) then y= d3
// else if (s = "10" ) then y= d2
// else if (s = "01" ) then y= d1
// else                    y= d0

endmodule
```

# Precedence of Operations in Verilog

---

**Highest**

~	NOT
*, /, %	mult, div, mod
+, -	add, sub
<<, >>	shift
<<<, >>>	arithmetic shift
<, <=, >, >=	comparison
==, !=	equal, not equal
&, ~&	AND, NAND
^, ~^	XOR, XNOR
, ~	OR, NOR
?:	ternary operator

**Lowest**

# How to Express Numbers ?

---


**N'** **B****xx**

**8'** **b****0000\_0001**

- **(N) Number of bits**
  - Expresses how many bits will be used to store the value
- **(B) Base**
  - Can be b (binary), h (hexadecimal), d (decimal), o (octal)
- **(xx) Number**
  - The value expressed in base
  - Can also have X (invalid) and Z (floating), as values
  - Underscore \_ can be used to improve readability

# Number Representation in Verilog


---

Verilog	Stored Number	Verilog	Stored Number
4'b1001	1001	4'd5	0101
8'b1001	0000 1001	12'hFA3	1111 1010 0011
8'b0000_1001	0000 1001	8'o12	00 001 010
8'bxX0X1zZ1	XX0X 1ZZ1	4'h7	0111
'b01	0000 .. 0001  <b>32 bits (default)</b>	12'h0	0000 0000 0000
 
# Reminder: Floating Signals (Z)

- **Floating signal:** Signal that is not driven by any circuit
  - Open circuit, floating wire
- Also known as: **high impedance, hi-Z, tri-stated** signals


```
module tristate_buffer(input [3:0] a,  
                      input      en,  
                      output [3:0] y);  
  
    assign y = en ? a : 4'bz;  
  
endmodule
```


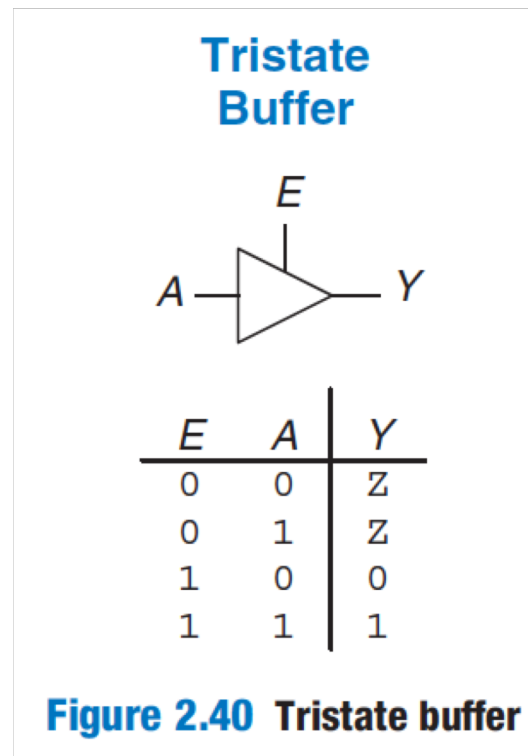
# Recall: Tri-State Buffer

---

- A tri-state buffer enables gating of different signals onto a wire






# Recall: Example Use of Tri-State Buffers

---

- Imagine a wire connecting the CPU and memory
  - At any time only the CPU or the memory can place a value on the wire, both not both
  - You can have two tri-state buffers: one driven by CPU, the other memory; and ensure at most one is enabled at any time

# Recall: Example Design with Tri-State Buffers

---

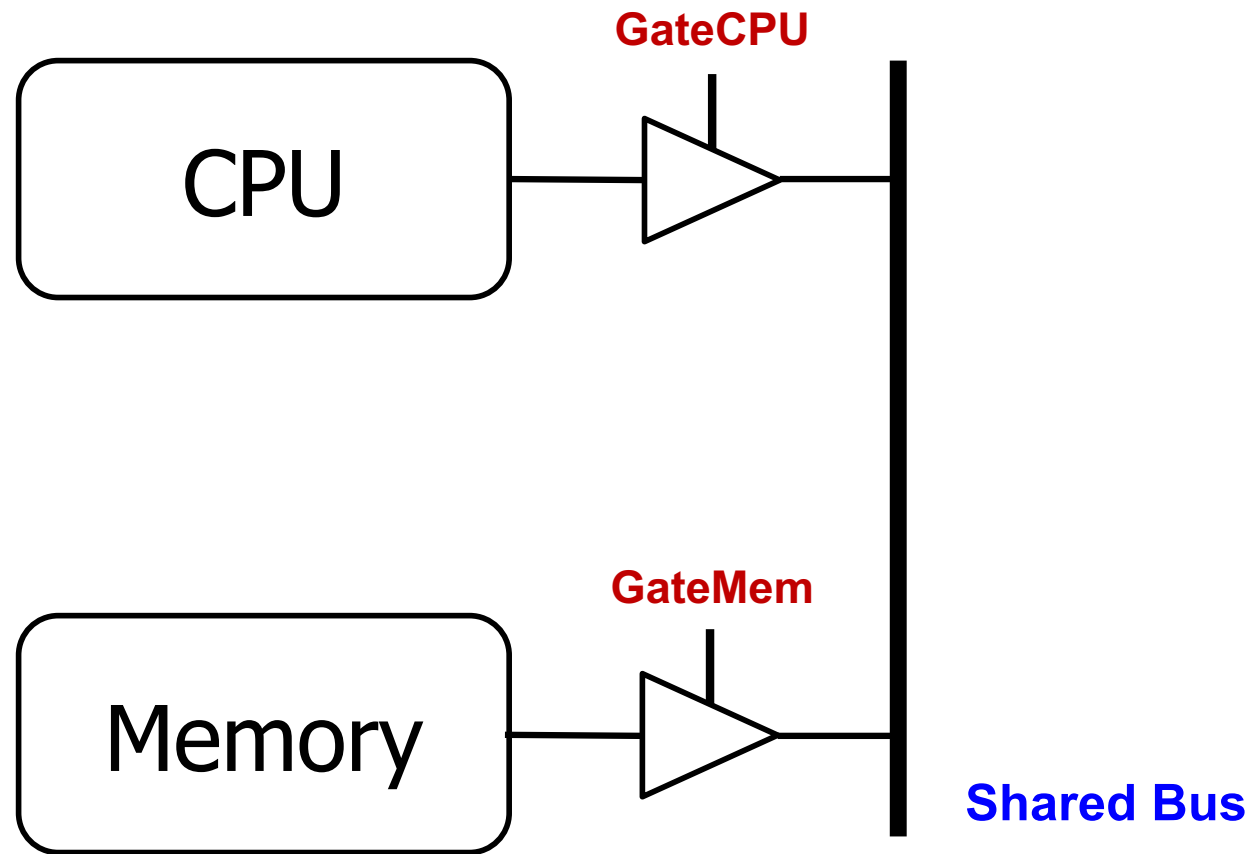

# Truth Table for AND with Z and X

---

<b>AND</b>		<b>A</b>			
		<b>0</b>	<b>1</b>	<b>Z</b>	<b>X</b>
<b>B</b>	<b>0</b>	0	0	0	0
	<b>1</b>	0	1	X	X
	<b>Z</b>	0	X	X	X
	<b>X</b>	0	X	X	X

# What Happens with HDL Code?

---

## ■ Synthesis

- ❑ Modern tools are able to **map synthesizable HDL code** into low-level *cell libraries* → *netlist describing gates and wires*
- ❑ They can perform many **optimizations**
- ❑ ... however they **can not guarantee** that a solution is optimal
  - Mainly due to **computationally expensive placement** and **routing** algorithms
- ❑ Most common way of Digital Design these days

## ■ Simulation

- ❑ Allows the behavior of the circuit to be **verified without actually manufacturing the circuit**
- ❑ Simulators can work on *structural* or *behavioral* HDL


# Recall This “example”

---



```
module example (a, b, c, y);  
    input a;  
    input b;  
    input c;  
    output y;  
  
    // here comes the circuit description  
    assign y = ~a & ~b & ~c |  
               a & ~b & ~c |  
               a & ~b & c;  
  
endmodule
```

# Synthesizing the “example”

---

 

# Simulating the “example”

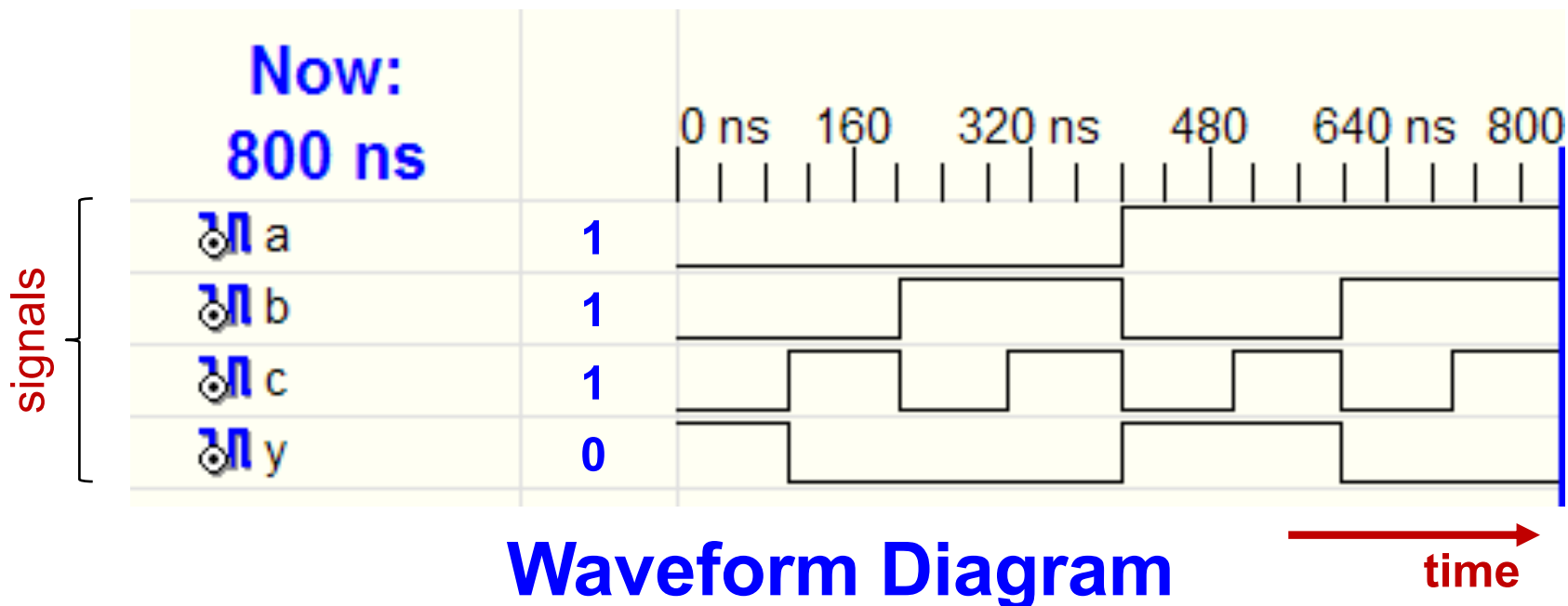 

# What We Have Seen So Far

---

- **Describing structural hierarchy with Verilog**
  - Instantiate modules in an other module
- **Describing functionality using behavioral modeling**
- **Writing simple logic equations**
  - We can write AND, OR, XOR, ...
- **Multiplexer functionality**
  - If ... then ... else
- **We can describe constants**
- **But there is more...**



# More Verilog Examples

---

- We can write Verilog code in **many different ways**
- Let's see how we can express the same functionality by developing Verilog code
  - At low-level
    - **Poor readability**
    - **More optimization** opportunities (especially for low-level tools)
  - At a higher-level of abstraction
    - **Better readability**
    - **Limited optimization** opportunities

# Comparing Two Numbers

---

- **Defining your own gates as new modules**
- We will use our gates to show the different ways of implementing a 4-bit comparator (equality checker)

## *An XNOR gate*

```
module MyXnor (input A, B,  
              output Z);  
  
    assign Z = ~(A ^ B); //not XOR  
  
endmodule
```

## *An AND gate*

```
module MyAnd (input A, B,  
            output Z);  
  
    assign Z = A & B;    // AND  
  
endmodule
```

# Gate-Level Implementation

---

```
module compare (input a0, a1, a2, a3, b0, b1, b2, b3,
                output eq);
    wire c0, c1, c2, c3, c01, c23;

    MyXnor i0 (.A(a0), .B(b0), .Z(c0) ); // XNOR
    MyXnor i1 (.A(a1), .B(b1), .Z(c1) ); // XNOR
    MyXnor i2 (.A(a2), .B(b2), .Z(c2) ); // XNOR
    MyXnor i3 (.A(a3), .B(b3), .Z(c3) ); // XNOR
    MyAnd haha (.A(c0), .B(c1), .Z(c01) ); // AND
    MyAnd hoho (.A(c2), .B(c3), .Z(c23) ); // AND
    MyAnd bubu (.A(c01), .B(c23), .Z(eq) ); // AND

endmodule
```

# Using Logical Operators

---

```
module compare (input a0, a1, a2, a3, b0, b1, b2, b3,
                output eq);
    wire c0, c1, c2, c3, c01, c23;

    MyXnor i0 (.A(a0), .B(b0), .Z(c0) ); // XNOR
    MyXnor i1 (.A(a1), .B(b1), .Z(c1) ); // XNOR
    MyXnor i2 (.A(a2), .B(b2), .Z(c2) ); // XNOR
    MyXnor i3 (.A(a3), .B(b3), .Z(c3) ); // XNOR
    assign c01 = c0 & c1;
    assign c23 = c2 & c3;
    assign eq  = c01 & c23;

endmodule
```

# Eliminating Intermediate Signals

---

```
module compare (input a0, a1, a2, a3, b0, b1, b2, b3,
                output eq);
    wire c0, c1, c2, c3;

    MyXnor i0 (.A(a0), .B(b0), .Z(c0) ); // XNOR
    MyXnor i1 (.A(a1), .B(b1), .Z(c1) ); // XNOR
    MyXnor i2 (.A(a2), .B(b2), .Z(c2) ); // XNOR
    MyXnor i3 (.A(a3), .B(b3), .Z(c3) ); // XNOR
    // assign c01 = c0 & c1;
    // assign c23 = c2 & c3;
    // assign eq  = c01 & c23;
    assign eq   = c0 & c1 & c2 & c3;

endmodule
```

# Multi-Bit Signals (Bus)

---

```
module compare (input [3:0] a, input [3:0] b,
                output eq);
    wire [3:0] c; // bus definition

    MyXnor i0 (.A(a[0]), .B(b[0]), .Z(c[0]) ); // XNOR
    MyXnor i1 (.A(a[1]), .B(b[1]), .Z(c[1]) ); // XNOR
    MyXnor i2 (.A(a[2]), .B(b[2]), .Z(c[2]) ); // XNOR
    MyXnor i3 (.A(a[3]), .B(b[3]), .Z(c[3]) ); // XNOR

    assign eq = &c; // short format

endmodule
```

# Bitwise Operations

---

```
module compare (input [3:0] a, input [3:0] b,
                output eq);
    wire [3:0] c; // bus definition

    // MyXnor i0 (.A(a[0]), .B(b[0]), .Z(c[0]) );
    // MyXnor i1 (.A(a[1]), .B(b[1]), .Z(c[1]) );
    // MyXnor i2 (.A(a[2]), .B(b[2]), .Z(c[2]) );
    // MyXnor i3 (.A(a[3]), .B(b[3]), .Z(c[3]) );

    assign c = ~(a ^ b); // XNOR

    assign eq = &c; // short format

endmodule
```

# Highest Abstraction Level: Comparing Two Numbers

---

```
module compare (input [3:0] a, input [3:0] b,  
               output eq);  
  
// assign c = ~(a ^ b); // XNOR  
  
// assign eq = &c; // short format  
  
assign eq = (a == b) ? 1 : 0; // really short  
  
endmodule
```



# Writing More Reusable Verilog Code

---

- We have a module that can compare two 4-bit numbers
- What if in the overall design we need to compare:
  - **5**-bit numbers?
  - **6**-bit numbers?
  - ...
  - **N**-bit numbers?
  - **Writing code for each case looks tedious**
- What could be a better way?

# Parameterized Modules

---

In Verilog, we can define **module parameters**

```
module mux2
  #(parameter width = 8) // name and default value
  (input [width-1:0] d0, d1,
   input                s,
   output [width-1:0] y);

  assign y = s ? d1 : d0;
endmodule
```

We can set the parameters to different values  
when instantiating the module

# Instantiating Parameterized Modules

---

```
module mux2
  #(parameter width = 8) // name and default value
  (input [width-1:0] d0, d1,
   input          s,
   output [width-1:0] y);

  assign y = s ? d1 : d0;
endmodule
```

# What About Timing?

---

- It is possible to define *timing relations* in Verilog. **BUT:**
  - These are **ONLY** for simulation
  - They **CAN NOT** be synthesized
  - They are used for *modeling delays* in a circuit

```
'timescale 1ns/1ps
module simple (input a, output z1, z2);

assign #5 z1 = ~a; // inverted output after 5ns
assign #9 z2 = a;  // output after 9ns

endmodule
```

**More to come later today!**

# Good Practices

---

- Develop/use a **consistent** naming style
- Use **MSB to LSB ordering** for buses
  - Use “**a[31:0]**”, **not** “**a[0:31]**”
- Define **one module per file**
  - Makes managing your design hierarchy easier
- Use a file name that equals module name
  - e.g., module **TryThis** is defined in a file called **TryThis.v**
- Always keep in mind that **Verilog describes hardware**

# Summary (HDL for Combinational Logic)


---

- We have seen an overview of Verilog
- Discussed structural and behavioral modeling
- Showed combinational logic constructs

# Implementing Sequential Logic Using Verilog

# Combinational + Memory = Sequential

---

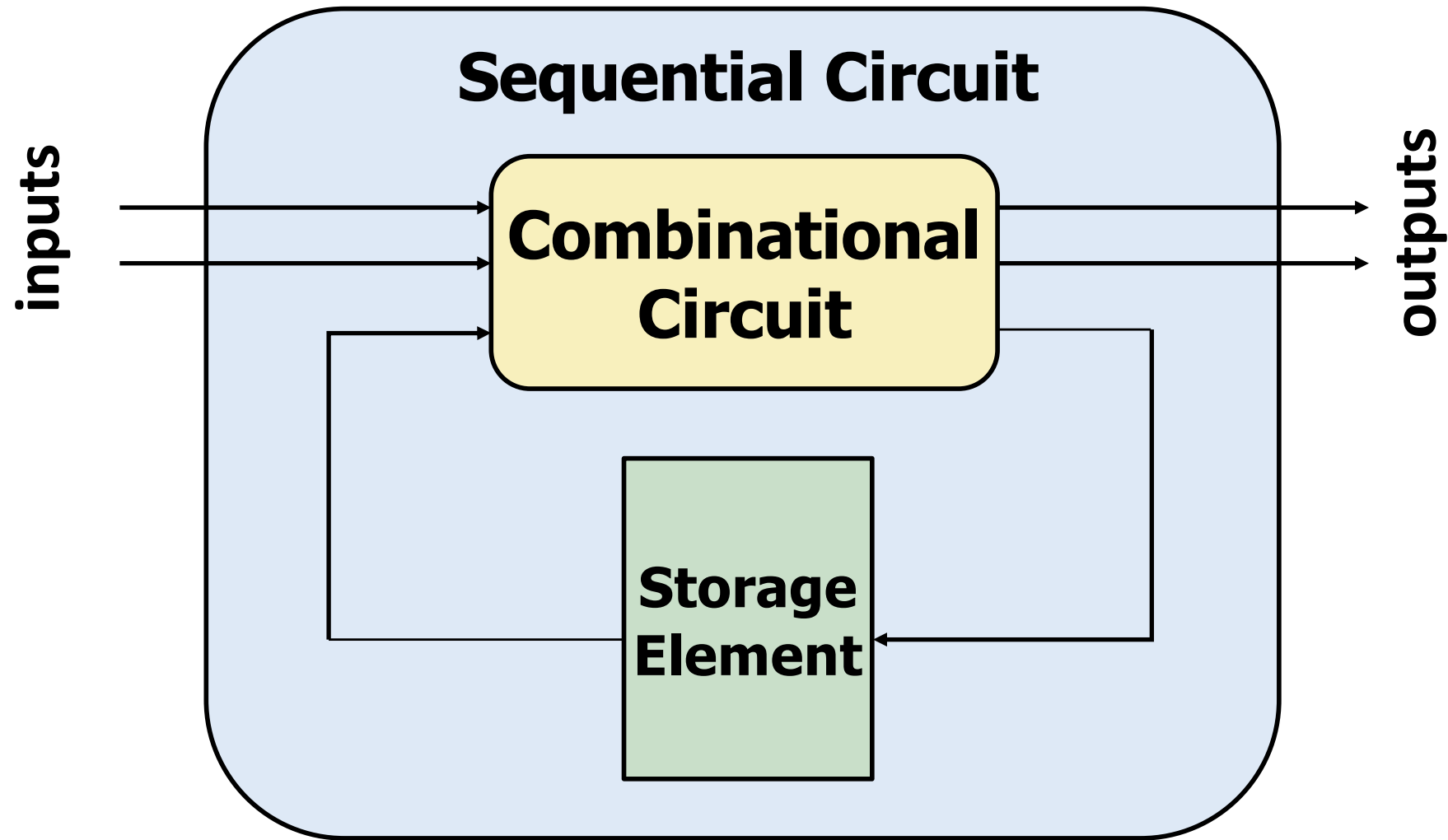



# Sequential Logic in Verilog

---

- Define blocks that have memory
  - *Flip-Flops, Latches, Finite State Machines*
- Sequential Logic state transition is triggered by a "CLOCK" signal
  - Latches are sensitive to level of the signal
  - Flip-flops are sensitive to the transitioning of signal
- Combinational constructs are **not** sufficient
  - We need **new constructs**:
    - **always**
    - **posedge/negedge**

# The “always” Block

---

```
always @ (sensitivity list)
    statement;
```

Whenever the event in the **sensitivity list** occurs,  
the statement is **executed**

# Example: D Flip-Flop

---

```
module flop(input          clk,
            input    [3:0] d,
            output reg [3:0] q);

    always @ (posedge clk)
        q <- d; // pronounced "q gets d"

endmodule
```

- **posedge** defines a rising edge (transition from 0 to 1).
- Statement executed when the **clk signal rises (posedge of clk)**
- Once the clk signal rises: the value of **d** is copied to **q**

# Example: D Flip-Flop

---

```
module flop(input          clk,
            input    [3:0] d,
            output reg [3:0] q);

    always @ (posedge clk)
        q <= d;           // pronounced "q gets d"

endmodule
```

- **assign** statement is **not** used within an always block
- **<=** describes a **non-blocking** assignment
  - We will see the difference between **blocking assignment** and **non-blocking** assignment soon

# Example: D Flip-Flop

---

```
module flop(input          clk,
            input          [3:0] d,
            output reg [3:0] q);

    always @ (posedge clk)
        q <= d;                // pronounced "q gets d"

endmodule
```

- Assigned variables need to be declared as **reg**
- The name **reg** does not necessarily mean that the value is a register (It could be, but it does not have to be)
- We will see examples later

# Asynchronous and Synchronous Reset

---

- **Reset** signals are used to **initialize** the hardware to a known state
  - Usually activated **at system start** (on power up)
- **Asynchronous Reset**
  - The reset signal is sampled **independent** of the clock
  - Reset gets the highest priority
  - Sensitive to **glitches**, may have **metastability** issues
    - Will be discussed in Lecture 8
- **Synchronous Reset**
  - The reset signal is sampled **with respect to the clock**
  - The reset **should be active long enough** to get sampled at the clock edge
  - Results in **completely synchronous circuit**

# D Flip-Flop with Asynchronous Reset

---

```
module flop_ar (input          clk,
                input          reset,
                input    [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk, negedge reset)
        begin
            if (reset == 0) q <= 0;    // when reset
            else            q <= d;    // when clk
        end
    endmodule
```

- In this example: two events can trigger the process:
  - A **rising edge** on clk
  - A **falling edge** on reset

# D Flip-Flop with Asynchronous Reset

---

```
module flop_ar (input          clk,
                input          reset,
                input    [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk, negedge reset)
    begin
        if (reset == 0) q <= 0;    // when reset
        else            q <= d;    // when clk
    end
endmodule
```

- For longer statements, a **begin-end** pair can be used
  - To improve readability
  - In this example, it was not necessary, but it is a good idea



# D Flip-Flop with Asynchronous Reset

---

```
module flop_ar (input          clk,
                input          reset,
                input    [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk, negedge reset)
    begin
        if (reset == 0) q <= 0; // when reset
        else             q <= d; // when clk
    end
endmodule
```

- First **reset** is checked: if **reset** is 0, **q** is set to 0.
  - This is an **asynchronous** reset as the reset can happen **independently** of the clock (on the negative edge of reset signal)
- If there is no reset, then regular assignment takes effect

# D Flip-Flop with Synchronous Reset

---

```
module flop_sr (input          clk,
                input          reset,
                input          [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk)
        begin
            if (reset == '0') q <= 0;    // when reset
            else                q <= d;    // when clk
        end
    endmodule
```

- The process is sensitive to only clock
  - Reset *happens only* when the *clock rises*. This is a *synchronous* reset

# D Flip-Flop with Enable and Reset

---

```
module flop_en_ar (input          clk,
                  input          reset,
                  input          en,
                  input [3:0] d,
                  output reg [3:0] q);

  always @ (posedge clk, negedge reset)
  begin
    if (reset == '0') q <= 0;    // when reset
    else if (en)      q <= d;    // when en AND clk
  end
endmodule
```

- A flip-flop with **enable** and **reset**
  - Note that the **en** signal is **not** in the *sensitivity list*
- **q** gets **d** only when **clk** is rising **and en** is **1**

# Example: D Latch

---

```
module latch (input          clk,
              input          [3:0] d,
              output reg [3:0] q);

    always @ (clk, d)
        if (clk) q <= d;           // latch is transparent when
                                   // clock is 1

endmodule
```

# Summary: Sequential Statements So Far

---

- Sequential statements are within an `always` block
- The sequential block is triggered with a change in the `sensitivity list`
- Signals assigned within an **`always`** must be declared as `reg`
- We use `<=` for (non-blocking) assignments and do not use `assign` within the `always` block.

# Basics of `always` Blocks

---

```
module example (input          clk,
                input    [3:0] d,
                output reg [3:0] q);

    wire [3:0] normal;           // standard wire
    reg  [3:0] special;          // assigned in always

    always @ (posedge clk)
        special <= d;           // first FF array

    assign normal = ~ special; // simple assignment

    always @ (posedge clk)
        q <= normal;           // second FF array
endmodule
```

You can have as many `always` blocks as needed

Assignment to the same signal in different `always` blocks is not allowed!

# Why Does an **always** Block Remember?

---

```
module flop (input          clk,
             input    [3:0] d,
             output reg [3:0] q);

    always @ (posedge clk)
        begin
            q <= d;    // when clk rises copy d to q
        end
endmodule
```

- This statement describes what happens to signal **q**
- ... but what happens when the clock is not rising?
- The value of **q** is preserved (remembered)

# An `always` Block Does **NOT** Always Remember

---

```
module comb (input          inv,
             input    [3:0] data,
             output reg [3:0] result);

    always @ (inv, data)          // trigger with inv, data
        if (inv) result <= ~data; // result is inverted data
        else    result <= data;  // result is data

endmodule
```

- This statement describes what happens to signal `result`
  - When `inv` is 1, `result` is `~data`
  - When `inv` is not 1, `result` is `data`
- The circuit is combinational (no memory)
  - `result` is assigned a value in all cases of the `if .. else` block, always



# always Blocks for Combinational Circuits

---

- An **always** block defines **combinational logic** if:
  - All outputs are always (**continuously**) updated
    1. All right-hand side signals are in the sensitivity list
      - You can use `always @*` for short
    2. All left-hand side signals get assigned in every possible condition of `if .. else` and `case` blocks
- It is easy to make mistakes and **unintentionally describe memorizing elements** (latches)
  - **Vivado** will most likely warn you. Make sure you check the warning messages
- **Always** blocks allow powerful combinational logic statements
  - `if .. else`
  - `case`

# Sequential or Combinational?

---

```
wire enable, data;
reg out_a, out_b;

always @ (*) begin
    out_a = 1'b0;
    if(enable) begin
        out_a = data;
        out_b = data;
    end
end
```

*No assignment for ~enable*

**Sequential**

```
wire enable, data;
reg out_a, out_b;

always @ (data) begin
    out_a = 1'b0;
    out_b = 1'b0;
    if(enable) begin
        out_a = data;
        out_b = data;
    end
end
```

*Not in the sensitivity list*

**Sequential**

# The `always` Block is **NOT** Always Practical/Nice

---

```
reg [31:0] result;
wire [31:0] a, b, comb;
wire      sel,

always @ (a, b, sel) // trigger with a, b, sel
    if (sel) result <= a; // result is a
    else    result <= b; // result is b

assign comb = sel ? a : b;
```

- Both statements describe the **same** multiplexer
- In this case, the `always` block is more work

# always Block for Case Statements (Handy!)

---

```
module sevensegment (input      [3:0] data,
                    output reg [6:0] segments);

    always @ ( * )           // * is short for all signals
    case (data)              // case statement
        4'd0: segments = 7'b111_1110; // when data is 0
        4'd1: segments = 7'b011_0000; // when data is 1
        4'd2: segments = 7'b110_1101;
        4'd3: segments = 7'b111_1001;
        4'd4: segments = 7'b011_0011;
        4'd5: segments = 7'b101_1011;
        // etc etc
        default: segments = 7'b000_0000; // required
    endcase

endmodule
```

# Summary: `always` Block

---

- `if .. else` can only be used in `always` blocks
- The `always` block is **combinational** only if all `regs` within the block are always assigned to a signal
  - Use the `default` case to make sure you do not forget an unimplemented case, which may otherwise result in a latch
- Use `casex` statement to be able to check for don't cares

# Non-Blocking and Blocking Assignments

---

## Non-blocking (<=)

```
always @ (a)
begin
    a <= 2'b01;
    b <= a;
    // all assignments are made here
    // b is not (yet) 2'b01
end
```

- All assignments are made at the end of the block
- All assignments are made in parallel, process flow is **not-blocked**

## Blocking (=)

```
always @ (a)
begin
    a = 2'b01;
    // a is 2'b01
    b = a;
    // b is now 2'b01 as well
end
```

- Each assignment is made immediately
- Process waits until the first assignment is complete, it **blocks** progress

# Example: Blocking Assignment

---

- Assume all inputs are initially '0'

```
always @ ( * )
begin
  p    = a ^ b ;           // p    = 0  1
  g    = a & b ;           // g    = 0  0
  s    = p ^ cin ;        // s    = 0  1
  cout = g | (p & cin) ;  // cout = 0  0
end
```

- If **a** changes to '1'
  - All values are updated in order

# The Same Example: Non-Blocking Assignment

---

- Assume all inputs are initially '0'

```
always @ ( * )
begin
  p    <= a ^ b ;           // p    = 0  1
  g    <= a & b ;           // g    = 0  0
  s    <= p ^ cin ;        // s    = 0  0
  cout <= g | (p & cin) ;  // cout = 0  0
end
```

- If **a** changes to '1'
  - All assignments are concurrent
  - When **s** is being assigned, **p** is still 0



# The Same Example: Non-Blocking Assignment

---

- After the first iteration, **p** has changed to '1' as well

```
always @ ( * )
begin
  p    <= a ^ b ;           // p    = 1  1
  g    <= a & b ;           // g    = 0  0
  s    <= p ^ cin ;        // s    = 0  1
  cout <= g | (p & cin) ;  // cout = 0  0
end
```

- Since there is a change in **p**, the process **triggers again**
- This time **s** is calculated with **p=1**

# Rules for Signal Assignment

---

- Use `always @(posedge clk)` and `non-blocking` assignments (`<=`) to model `synchronous sequential logic`

```
always @ (posedge clk)
    q <= d; // non-blocking
```


- Use continuous assignments (`assign`) to model simple combinational logic.

```
assign y = a & b;
```

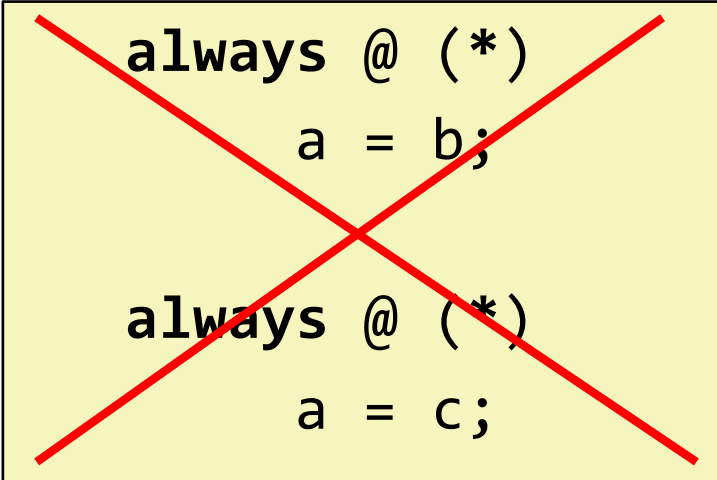
# Rules for Signal Assignment (Cont.)

---

- Use **always @ (\*)** and **blocking** assignments (=) to model more **complicated combinational logic**.
- You **cannot** make assignments to the **same** signal in more than one always block or in a *continuous assignment*


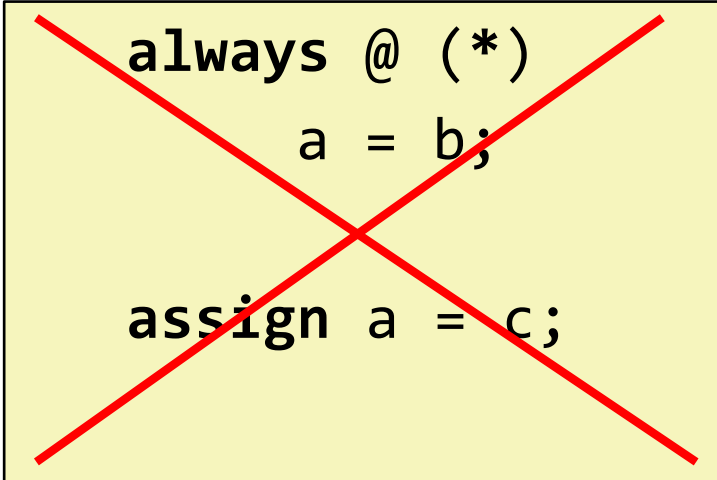
```
always @ (*)  
    a = b;  
  
always @ (*)  
    a = c;
```




```
always @ (*)  
    a = b;  
  
assign a = c;
```
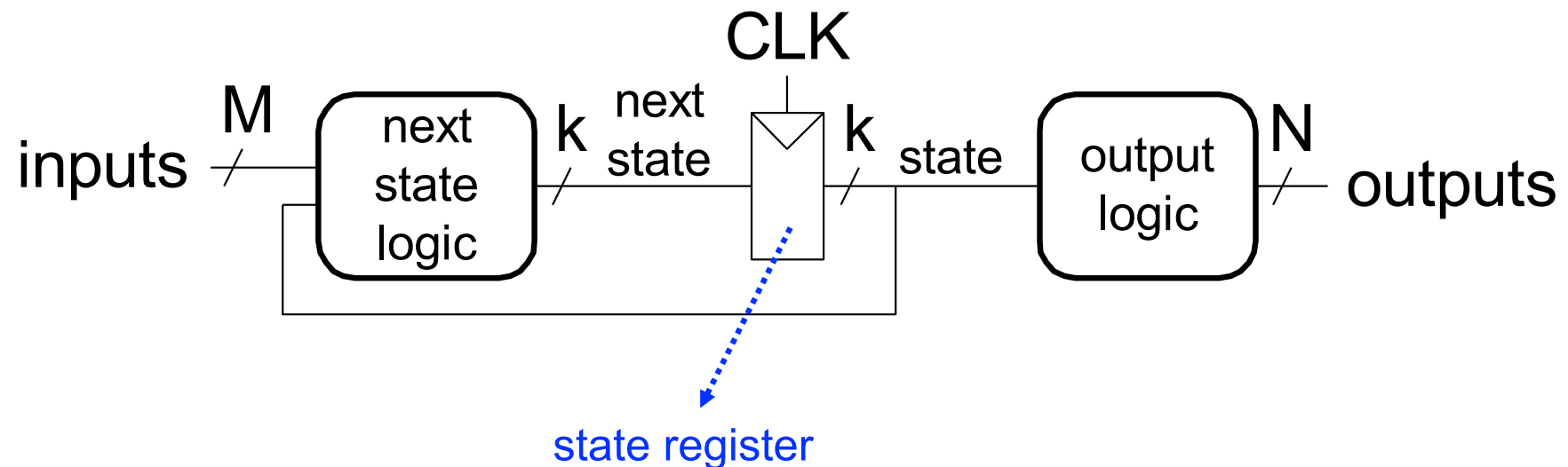
# Recall: Finite State Machines (FSMs)

---

- Each FSM consists of three separate parts:
  - next state logic
  - state register
  - output logic




# Recall: Finite State Machines (FSMs) Comprise

---


 
## ■ Sequential circuits

- State register(s)
  - Store the current state and
  - Load the next state at the clock edge



  
## ■ Combinational Circuits

- Next state logic
  - Determines what the next state will be
  
- Output logic
  - Generates the outputs




# FSM Example 1: Divide the Clock Frequency by 3

---

 

 The output *Y* is HIGH for **one clock cycle out of every 3**. In other words, the output **divides the frequency of the clock by 3**.



# Implementing FSM Example 1: Definitions

---



```
module divideby3FSM (input clk,
                    input reset,
                    output q);

    reg [1:0] state, nextstate;

    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b10;
```

- We define `state` and `nextstate` as 2-bit reg
- The parameter descriptions are `optional`, it makes reading easier
  
# Implementing FSM Example 1: State Register





```
// state register
always @ (posedge clk, posedge reset)
    if (reset) state <= S0;
    else      state <= nextstate;
```

- This part defines the **state register** (memorizing process)
- Sensitive to only **clk**, **reset**
- In this example, **reset** is active when it is '1' (active-high)




  
# Implementing FSM Example 1: Next State Logic



```
// next state logic
always @ (*)
  case (state)
    S0:      nextstate = S1;
    S1:      nextstate = S2;
    S2:      nextstate = S0;
    default: nextstate = S0;
  endcase
```
 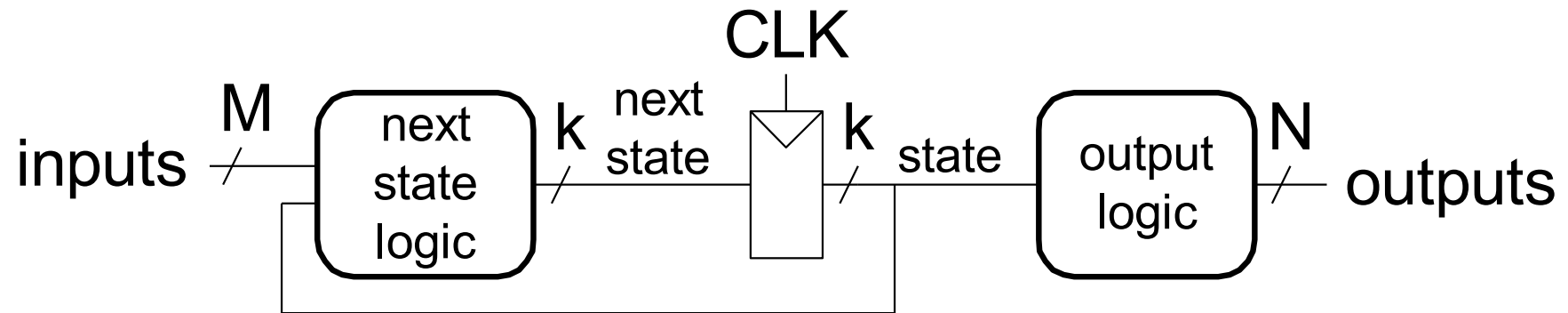
# Implementing FSM Example 1: Output Logic



```
// output logic  
assign q = (state == S0);
```

- In this example, output depends only on state
  - **Moore type FSM**

# Implementation of FSM Example 1

---

```
module divideby3FSM (input clk, input reset, output q);
    reg [1:0] state, nextstate;

    parameter S0 = 2'b00; parameter S1 = 2'b01; parameter S2 = 2'b10;

    always @ (posedge clk, posedge reset) // state register
        if (reset) state <= S0;
        else      state <= nextstate;

    always @ (*) // next state logic
        case (state)
            S0:      nextstate = S1;
            S1:      nextstate = S2;
            S2:      nextstate = S0;
            default: nextstate = S0;
        endcase
    assign q = (state == S0); // output logic
endmodule
```

# Design of Digital Circuits

## Lecture 7.2: Hardware Description Languages and Verilog

Prof. Onur Mutlu

ETH Zurich

Spring 2019


14 March 2019

We did not cover the following.  
They are for your preparation.


 
# Implementing FSM Example 2: Definitions

```
module SmilingSnail (input clk,  
                    input reset,  
                    input number,  
                    output smile);  
  
    reg [1:0] state, nextstate;  
  
    parameter S0 = 2'b00;  
    parameter S1 = 2'b01;  
    parameter S2 = 2'b10;  
    parameter S3 = 2'b11;
```



# Implementing FSM Example 2: State Register

---


```
// state register
always @ (posedge clk, posedge reset)
    if (reset) state <= S0;
    else      state <= nextstate;
```

- This part defines the **state register** (memorizing process)
- Sensitive to only **clk**, **reset**
- In this example **reset** is active when '1' (active-high)


 
# Implementing FSM Example 2: Next State Logic

```
// next state logic
always @ (*)
  case (state)
    S0: if (number) nextstate = S1;
        else nextstate = S0;
    S1: if (number) nextstate = S2;
        else nextstate = S0;
    S2: if (number) nextstate = S2;
        else nextstate = S3;
    S3: if (number) nextstate = S1;
        else nextstate = S0;
  default: nextstate = S0;
endcase
```



# Implementing FSM Example 2: Output Logic

---

```
// output logic
assign smile = (number & state == S3);
```

- In this example, output depends on state and input
  - **Mealy type FSM**
- We used a simple combinational assignment

# Implementation of FSM Example 2

```
module SmilingSnail (input clk,
                    input reset,
                    input number,
                    output smile);

    reg [1:0] state, nextstate;

    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b10;
    parameter S3 = 2'b11;

    // state register
    always @ (posedge clk, posedge
reset)
        if (reset) state <= S0;
        else      state <= nextstate;
```

```
always @ (*) // next state logic
    case (state)
        S0: if (number)
                nextstate = S1;
            else nextstate = S0;
        S1: if (number)
                nextstate = S2;
            else nextstate = S0;
        S2: if (number)
                nextstate = S2;
            else nextstate = S3;
        S3: if (number)
                nextstate = S1;
            else nextstate = S0;
        default: nextstate = S0;
    endcase
    // output logic
    assign smile = (number & state==S3);

endmodule
```

# What Did We Learn?

---

- Basics of defining **sequential circuits** in Verilog
- The **always** statement
  - Needed for defining memorizing elements (**flip-flops, latches**)
  - Can also be used to define **combinational circuits**
- **Blocking** vs **Non-blocking** statements
  - = assigns the value **immediately**
  - <= assigns the value **at the end of the block**
- Writing FSMs
  - Next state logic
  - State assignment
  - Output logic

**Next Lecture:**

Timing and Verification