

Digital Design & Computer Arch.

Lecture 7a: Sequential Logic Design II

Prof. Onur Mutlu

ETH Zürich

Spring 2020

12 March 2020

Agenda for This Week

■ Today

- Wrap up Sequential Logic
- Hardware Description Languages and Verilog
 - Combinational Logic
 - Sequential Logic

■ Tomorrow

- Timing and Verification

Agenda for Next Week

■ Thursday

- Von Neumann Model of Execution
- Instruction Set Architecture
 - LC-3 and MIPS

■ Friday

- ISA and Assembly Programming

Assignment: Required Lecture Video

- Why study computer architecture?
- Why is it important?
- **Future Computing Architectures**
- **Required Assignment**
 - **Watch** Prof. Mutlu's inaugural lecture at ETH and understand it
 - <https://www.youtube.com/watch?v=kgiZISOcGFM>
- **Optional Assignment – for 1% extra credit**
 - **Write a 1-page summary** of the lecture and email us
 - What are your key takeaways?
 - What did you learn?
 - What did you like or dislike?
 - Submit your summary to [Moodle](#) – Deadline: April 1

Extra Assignment: Moore's Law (I)

- **Paper review**
- G.E. Moore. "Cramming more components onto integrated circuits," Electronics magazine, 1965

- **Optional Assignment – for 1% extra credit**
 - **Write a 1-page review**
 - Upload PDF file to Moodle – Deadline: April 1

- I strongly recommend that you **follow my guidelines for (paper) review** (see next slide)

Extra Assignment: Moore's Law (II)

■ Guidelines on how to review papers critically

- **Guideline slides:** [pdf](#) [ppt](#)
- **Video:** <https://www.youtube.com/watch?v=tOL6FANAJ8c>

- Example reviews on "Main Memory Scaling: Challenges and Solution Directions" ([link to the paper](#))
 - [Review 1](#)
 - [Review 2](#)

- Example review on "Staged memory scheduling: Achieving high performance and scalability in heterogeneous systems" ([link to the paper](#))
 - [Review 1](#)

Required Readings (This Week)

- Hardware Description Languages and Verilog
 - H&H Chapter 4 in full

- Timing and Verification
 - H&H Chapters 2.9 and 3.5 + (start Chapter 5)

- By tomorrow, make sure you are done with
 - **P&P Chapters 1-3 + H&H Chapters 1-4**

Required Readings (Next Week)

- Von Neumann Model, LC-3, and MIPS
 - P&P, Chapters 4, 5
 - H&H, Chapter 6
 - P&P, Appendices A and C (ISA and microarchitecture of LC-3)
 - H&H, Appendix B (MIPS instructions)


- Programming
 - P&P, Chapter 6

- **Recommended:** Digital Building Blocks
 - H&H, Chapter 5


Wrap-Up Sequential Logic Circuits and Design

Finite State Machine: Schematic


FSM Schematic: State Register

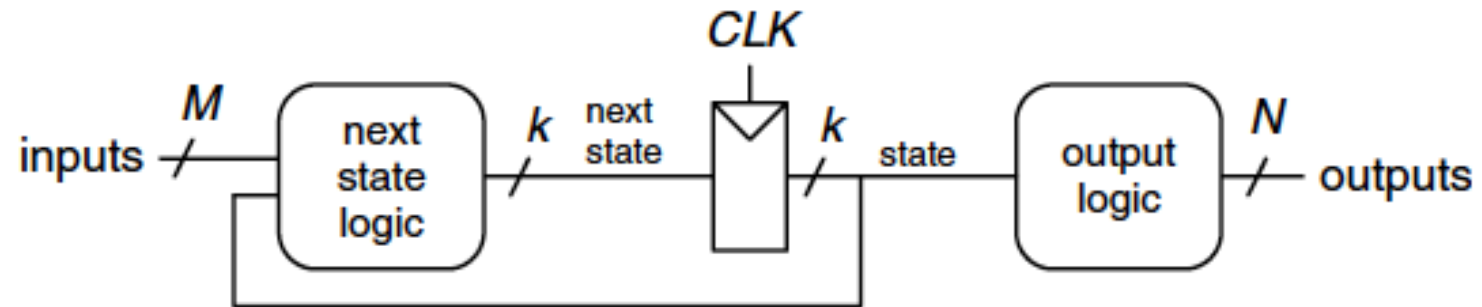

FSM Schematic: State Register

 


FSM Schematic: Next State Logic

 

$$S'_1 = S_1 \text{ xor } S_0$$


$$S'_0 = (\overline{S_1} \cdot \overline{S_0} \cdot \overline{T_A}) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B})$$

FSM Schematic: Output Logic

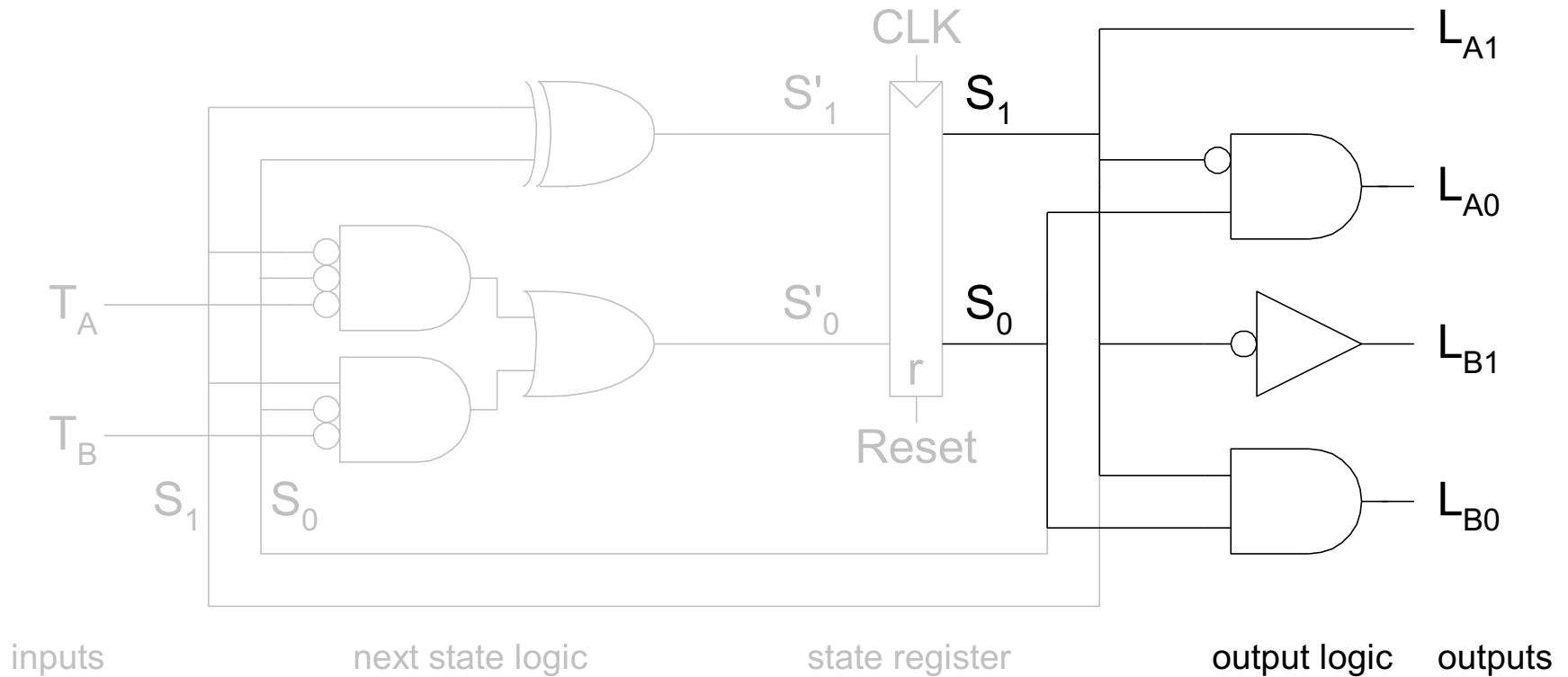

$$\begin{aligned}L_{A1} &= S_1 \\L_{A0} &= \overline{S_1} \cdot S_0 \\L_{B1} &= \overline{S_1} \\L_{B0} &= S_1 \cdot S_0\end{aligned}$$

FSM Timing Diagram

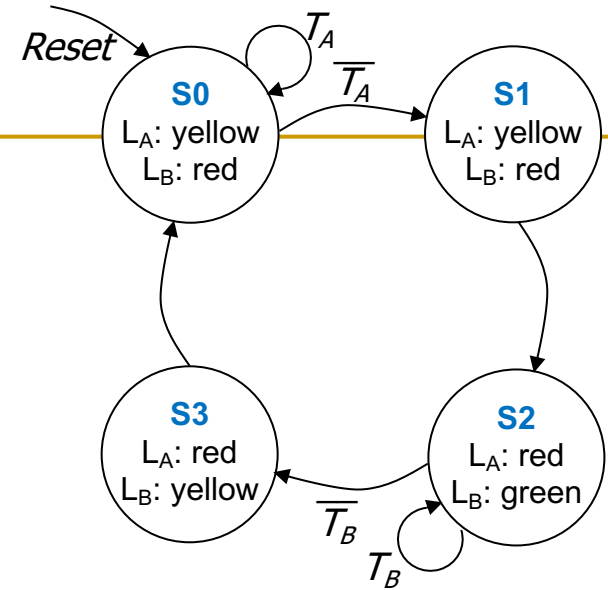

CLK_

Reset_

T_A _

T_B _



S' _

S_{1:0} _



L_{A:1:0} _

L_{B:1:0} _



FSM Timing Diagram

  



FSM Timing Diagram

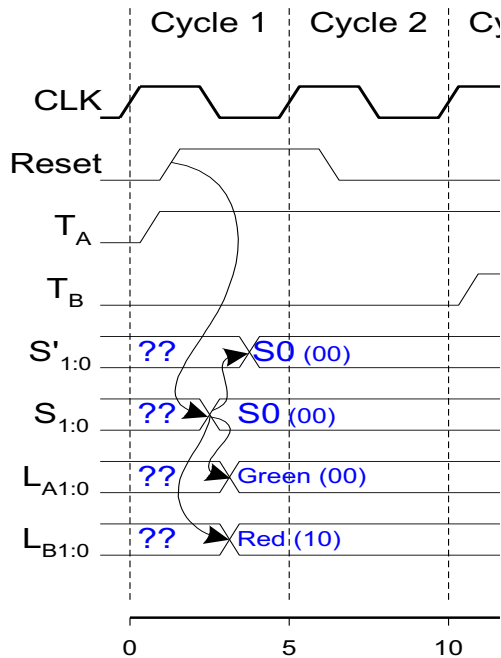 



FSM Timing Diagram

  



FSM Timing Diagram

  


FSM Timing Diagram

  


FSM Timing Diagram

  



FSM Timing Diagram

 

This is from H&H Section 3.4.1


 


FSM Timing Diagram

  

FSM Timing Diagram


See H&H Chapter 3.4

  

Finite State Machine: State Encoding

FSM State Encoding

 - How do we encode the state bits?
 - Three common state binary encodings with different tradeoffs
 1. **Fully Encoded**
 2. **1-Hot Encoded**
 3. **Output Encoded**
- Let's see an example **Swiss** traffic light with 4 states
 - Green, Yellow, Red, Yellow+Red



FSM State Encoding (II)

1. Binary Encoding (Full Encoding):

- Use the minimum number of bits used to encode all states
 - Use $\log_2(num_states)$ bits to represent the states
- *Example states:* 00, 01, 10, 11
- **Minimizes** # flip-flops, but not necessarily output logic or next state logic

2. One-Hot Encoding:

- Each bit encodes a different state
 - Uses num_states bits to represent the states
 - Exactly 1 bit is “hot” for a given state
- *Example states:* 0001, 0010, 0100, 1000
- **Simplest design process** – very automatable
- **Maximizes** # flip-flops, **minimizes** next state logic

FSM State Encoding (III)

3. Output Encoding:

- ❑ Outputs are **directly accessible** in the state encoding
- ❑ For example, since we have **3 outputs** (light color), encode state with **3 bits**, where each bit represents a color
- ❑ *Example states:* 001, 010, 100, 110
 - Bit₀ encodes **green** light output,
 - Bit₁ encodes **yellow** light output
 - Bit₂ encodes **red** light output
- ❑ **Minimizes** output logic
- ❑ Only works for Moore Machines (output function of state)

FSM State Encoding (III)

3. Output Encoding:

- Outputs are **directly accessible** in the state encoding

The **designer** must **carefully** choose an encoding scheme to **optimize** the design under given constraints


- **Minimizes** output logic
- Only works for Moore Machines (output function of state)

Moore vs. Mealy Machines


Recall: Moore vs. Mealy FSMs

- Next state is determined by the current state and the inputs
- Two types of finite state machines differ in the **output logic**:
 - **Moore FSM**: outputs depend only on the current state
 - **Mealy FSM**: outputs depend on the current state and the inputs

Moore FSM

 



Mealy FSM

 

Moore vs. Mealy FSM Examples


- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it.
- The snail smiles whenever the last four digits it has crawled over are **1101**.
- Design Moore and Mealy FSMs of the snail's brain.

Moore FSM

  


Moore vs. Mealy FSM Examples

 
- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it.
- The snail smiles whenever the last four digits it has crawled over are **1101**.
- Design Moore and Mealy FSMs of the snail's brain.



Moore FSM

 


Mealy FSM

 



State Transition Diagrams

Moore FSM

 

What are the tradeoffs?

Mealy FSM

  

FSM Design Procedure

- **Determine** all possible states of your machine
- **Develop** a **state transition diagram**
 - Generally this is done from a textual description
 - You need to 1) determine the **inputs** and **outputs** for each **state** and 2) figure out how to get from one state to another
- **Approach**
 - Start by defining the **reset state** and what happens from it – this is typically an easy point to start from
 - Then continue to add **transitions** and **states**
 - Picking **good state names** is very important
 - Building an FSM is **like** programming (but it *is not* programming!)
 - An FSM has a sequential “control-flow” like a program with conditionals and goto’s
 - The if-then-else construct is controlled by one or more inputs
 - The outputs are controlled by the state or the inputs
 - In hardware, we typically have many concurrent FSMs

What is to Come: LC-3 Processor


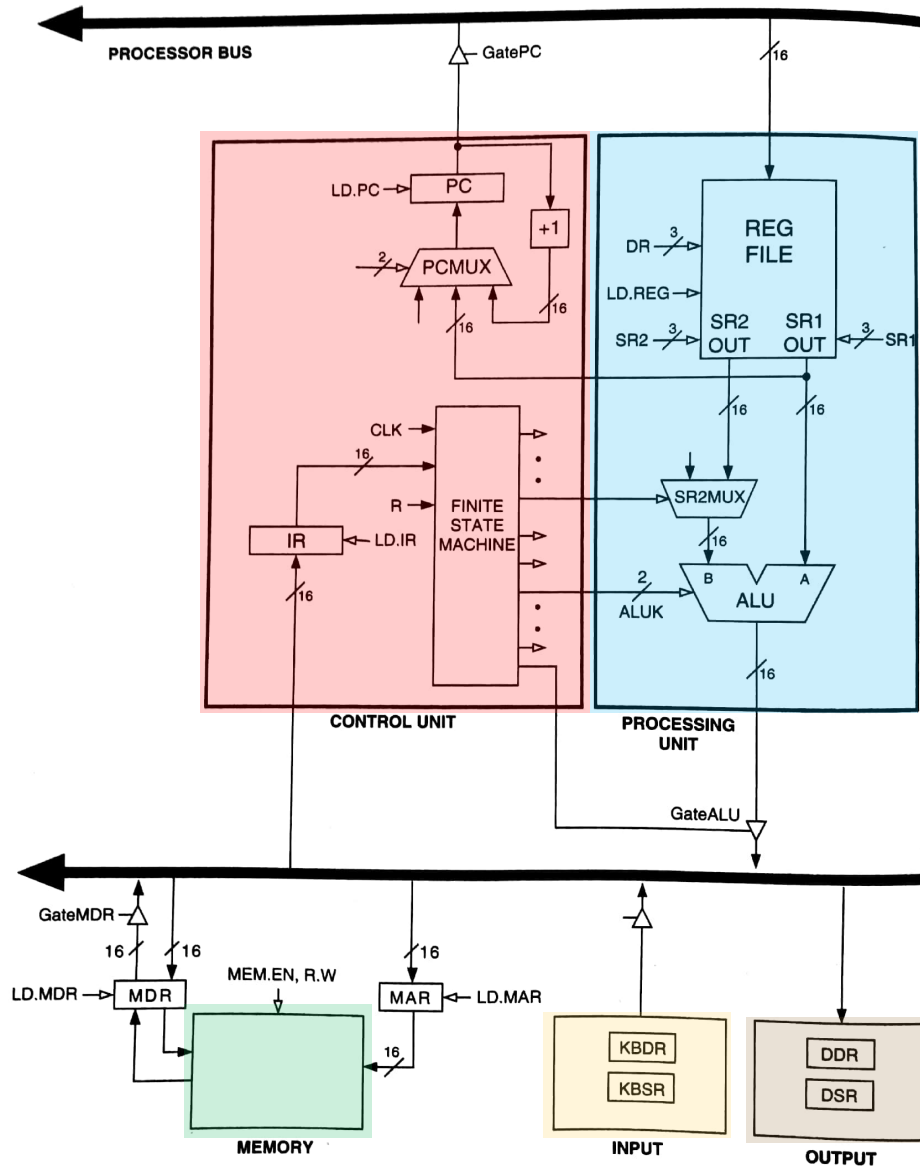


Figure 4.3 The LC-3 as an example of the von Neumann model

What is to Come: LC-3 Datapath

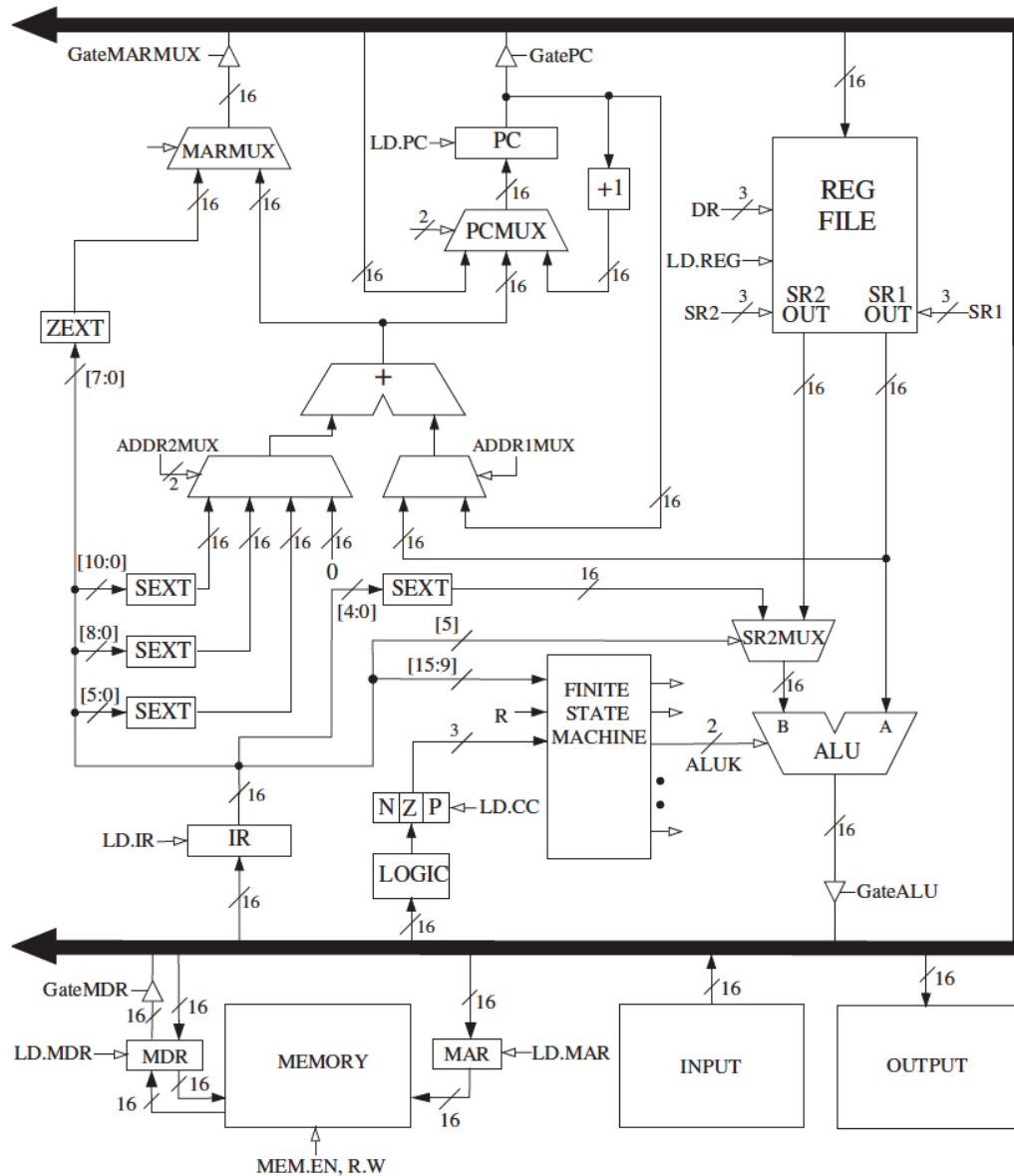

Digital Design & Computer Arch.

Lecture 7a: Sequential Logic Design II

Prof. Onur Mutlu

ETH Zürich

Spring 2020

12 March 2020