

# Digital Design & Computer Arch.

## Lab 1 Supplement: Drawing Basic Circuits

Prof. Onur Mutlu

ETH Zurich

Spring 2021

9 March 2021

# What We Will Learn?

---

- In Lab 1, you will **design simple combinatorial circuits**
- We will cover a tutorial about:
  - Boolean Equations
    - Logic operations with binary numbers
  - Logic Gates
    - Basic blocks that are interconnected to form larger units that are needed to construct a computer

# Boolean Equations and Logic Gates

# Simple Equations: NOT / AND / OR

$\bar{A}$  (reads "not A") is 1 iff A is 0



A	$\bar{A}$
0	1
1	0

$A \cdot B$  (reads "A and B") is 1 iff A and B are both 1



A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

$A + B$  (reads "A or B") is 1 iff either A or B is 1




A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1
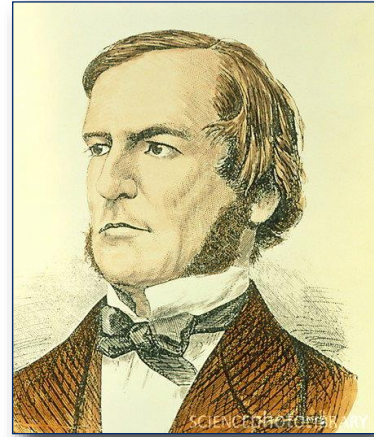
# Boolean Algebra: Big Picture

---

- An algebra on 1's and 0's
  - with AND, OR, NOT operations
- What you start with
  - **Axioms:** basic stuff about objects and operations you just assume to be true at the start
- What you derive first
  - **Laws and theorems:** allow you to manipulate Boolean expressions
  - ...also allow us to do some simplification on Boolean expressions
- What you derive later
  - More "sophisticated" properties useful for manipulating digital designs represented in the form of Boolean equations



# Common Logic Gates

### Buffer



A	Z
0	0
1	1

### AND



A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

### OR



A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

### XOR



A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

### Inverter



A	Z
0	1
1	0

### NAND




A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0

### NOR



A	B	Z
0	0	1
0	1	0
1	0	0
1	1	0

### XNOR

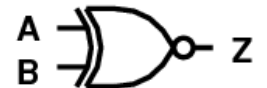

A	B	Z
0	0	1
0	1	0
1	0	0
1	1	1

# Boolean Algebra: Axioms

## *Formal version*

1.  $B$  contains at least two elements,  $0$  and  $1$ , such that  $0 \neq 1$

2. *Closure*  $a, b \in B$ ,  
(i)  $a + b \in B$   
(ii)  $a \cdot b \in B$

3. *Commutative Laws*:  $a, b \in B$ ,  
(i)  $a + b = b + a$   
(ii)  $a \cdot b = b \cdot a$

4. *Identities*:  $0, 1 \in B$   
(i)  $a + 0 = a$   
(ii)  $a \cdot 1 = a$

5. *Distributive Laws*:  
(i)  $a + (b \cdot c) = (a + b) \cdot (a + c)$   
(ii)  $a \cdot (b + c) = a \cdot b + a \cdot c$

6. *Complement*:  
(i)  $a + a' = 1$   
(ii)  $a \cdot a' = 0$

## *English version*

Math formality...

Result of AND, OR stays in set you start with

For primitive AND, OR of 2 inputs, order doesn't matter

There are identity elements for AND, OR, give you back what you started with

- distributes over +, just like algebra ...but + distributes over •, also (!!)

There is a complement element, ANDing, ORing give you an identity

# Boolean Algebra: Duality

---

- Interesting observation
  - All the axioms come in “dual” form
  - Anything true for an expression also true for its dual
  - So any derivation you could make that is true, can be flipped into dual form, and it stays true
- Duality -- More formally
  - A dual of a Boolean expression is derived by replacing
    - Every **AND** operation with... an **OR** operation
    - Every **OR** operation with... an **AND**
    - Every **constant 1** with... a **constant 0**
    - Every **constant 0** with... a **constant 1**
    - But don't change any of the literals or play with the complements!

**Example**

$$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$$
$$\rightarrow a + (b \cdot c) = (a + b) \cdot (a + c)$$



# Boolean Algebra: Useful Laws

---

Dual



*Operations with 0 and 1:*

1.  $X + 0 = X$
2.  $X + 1 = 1$

- 1D.  $X \cdot 1 = X$
- 2D.  $X \cdot 0 = 0$

AND, OR with identities gives you back the original variable or the identity

---

*Idempotent Law:*

3.  $X + X = X$

- 3D.  $X \cdot X = X$

AND, OR with self = self

---

*Involution Law:*

4.  $\overline{\overline{X}} = X$

double complement = no complement

---

*Laws of Complementarity:*

5.  $X + \overline{X} = 1$

- 5D.  $X \cdot \overline{X} = 0$

AND, OR with complement gives you an identity

---

*Commutative Law:*

6.  $X + Y = Y + X$

- 6D.  $X \cdot Y = Y \cdot X$

Just an axiom...

---

# Useful Laws (cont.)

---

## *Associative Laws:*

$$7. (X + Y) + Z = X + (Y + Z) \\ = X + Y + Z$$

$$7D. (X \cdot Y) \cdot Z = X \cdot (Y \cdot Z) \\ = X \cdot Y \cdot Z$$

Parenthesis order  
doesn't matter

## *Distributive Laws:*

$$8. X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$$

$$8D. X + (Y \cdot Z) = (X + Y) \cdot (X + Z) \quad \text{Axiom}$$

## *Simplification Theorems:*

$$9. X \cdot Y + X \cdot \bar{Y} = X$$

$$9D. (X + Y) \cdot (X + \bar{Y}) = X$$

$$10. X + X \cdot Y = X$$

$$10D. X \cdot (X + Y) = X$$

$$11. (X + \bar{Y}) \cdot Y = X \cdot Y$$

$$11D. (X \cdot \bar{Y}) + Y = X + Y$$

Useful for  
simplifying  
expressions

Actually worth remembering — they show up a lot in real designs...

# DeMorgan's Law

---

*DeMorgan's Law:*

$$12. \overline{(X + Y + Z + \dots)} = \bar{X} \cdot \bar{Y} \cdot \bar{Z} \cdot \dots$$

$$12D. \overline{(X \cdot Y \cdot Z \cdot \dots)} = \bar{X} + \bar{Y} + \bar{Z} + \dots$$

---

- **Think of this as a transformation**
  - Let's say we have:

$$F = A + B + C$$

- Applying DeMorgan's Law (12), gives us:

$$F = \overline{\overline{(A + B + C)}} = \overline{(\bar{A} \cdot \bar{B} \cdot \bar{C})}$$


# DeMorgan's Law (cont.)

Interesting — these are conversions between **different types of logic**

That's useful given you don't always have **every type of gate**

$$A = \overline{(X + Y)} = \bar{X}\bar{Y}$$

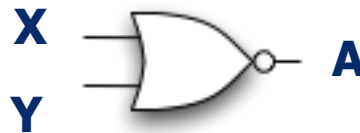**NOR is equivalent to AND with inputs complemented**



X	Y	$\overline{X+Y}$	$\bar{X}$	$\bar{Y}$	$\bar{X}\bar{Y}$
0	0	1	1	1	1
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	0

$$B = \overline{(XY)} = \bar{X} + \bar{Y}$$

**NAND is equivalent to OR with inputs complemented**



X	Y	$\overline{XY}$	$\bar{X}$	$\bar{Y}$	$\bar{X} + \bar{Y}$
0	0	1	1	1	1
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	0	0	0

# Part 1: A Comparator Circuit

---

- Design a comparator that receives two 4-bit numbers A and B, and sets the output bit EQ to logic-1 if A and B are equal



- **Hints:**
  - First compare A and B bit by bit
  - Then combine the results of the previous steps to set EQ to logic-1 if all A and B are equal

# Part 2: A More General Comparator

---

- Design a circuit that receives two 1-bit inputs A and B, and:
  - sets its first output (O1) to 1 if  $A > B$ ,
  - sets the second output (O2) to 1 if  $A = B$ ,
  - sets the third output (O3) to 1 if  $A < B$ .



# Part 3: Circuits with Only NAND Gates

---

- Design the circuit of Part 2 using **only NAND gates**
  
- **Logical Completeness:**
  - The set of gates {AND, OR, NOT} is **logically complete** because we can build a circuit to carry out the specification of any combinatorial logic we wish, without any other kind of gate
  
  - NAND and NOR are also logically complete

# Last Words

---

- In this lab, you will draw the schematics of some simple operations
- Part 1: A comparator circuit
- Part 2: A more general comparator circuit
- Part 3: Designing circuits using **only NAND gates**
- You will find **more exercises in the lab report**



# Report Deadline

---

23:59, 26 March 2021

---

# Digital Design & Computer Arch.

## Lab 1 Supplement: Drawing Basic Circuits

Prof. Onur Mutlu

ETH Zurich

Spring 2021

9 March 2021