

Design of Digital Circuits

Lab 2 Supplement: Mapping Your Circuit to an FPGA

Prof. Onur Mutlu

ETH Zurich

Spring 2021

16 March 2021

What Will We Learn?

- In Lab 2, you will:
 - Design a [4-bit adder](#).
 - Design a 1-bit full-adder.
 - Use full-adders to design a 4-bit adder.
 - Learn [how to map your circuits to an FPGA](#).
 - Program your FPGA using the [Vivado Design Suite](#) for HDL design.
 - Work with your FPGA board and see the results of your designs on the FPGA output.

Binary Addition

Binary Addition (1)


$$\begin{array}{rcccccc} & & & 0 & 1 & 1 & 1 & \longrightarrow & \boxed{A} \\ + & & & 1 & 0 & 1 & 0 & \longrightarrow & \boxed{B} \\ \hline \end{array}$$

Binary Addition (2)

$$\begin{array}{r} \\ + \\ \hline \end{array}$$

1  Carry


Binary Addition (3)

 

The Full-Adder (1)

$$\begin{array}{rcccccc} & & 1 & \mathbf{1} & \mathbf{1} & & \\ & & & 0 & \mathbf{1} & 1 & 1 \\ + & & & 1 & \mathbf{0} & 1 & 0 \\ \hline & & 1 & 0 & \mathbf{0} & 0 & 1 \end{array}$$

The Full-Adder (2)

 

Design an Adder (1)

- Design a full-adder:

- **Inputs:** input 1 (A), input 2 (B), carry-in (C_{in}).
- **Outputs:** sum (S), carry-out (C_{out}).
- All inputs and outputs are 1-bit wide.

- **Example:**

- $A = 1, B = 1, C_{in} = 1$
- $S = 1, C_{out} = 1$




Design an Adder (2)

- Design a 4-bit adder:
 - Receives two 1-bit numbers A and B and a 1-bit input carry (C_{in})
 - Returns outputs S and C as sum and carry of the operation, respectively.

■ Example: A = 1110, B = 0001, $C_{in}=1$

- S = 0000
- C = 1

 

- **Hint:** Use four full-adders to design a 4-bit adder.

Design an Adder (Overview)

1. You will use **truth tables** to derive the **Boolean equation** of the adder.
2. You will design the **schematic of the circuit** using logic gates.
3. You will use Vivado to write your design in **Verilog**.
4. You will use Vivado to **program the FPGA**.

Vivado Design Suite

- We will use the **Vivado Design Suite** for FPGA programming.
 - Vivado is installed in the computers in the lab rooms.
 - If you wish to use your own computer, you can follow these instructions:
<https://reference.digilentinc.com/learn/programmable-logic/tutorials/basys-3-getting-started/start>



Verilog

Defining a Module in Verilog


- A **module** is the main building block in Verilog.
- We first need to define:
 - **Name** of the module
 - **Directions** of its **ports** (e.g., **input**, **output**)
 - **Names** of its **ports**
- Then:
 - Describe the **functionality** of the module.



Implementing a Module in Verilog

  


Structural HDL: Instantiating a Module

 

Schematic of module "top" that is built from two instances of module "small"

Structural HDL Example (1)

■ Module Definitions in Verilog

 


```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```

Structural HDL Example (2)

■ Module Definitions in Verilog

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```


```
endmodule
```

Structural HDL Example (3)

■ Defining wires (module interconnections)

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```

```
endmodule
```


Structural HDL Example (4)

■ The first instantiation of the "small" module

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
// instantiate small once  
small i_first ( .A(A),  
                .B(SEL),  
                .Y(n1) );
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```


```
// description of small
```

```
endmodule
```

Structural HDL Example (5)

■ The second instantiation of the “small” module
 
```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
  // instantiate small once  
  small i_first ( .A(A),  
                 .B(SEL),  
                 .Y(n1) );  
  
  // instantiate small second time  
  small i_second ( .A(n1),  
                  .B(C),  
                  .Y(Y) );  
  
endmodule
```




```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```

Structural HDL Example (6)

■ Short form of module instantiation

 
```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
  // alternative  
  small i_first ( A, SEL, n1 );  
  
  /* Shorter instantiation,  
     pin order very important */  
  
  // any pin order, safer choice  
  small i_second ( .B(C),  
                  .Y(Y),  
                  .A(n1) );  
  
endmodule
```



```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```

What about logic gates?

Instantiating Logic Gates: The NOT Gate

 

A	\bar{A}
0	1
1	0

```
not my_not(output, input);
```

gate type

gate name

output signal

input signal

Instantiating Logic Gates: The AND Gate (1)



<i>A</i>	<i>B</i>	<i>A • B</i>
0	0	0
0	1	0
1	0	0
1	1	1

gate type gate name output signal input signals

```
and my_and(output, input1, input2);
```

Instantiating Logic Gates: The AND Gate (2)



<i>A</i>	<i>B</i>	<i>A • B</i>
0	0	0
0	1	0
1	0	0
1	1	1

gate type gate name output signal input signals

```
and my_and(output, input1, input2);
```

or...

```
and my_and(output, input1, input2, input3, ...);
```

gate type gate name output signal input signals
(as many as you want)

Instantiating Logic Gates: More Gates...


```
not my_not(output, input);

and my_and(output, input1, input2, ...),
or my_or(output, input1, input2, ...);
xor my_xor(output, input1, input2, ...);

nand my_nand(output, input1, input2, ...);
nor my_nor(output, input1, input2, ...);
xnor my_xnor(output, input1, input2, ...);
```

Instantiating Logic Gates: A Simple Example (1)

$$\mathit{out} = \bar{A} \cdot \bar{B}$$

 

Instantiating Logic Gates: A Simple Example (2)


```
// Notice the alternative port declaration
module check_zeros (
    input A,
    input B,
    output out
);

// wires for the intermediate signals
wire not_a, not_b;

// instantiate the NOT gates
not(not_a, A);
not(not_b, B);

// instantiate the AND gate
and(out, not_a, not_b);

endmodule
```

 


Basys 3 FPGA Board

In this course, we will be using the Basys 3 boards from Digilent, as shown below.

You can learn more about the Basys 3 Starter Board from:
 
<http://store.digilentinc.com/basys-3-artix-7-fpga-trainer-board-recommended-for-introductory-users/>



For this week's lab:

Output LEDs

Input Switches

Last Words

- In this lab, you will map your circuit to an FPGA.
- First you will design a full-adder. You will then use the full-adder as a building block to build a 4-bit adder.
- Then, you will learn how to use Xilinx Vivado for writing Verilog and how to connect to the Basys 3 board.
- Finally, you will program the FPGA and get the circuit running on the FPGA board.
- You will find **more exercises in the lab report.**

Report Deadline

23:59, 2 April 2021

Design of Digital Circuits

Lab 2 Supplement:

Mapping Your Circuit to FPGA

Prof. Onur Mutlu

ETH Zurich

Spring 2021

16 March 2021