

# Design of Digital Circuits

## Lab 4 Supplement: Finite-State Machines

Prof. Onur Mutlu

ETH Zurich

Spring 2021

30 March 2021

# What Will We Learn?


---

- In Lab 4, you will **implement a finite-state machine using Verilog.**
- Design and implement a simple circuit that emulates the blinking lights of a Ford Thunderbird.
- Understand how the **clock signal is derived in the FPGA board.**
- **Write an FSM** that implements the Ford Thunderbird blinking sequence.
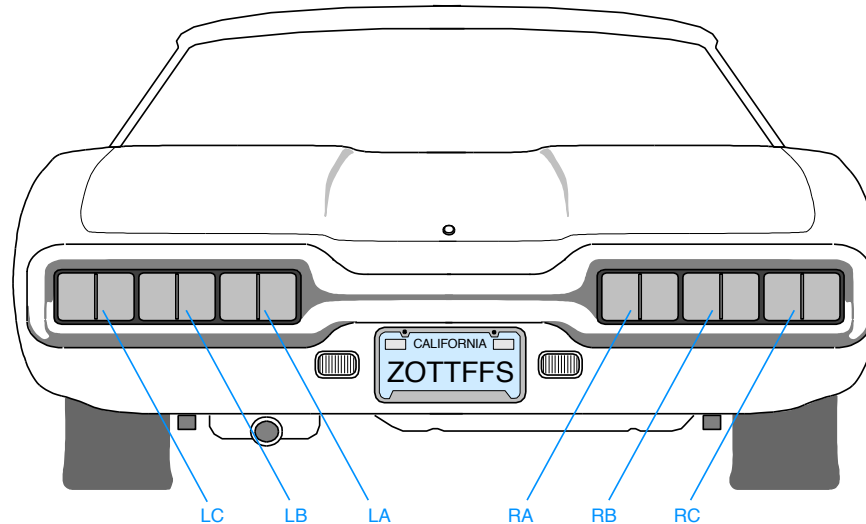
# Tail Lights of a 1965 Ford Thunderbird

---

- In this lab, you will design a finite-state machine to control the tail lights of a 1965 Ford Thunderbird.




Copyright © 2000 by Prentice Hall, Inc.  
Digital Design Principles and Practices, 3/e
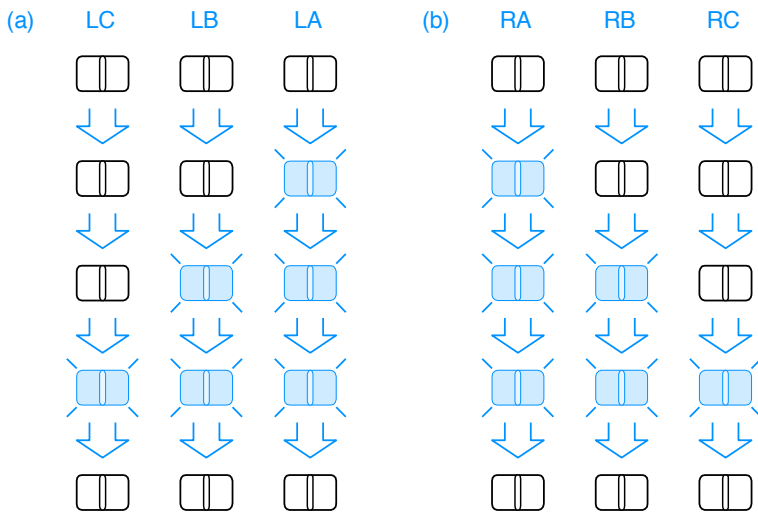
# Tail Lights of a 1965 Ford Thunderbird

- There are three lights on each side that operate in sequence to indicate the direction of a turn.

Copyright © 2000 by Prentice Hall, Inc.  
Digital Design Principles and Practices, 3/e



Copyright from ClassicLEDs.com



# Part 1: FSM Design

---

- An FSM must do three things:
  - **Next State Logic:** Determine the next state from **the present state and the inputs.**
  - **Output Logic:** **Determine the output signals** based on the present state and input signals.
  - **State Register:** keeps track of the present state; must be **updated at every clock cycle.**

The manual contains the details of this FSM specifications.

# Part 1: FSM Design

---

- An FSM must do three things:
  - **Next State Logic:** Determine the next state from **the present state and the inputs.**
  - **Output Logic:** **Determine the output signals** based on the present state and input signals.
  - **State Register:** keeps track of the present state; must be **updated at every clock cycle.**


For more details please refer to [lecture 6](#):

- Slide 67: Finite-State Machines.
- Slide 113: Moore vs. Mealy FSMs.

# Part 2: Verilog Implementation

---


- Separate three parts of the code:

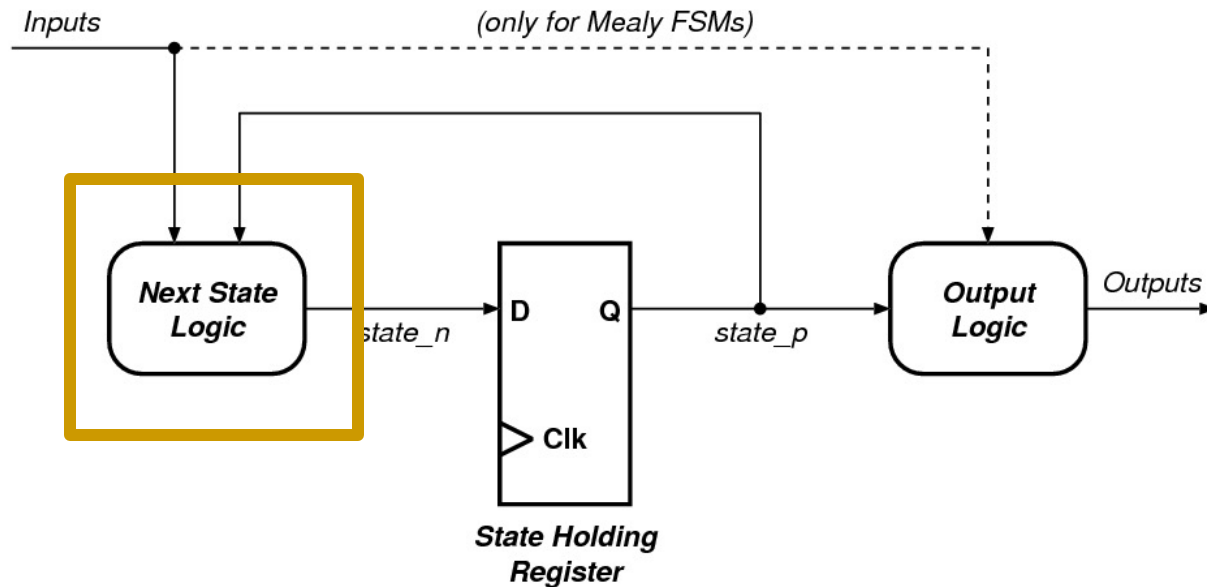

# Part 2: Verilog Implementation

---

- Separate three parts of the code:

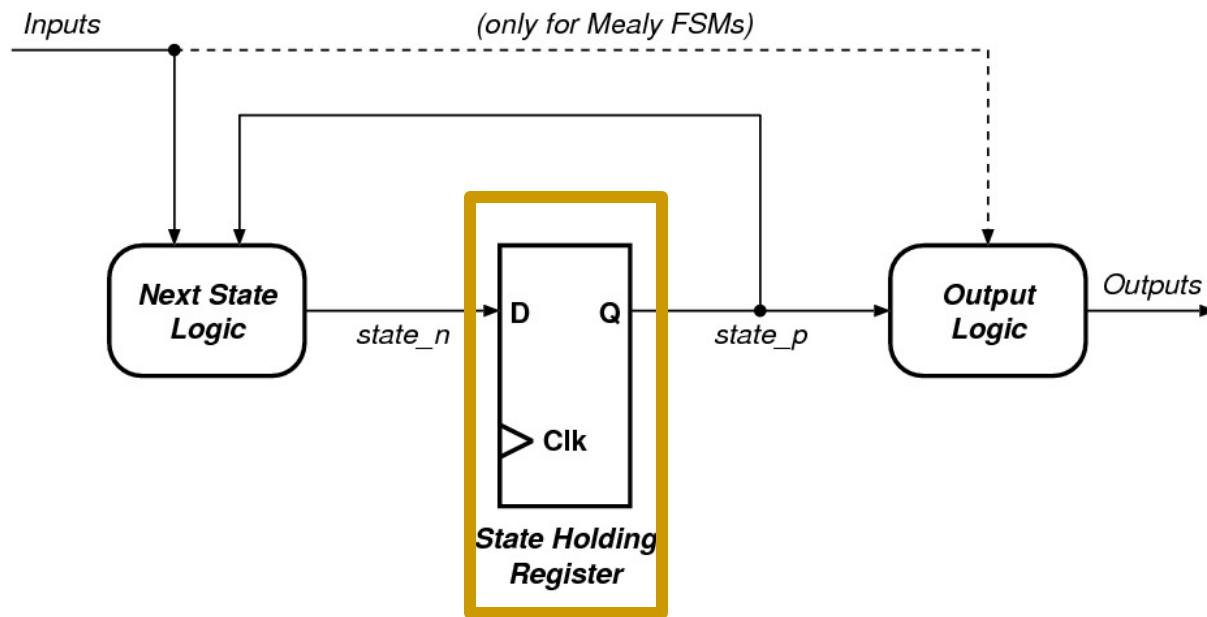




# Part 2: Verilog Implementation


---

- Separate three parts of the code:

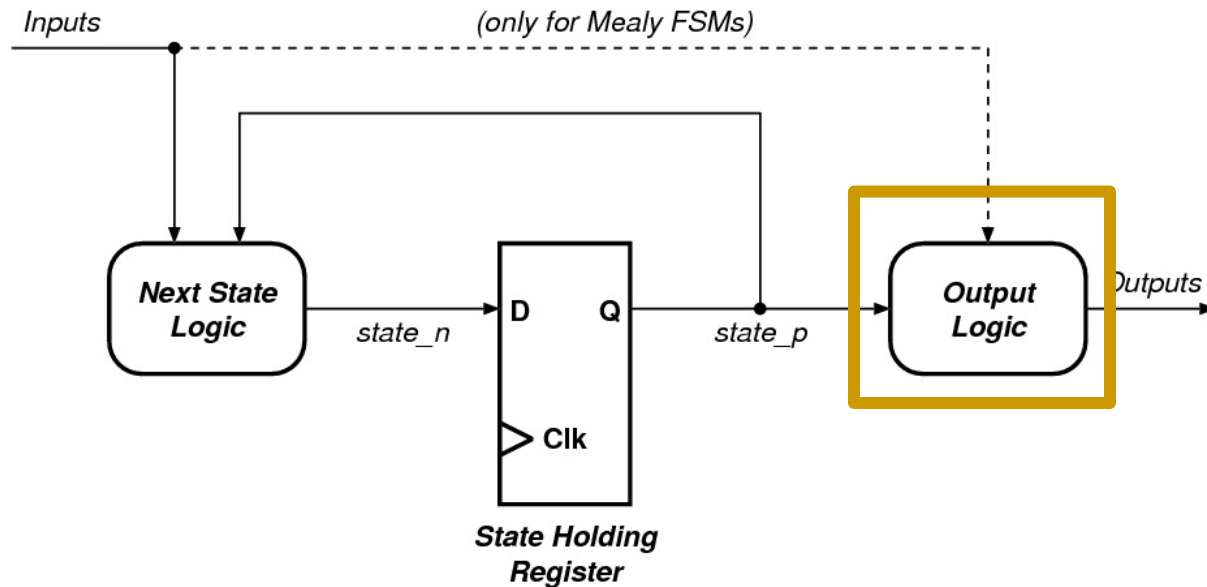
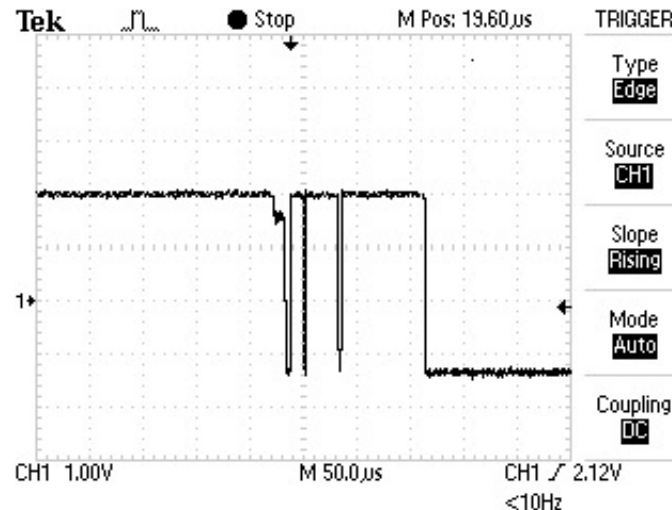
# Part 3: Implementing the Clock (I)

- The problem of using push-buttons as clock:
  - Compared to the speed of the FPGA the change in a push button is *very* slow ( $\sim$  1 million times slower)
  - During the slow transition, the FPGA will see many fast occurring transitions and would interpret each of them as a clock edge. (Bouncing)



# Part 3: Implementing the Clock (II)

---

- **CLK100Mhz (W5):** Your board contains a 100Mhz crystal oscillator circuit.
- **Problem:** The clock is too fast.
- **Solution:** A clock divider:

```
module clk_div(input clk, input rst, output clk_en);  
    reg [24:0] clk_count;  
    always @ (posedge clk)  
        //posedge defines a rising edge (transition from 0 to 1)  
        begin  
            if (rst)  
                clk_count <= 0;  
            else  
                clk_count <= clk_count + 1;  
            end  
            assign clk_en = &clk_count;  
        endmodule
```

# Part 4: Defining the Constraints

---

- We must specify constraints for:
  - Buttons for control
  - LEDs for output lights
  - Connections for clock

The manual contains more information  
about the constraints.

# Last Words

---

- In Lab 4, you will **implement a finite-state machine using Verilog**.
- Design and implement a simple circuit that emulates the blinking lights of a Ford Thunderbird.
- Understand how the **clock signal is derived in the FPGA board**.
- **Write an FSM** that implements the Ford Thunderbird blinking sequence.
- In the report you will implement a **dimming function**, so that the lights are not only on and off, but can have intermediate levels

# Report Deadline

---

**23:59, 30 April 2021**

# Design of Digital Circuits

## Lab 4 Supplement: Finite-State Machines

Prof. Onur Mutlu

ETH Zurich

Spring 2021

30 March 2021